

Synchronous Sequential Logic

2019. 4. 29.

K-S. Sohn




Contents

- Sequential circuits
- Latches
- Flip-flops
- Analysis of clocked sequential circuits
- State reduction and assignment
- Design of sequential circuits

Synchronous Sequential Logic

-2-



Introduction

- Combinational circuits
 - neither memory element nor feedback
 - $\langle \text{output} \rangle = F(\langle \text{input} \rangle)$


Synchronous Sequential Logic

-3-



Sequential circuits


- Block diagram of sequential circuit

 

- feedback path
- memory element

Synchronous Sequential Logic

-4-

 

Sequential Circuits

□ State


- the binary information stored in the memory element at any given time defines the state of the sequential circuit at that time.
- $\langle \text{output} \rangle = F(\langle \text{state} \rangle, \langle \text{input} \rangle; \langle \text{control signal} \rangle)$

□ Synchronous

- the transition happens at discrete instants of time

□ Asynchronous

 
- the transition happens at any instant of time



Sequential Circuits

□ Asynchronous sequential circuits

 - having only feedback path (or with the "pseudo-memory")
- $\langle \text{output} \rangle = F(\langle \text{state} \rangle, \langle \text{input} \rangle)$
- difficult to avoid instability in design



Synchronous Sequential Circuits

□ Clock generator


- a master-clock generator to generate a periodic train of clock pulses
- the clock pulses are distributed throughout the system

□ clocked sequential circuits

- most commonly used
- no instability problems

□ clock speed

 - limited by the operational speed of the combinational circuit



Synchronous Sequential Circuits


□ the memory elements: flip-flops

- binary cells capable of storing one bit of information
- two outputs: one for the normal value and one for the complement value
- maintain a binary state indefinitely until directed by an input signal to switch states



Synchronous Sequential Circuits

□ Synchronous clocked sequential circuit

 

(a) Block diagram



(b) Timing diagram of clock pulses




Latches

□ asynchronous sequential circuits

- binary state (0 or 1)
- $Q(t+1) = F(Q(t), \text{input})$


□ Level sensitive circuits

 - the next state is determined by the level of inputs and the current state
- can not be used for synchronous sequential circuits,
- but, building blocks of flip-flop



SR Latch

 □ Two NOR gates with cross-coupled connection



(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(b) Function table



SR Latch

□ Most fundamental building block


- more complicated types can be built upon this SR latch

□ Functional characteristics

- (S,R)=(0,0): no operation (usual position of the level of inputs)
- (S,R)=(0,1): reset (Q=0, the clear state)
- (S,R)=(1,0): set (Q=1, the set state)
- (S,R)=(1,1): indeterminate state (Q=Q'=0, out of SR rules)

SR Latch

 - NAND implementation
 - complement of the NOR version
 - S'R' latch




Synchronous Sequential Logic

-13-

SR Latch

 - SR latch with control input
 - $En = 0$, no change
 - $En = 1$, enable input




Synchronous Sequential Logic

-14-

D Latch

 - Design objectives
 - eliminate the undesirable conditions of the indeterminate state in the SR latch by using an inverter and tied inputs
- 'D' comes from:
 - $Q = \text{input data}$, transparent latch




Synchronous Sequential Logic


-15-

Graphic Symbols

- SR latches

 

- D latch

 

Synchronous Sequential Logic

-16-


Flip-Flops

- Trigger
 - the momentary change of control inputs
 - the state of a latch or flip-flop is switched by a change of the control input

□ Level triggered: latch




□ Edge triggered: F-F

 

Flip-Flop

□ Why F-F as the memory element in the S.S.L.?

- If a latch used:

 

- the feedback path may cause instability problem


□ Edge-triggered F-Fs

- the state transition happens only at the edge
- eliminate the multiple-transition problem

Edge-triggered D Flip-Flop

□ Master-slave D flip-flop

 
- two separate D latches and an inverter
- master latch (triggered during clk's positive level)
- slave latch (triggered during clk's negative level)




- triggered at negative or positive edge?
- how to reverse the direction of triggering edge?

Edge-triggered D Flip-Flop

□ D type positive-edge triggered F-F

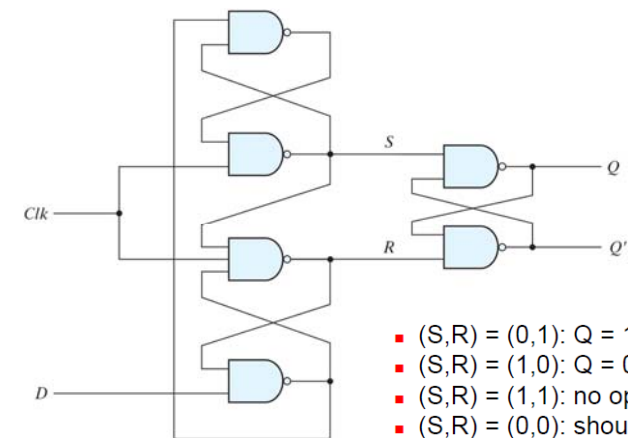

 
- (S,R) = (0,1): Q = 1
- (S,R) = (1,0): Q = 0
- (S,R) = (1,1): no operation
- (S,R) = (0,0): should be avoided



Edge-triggered D Flip-Flop

□ In sum.


 
- $CP=0$: $(S,R) = (1,1)$, no state change
- $CP=\uparrow$: state change once
- $CP=1$: state holds
- eliminate the feedback problems in sequential circuits



Graphic Symbols of D F-F

□ The edge-triggered D F-F

  - the most economical and efficient
- positive-edge and negative-edge





Specifications of Flip-Flop

□ Setup time

- A minimum time for which the D input must be maintained at a constant value prior to the occurrence of the clock transition

□ Hold time

  
- A minimum time for which the D input must not change after the application of the positive transition of the clock




Specification of Flip-Flop

□ Time contribution analysis

 - setup time $> td1 + td4$
- hold time $> td3$



 


JK Flip-Flop

Operational requirements

- Set: $J=1, K=0, Q(t+1)=1$
- Reset: $J=0, K=1, Q(t+1)=0$
- Complement: $J=1, K=1, Q(t+1)=Q'(t)$
- No change: $J = K = 0, Q(t+1)=Q(t)$

Constraints

 - Use D F-F and some logic gates including inverters



Synchronous Sequential Logic

-25-




JK Flip-Flop

Front logic


- $D = JQ' + K'Q$
- How?

Logic diagram and graphical symbol

 

Synchronous Sequential Logic

-26-

 


T Flip-Flop

Functional requirements

- toggle output with a T input
- $T=0, Q(t+1)=Q(t)$
- $T=1, Q(t+1)=Q'(t)$

Constraints

- Use D F-F and some logic gates

 

Synchronous Sequential Logic

-27-




T Flip-Flop

Front logic

- $D = TQ' + T'Q$
- Why?

Logic diagram and graphical symbol

 

Synchronous Sequential Logic

-28-

Characteristics Tables

□ t

- a period of the clock pulse
- $(t+1)$ means the next clock pulse period

□ $Q(t)$

- present state

□ $Q(t+1)$

- next state

J/K Flip-Flop			
J	K	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

D Flip-Flop			T Flip-Flop		
D	$Q(t+1)$		T	$Q(t+1)$	
0	0	Reset	0	$Q(t)$	No change
1	1	Set	1	$Q'(t)$	Complement

Characteristic Equations

□ D flip-flop

- $Q(t+1) = D$

□ JK flip-flop


- $Q(t+1) = JQ' + K'Q$

□ T flip-flop

- $Q(t+1) = TQ' + T'Q$

Direct Inputs

□ Asynchronous set and/or reset

 

Analysis of Clocked sequential Circuits(SSC)

□ Analysis of clocked sequential circuit(SSC)


- the behavior of a clocked sequential circuit is determined from the inputs, the outputs, and the state of its flip-flops
- SSC(synchronized sequential circuits)

□ Clocked sequential circuit

- $\langle \text{output} \rangle = \text{FUNC}(\langle \text{inputs} \rangle, \langle \text{curr state} \rangle)$
- $\langle \text{next state} \rangle = \text{FUNC}(\langle \text{inputs} \rangle, \langle \text{curr state} \rangle)$

□ Results of analysis

 - State equations
- State table
- State diagram



State Equations(Transition Equation)

Definition

- Algebraic expression of the condition of state transition \Rightarrow Transition equation

Objectives -- Specifying the next state of the SSC by:


- Specifying the output of flip-flop
- Deriving the output of SSC \Rightarrow Output equation

Specifying the output of flip-flop

- $\langle \text{F-F output} \rangle(t+1) = \text{FUNC}(\langle \text{F-F output} \rangle(t), \langle \text{input} \rangle(t))$
- $(t+1)$: one clock edge later than time (t)

Output equation

 - $\langle \text{SSC output} \rangle(t) = \text{FUNC}(\langle \text{F-F output} \rangle(t), \langle \text{input} \rangle(t))$



State Table(Transition Table)

Structure of the state table

All possible combinations of states and inputs

Present state	Inputs	Next state	Outputs
		$\text{FUNC}(\langle \text{present state} \rangle, \langle \text{input} \rangle)$	
			$\text{FUNC}(\langle \text{present state} \rangle, \langle \text{input} \rangle)$
List of all possible states of flip-flops at a given time t or t -th clock edge	All possible values of inputs for each present state	States of the flip-flops at a given time $t+1$ or $(t+1)$ -th clock edge	Values of outputs for each possible input and present state



State Table

Derivation of a state table

Present states	Inputs	Next states	Outputs
row ₀			
using state eq. or characteristic table			
row _{N-1}			
using output eq.			

All combination of present state values and input values (m flip-flops and n inputs $\Rightarrow 2^{m+n}$ rows)




State Diagram

Objectives

- A graphical representation of a state table
- Easier human interpretation

Components

 
- Bubbles(states) and directed lines(transitions)



F-F Input Equations

Definition

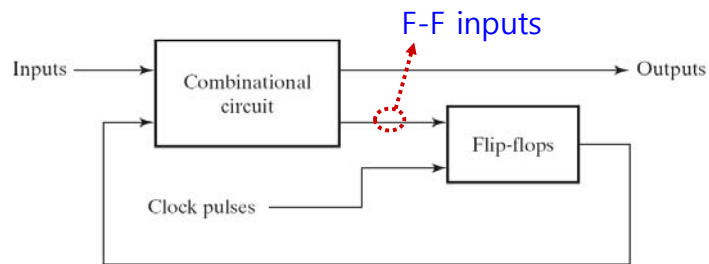- Output functions of the combinational circuit generating the F-F input.
- Only an internal expression used for deriving the state equations




Synchronous Sequential Logic

-37-

Overview of Analysis of SSC

Flow diagram of analysis of SSC

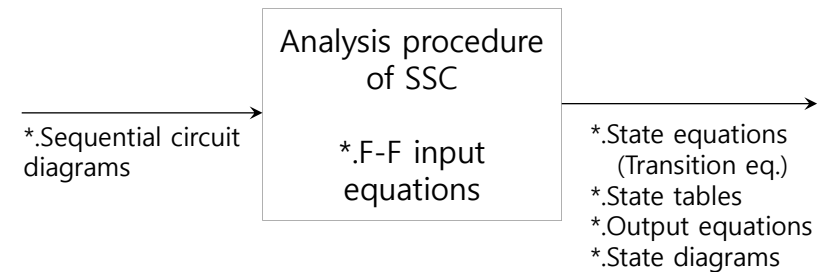

Synchronous Sequential Logic

-38-

Analysis Procedure

- Step-1. Check if clocked seq. circuit
- Step-2. F-F input equations
 - Use the given circuit diagram
- Step-3. Output equations
 - Use the given circuit diagram
- Step-4. State tables
 - Generate full combination of <present states> and <inputs>
 - Refer F-F's characteristic tables to get <next state> columns
- Step-5. State equations
 - Use the state table and K-map or given circuit diagram
- Step-6. State diagrams
 - Use the state table or given circuit diagram

Synchronous Sequential Logic

-39-

Analysis Example

- Circuit diagram
- Input equations

$$D_A = Ax + Bx$$

$$D_B = A'x$$


- State equations

$$A(t+1) = D_A(t) = A(t)x + B(t)x$$

$$B(t+1) = D_B = A'(t)x$$

- Output equations

$$y = (A + B)x'$$

 

Since the next state of D F-F. is determined only the F-F. input D.

Synchronous Sequential Logic

-40-

Analysis Example

State table

state equations

$$A(t+1) = D_A(t) = A(t)x + B(t)x$$

$$B(t+1) = D_B = A'(t)x$$

all binary combination of present states and inputs

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

$$y = (A + B)x'$$

Output equations

Synchronous Sequential Logic

-41-

Analysis Example

State table

State equation

			1	
		1	1	

$$A_{t+1} = A_t x + B_t x$$

		1	1	

$$B_{t+1} = A'_t x$$

Output equation

			1	
1			1	

$$y_t = (A_t + B_t)x'$$

Synchronous Sequential Logic

-42-


Analysis Example

State diagram

(transition diagram)

present input and output

 after the next clock cycle, the circuit goes to the next state 01.



Synchronous Sequential Logic

-43-

Analysis Example

F-F input equations (excitation equations)


$$D_A = Ax + Bx$$

$$D_B = A'x$$

- fully specify the combinational logic that drives the F-F's
- necessary for drawing full logic diagram
- imply the type of F-F from the letter symbol (D_A , J_B , K_B , T_C , ...)

Synchronous Sequential Logic

-44-

 


Analysis with D F-F

Input equation

$$D_A = A \oplus x \oplus y$$


- the D_A symbol implies a D F-F with output A
- x, y are the inputs to the circuit.
- no output equation means that <output> = <F-F output>

Logic diagram

 

Synchronous Sequential Logic

-45-

 

Analysis with D F-F's


State table

- 1 col. for curr. state, 2 col's for inputs, 1 col. for next state.

State equation

$$A(t+1) = A(t) \oplus x(t) \oplus y(t)$$


State diagram

 

Synchronous Sequential Logic

-46-

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

Analysis with JK F-F's

Structure of the state table with JK F-F

- 4 sections: <present state>, <inputs>, <next state>, <outputs>
- all combination of {<present state>, <inputs>}

Present State	Input	Next State	Output

Synchronous Sequential Logic

-47-




Analysis with JK F-F's

Derivation steps of the next-state values in the state table

- Determine the F-F input equation
 - in terms of the present state and input variables
- List the binary values of each input equation
- Use the F-F characteristic table
 - to determine the next-state values in the state table

Synchronous Sequential Logic


-48-

 

Analysis with JK F-F's (Ex.)

Given circuit diagram

 - 1 input, 2 JK F-F's (2-bit state value), no output (F-F's outputs may be considered as the circuit outputs)



Synchronous Sequential Logic

-49-



Analysis with JK F-F's (Ex.)

F-F input equations


$$J_A = B, \quad K_A = Bx'$$

$$J_B = x', \quad K_B = A \oplus x = A'x + Ax'$$

F-F input binary values

Present State		Input	Next State	Flip-Flop Inputs			
A	B	x		J _A	K _A	J _B	K _B
0	0	0		0	0	1	0
0	0	1		0	0	0	1
0	1	0		1	1	1	0
0	1	1		1	0	0	1
1	0	0		0	0	1	1
1	0	1		0	0	0	0
1	1	0		1	1	1	1
1	1	1		1	0	0	0

Synchro

 

Analysis with JK F-F's (Ex.)

Determine the next state(1)

- current input JK value and the characteristic table

JK Flip-Flop		Q(t + 1)	
J	K	Q(t)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	J _A	K _A	J _B	K _B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

Synchronous Sequential Logic

-51-



Analysis with JK F-F's (Ex.)

Derive state equations

- JK F-F characteristic equations

$$Q(t+1) = JQ' + K'Q$$

$$A(t+1) = JA' + K'A \quad B(t+1) = JB' + K'B$$

- substitute input eq. into char. eq.

$$A(t+1) = BA' + (Bx')'A = A'B + AB' + Ax$$

$$B(t+1) = x'B' + (A \oplus x)'B = B'x' + ABx + A'Bx'$$

Synchronous Sequential Logic

-52-



Analysis with JK F-F's (Ex.)

□ Determine the next state value(2)

- obtain the next state value by evaluating the state equations
- the state equations can be obtained by substituting the F-F input equations into the F-F characteristic equation

Present State		Input <i>x</i>	Next State	
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1


Synchronous

-53-



Analysis with JK F-F's (Ex.)

□ State diagram

 

Synchronous Sequential Logic

-54-



Analysis with T F-F's

□ Review

- T F-F characteristic table

T Flip-Flop		
<i>T</i>	<i>Q(t + 1)</i>	
0	<i>Q(t)</i>	No change
1	<i>Q'(t)</i>	Complement

- characteristic equation

$$Q(t+1) = T \oplus Q = T'Q + TQ'$$


Synchronous Sequential Logic

-55-




Analysis with T F-F's

□ Given circuit diagram

 

Synchronous Sequential Logic

-56-

 

Analysis with T F-F's

Input equations

$$T_A = Bx$$

$$T_B = x$$

Output equation

$$y = AB$$

State equations

$$A(t+1) = (Bx)'A + (Bx)A' = AB' + Ax' + A'Bx$$


$$B(t+1) = x \oplus B$$



Analysis with T F-F's

State table



Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

 

Analysis with T F-F's

State diagram

- Binary counter as long as $x=1$

  


Mealy and Moore Models of FSM

General model of a sequential circuit

- inputs, outputs, and internal states

Mealy model

 - Output is a function of both the present state and input
- $\langle \text{output} \rangle = \text{FUNC}(\langle \text{input} \rangle, \langle \text{present state} \rangle)$
- the output should be sampled immediately before the active edge of the clock with concerning the output stabilization.






Mealy and Moore Models of FSM

Moore model

 - output is a function of the present state only
- $\langle \text{output} \rangle = \text{FUNC}(\langle \text{present state} \rangle)$
- the output is synchronized with the clock
- Examples:
 - circuit output is the flip-flop states



Synchronous Sequential Logic

-61-




State Reduction and Assignment

Number of F-F's in a SC

- determined as $\log_2 N$, where N is the number of required states
- cost $\propto N$
- in general, state reduction is needed.


As an example, a state diagram is given

- 7 states: a ~ g

 

Synchronous Sequential Logic

-62-

 

State Reduction

Input-output relationship (a is the initial state)

- input: 01010110100
- output: 00000110100

state	a	a	b	c	d	e	f	f	g	f	g	a
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

State reduction problem

- to find ways of reducing N without altering the input-output relationships

Synchronous Sequential Logic

-63-




State Reduction

State table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Synchronous Sequential Logic

-64-

 

State Reduction

- ❑ two circuits are equivalent:
 - have identical outputs for all input sequences
 - the number of states is not important
- ❑ Two states are said to be equivalent:
 - for each member of the set of inputs, they give exactly the same output and send the circuit to the same state or to an equivalent state
 - one of them can be removed




State Reduction

- ❑ Find the equivalent states in the state table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

 ☞ *e* and *g* are equivalent. '*e*' or '*g*' can be eliminated if '*g*' is eliminated, all '*g*' is replaced by '*e*' and the row that '*g*' is the present state is eliminated from both the table and the diagram.



State Reduction

- ❑ Reduced state table(1)

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1

☞ *d* and *f* are equivalent again. '*d*' or '*f*' can be eliminated. If '*f*' is eliminated, all '*f*'s are replaced by '*d*' and the row that '*f*' is the present state is erased.




State Reduction

- ❑ Reduced state table(2)

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

State Reduction

Reduced state diagram

 

State Reduction

Test of reduction (a is the initial state)

input: 01010110100

output: 00000110100

state	a	a	b	c	d	e	d	d	e	d	e	a
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

State Assignment

Why assign values to states

- to design a SC with physical components.

Possible state binary assignment

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
a	000	000	00001
b	001	001	00010
c	010	011	00100
d	011	010	01000
e	100	110	10000

- gray code: simplification of the Boolean function
- one-hot : use easy decoder logic

State Assignment

Reduced state table with binary assignment

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1

- Unused states can be considered as don't care




Design Procedure Overview

[!] We usually know the transition from present state to next state and wish to find the F-F, input conditions that will cause the required transition

Requirement spec.'s

- Word statements
- State tables ...

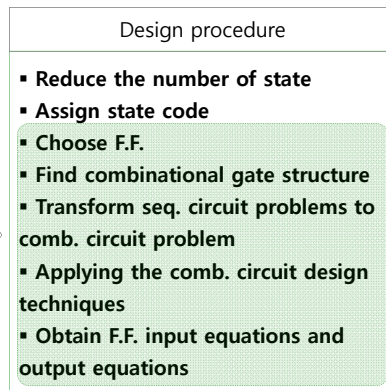[!] Truth tables is the sufficient requirement spec. for combinational circuit



❖ Circuit diagrams
❖ Boolean functions

→ Synthesis

Synchronous Sequential Logic

-73-




Requirements Specification

- Word description
 - the word description of the circuit behavior
- State representation
 - state diagram
 - state table
 - state equation
- Etc.
 - block diagram
 - truth table

Synchronous Sequential Logic

-74-

 

Design Procedure

- Core of design procedure
 - state reduction if necessary
 - assign binary values to the states
 - obtain the binary-coded state table
 - choose the type of flip-flops
 - derive the simplified flip-flop input equations and output equations
 - draw the logic diagram

Synchronous Sequential Logic


-75-



 Example: Bit Sequence Detector

- Word description
 - We wish to design a circuit that detects three or more consecutive 1's in a string of bits coming through an input line
- State diagram

Moore model
∴ output is determined by the state



Synchronous Sequential Logic

-76-

Ex.) Bit Sequence Detector

- Construct a state table
 - by assigning binary value to each state

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

Synchronous Sequential Logic

-77-

Synthesis with D F-F's

- Number of F-F's
 - 2 D F-F's to represent 4 states
- Characteristic function

$$Q(t+1) = D_Q$$
- State equation

$$A(t+1) = \sum(3, 5, 7) = Ax + Bx$$

$$B(t+1) = \sum(1, 5, 7) = Ax + B'x$$
- Output equation

$$y(A, B, x) = \sum(6, 7) = AB$$

Synchronous Sequential Logic

-78-


Synthesis with D F-F's

- Input equation
 - Input function is the same form as state equation

$$D_A = Ax + Bx$$

$$D_B = Ax + B'x$$

- Circuit diagram

 

Synchronous Sequential Logic

Excitation Table

- Definition of excitation table
 - Explains the requirement for state transition of the sequential circuits
 - Represents the F-F. input conditions required for the given change of state
- Why excitation table?
 - F-F. input equations can not be derived directly from the state table in case of JK and T F-F.s.
- [C.F.] Characteristic tables
 - Provide the value of the next state of a F-F. when the F-F. inputs and present state are known
 - Provides the information for constructing the excitation table

Synchronous Sequential Logic

-80-

Excitation Table

- Typical form of excitation table

<Present state»Next state>	<F-F. inputs>
List of given changes of states	List of F-F. inputs required for each state transition

- Excitation tables of JK F-F. and T F-F.

$Q(t)$	$Q(t = 1)$	J	K	$Q(t)$	$Q(t = 1)$	T
0	0	0	X	0	0	0
0	1	1	X	0	1	1
1	0	X	1	1	0	1
1	1	X	0	1	1	0

Synchronous Sequential Logic

-81-

Synthesis with JK F-F's

- State table and JK F-F inputs

- JK F-F input equations are derived from the excitation table

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J _A	K _A	J _B	K _B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Excitation table

Excitation table

Synchronous Sequential Logic

-82-

Synthesis with JK F-F's

- Derive JK F-F. input equations

- Using the extended state table

$$J_A = Bx'$$

$$K_A = Bx$$

$$J_B = x$$

$$K_B = (A \oplus x)'$$

<present state>	<inputs>	<F-F. inputs>

[NOTE] <next state> is not used for deriving the F-F. input equations

Bx		B		
00	01	11	10	
A				
0				
1	X	X	X	X

$J_A = Bx'$

Bx		B		
00	01	11	10	
A				
0	X	X	X	X
1				

$K_A = Bx$

Bx		B		
00	01	11	10	
A				
0		1	X	X
1	1	X	X	

$J_B = x$

Bx		B		
00	01	11	10	
A				
0	X	X		1
1	X	X	1	


$K_B = (A \oplus x)'$

Synchronous Sequential Logic

-83-

Synthesis with JK F-F's


- Circuit diagram

 

Synchronous Sequential Logic

-84-

 - The counter is driven by the clock signal
- There's no input and no output notation



-85-

- from the state diagram and T F-F excitation table

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

-86-

- From the extended state table and by simplifying with K-maps

$$T_{A_2} = A_1 A_0$$




$$T_{A1} = A_0$$



$$T_{A0} = 1$$

-87-

 

-88-



Discussion ~ ~ ~