

Ch. 06. Registers and Counters



2019. 5. 13.

K-S. Sohn



Contents



Registers and Counters

❑ Register

- A clocked sequential logic
- n-bit register \Rightarrow n flip-flops

❑ Counter

- A register with determined sequence of states
- Ripple counter
 - Cascaded clock signal \Rightarrow ripple effect
- Synchronous counter
 - Common clock signal

A Basic Register

❑ 4-bit register with 4 D flip-flops

○ Signals


- R : reset with clear signal
- C : clock signal input

○ Data input(4bit binary) : $I_0 \sim I_4$

○ Data output(4bit binary) : $A_0 \sim A_4$

○ State transition

 - Each bit of data output is changed at the clock's positive edge whenever the corresponding data input changes.
- How to parallelism and maintain stability





Parallel Data Loading

❑ Objectives

- Preventing the premature input data from putting into the register


❑ Definition

- All input data bits are loaded to the register in a clock time when the load is needed.

❑ Control methods for parallel loading

- Data input control
 - Violation of parallelism due to the delay on the paths of input data
- Clock control
 - Violation of synchronism due to the delay on the paths of clock signal

Four-bit Register with Parallel Load

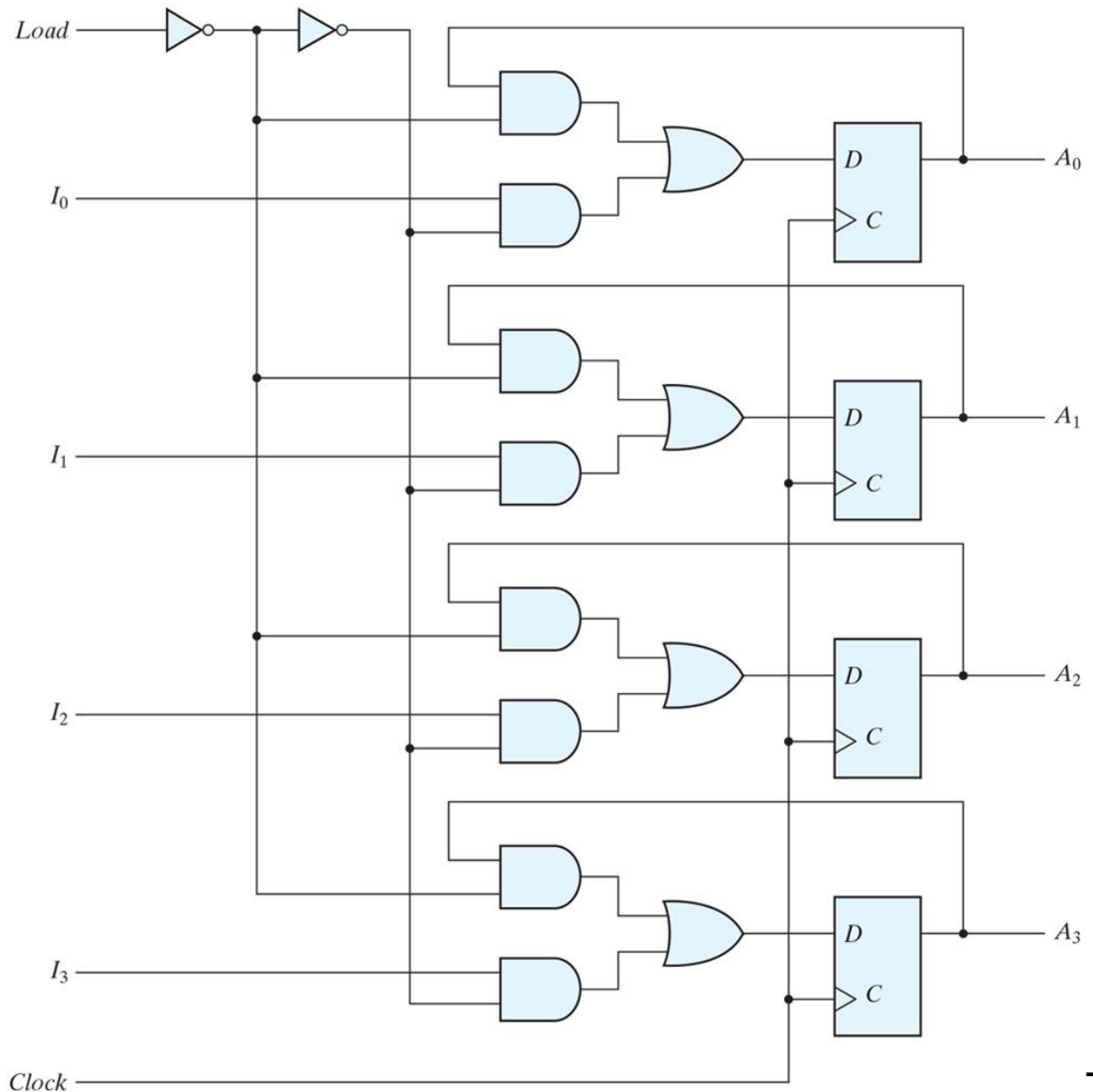



Four-bit Register with Parallel Load

❑ 4-bit register with parallel load

- Load signal

- Input equations


➤ $D_i = L_i' A_i + L_i I_i$

❑ Derivation of input equations


$A_i(t)$	I_i	L_i	$A_i(t+1)$	D
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	1	1

Shift Registers

 
- ❑ A simple 4-bit shift register
 - Serial input and serial output (SISO)



Serial Transfer

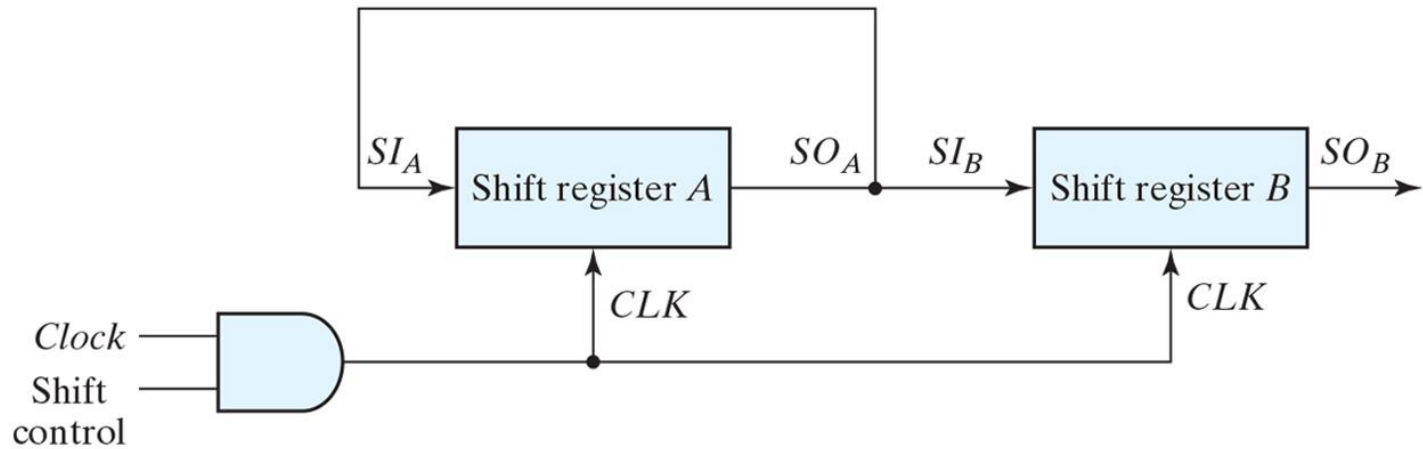

(a) Block diagram

 

(b) Timing diagram




Serial Transfer

- ❑ Serial transfer between registers
 - Source register : shift register A
 - Destination register : shift register B
- ❑ Option: preventing reg-A from losing its content
 - loopback
- ❑ State transition table

Timing Pulse	Shift Register A				Shift Register B			
Initial value	1	0	1	1	0	0	1	0
After T_1	1	1	0	1	1	0	0	1
After T_2	1	1	1	0	1	1	0	0
After T_3	0	1	1	1	0	1	1	0
After T_4	1	0	1	1	1	0	1	1

Serial Addition

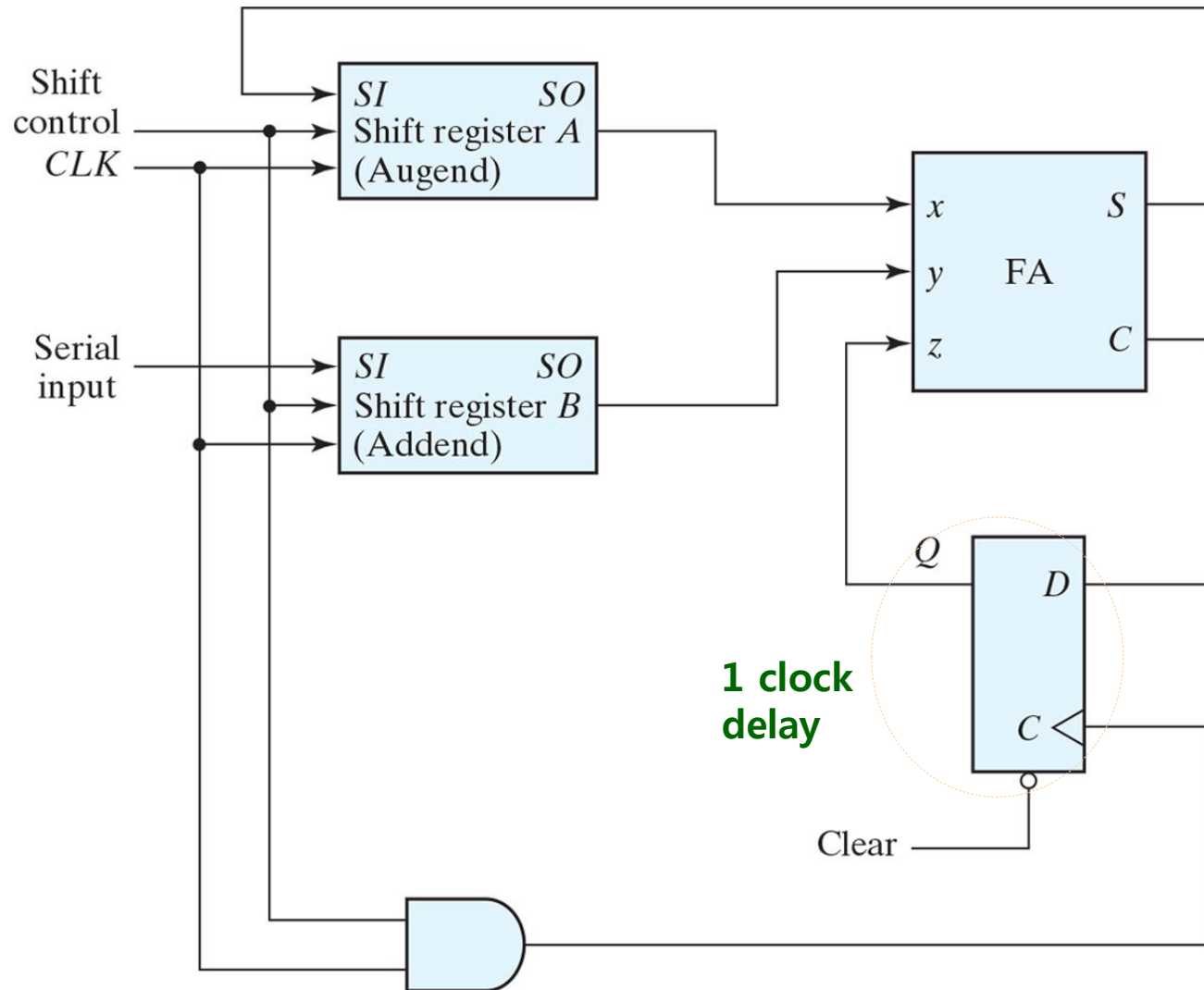



Serial Addition

- 4bit binary number addition
- 1 FA instead 4 FAs but slower
- augend and addend are stored in register A and B, respectively
- result(sum) is stored in register A
- When control=1, bit by bit addition is executed serially.
- The number of clock ticks when control = 1 should exactly equal to the number of bits of data.
- The length of register A and B should be same.



Serial Adder

□ State table


Present State		Inputs		Next State	Output	Flip-Flop Inputs	
Q		x	y	Q	S	J _Q	K _Q
0		0	0	0	0	0	X
0		0	1	0	1	0	X
0		1	0	0	1	0	X
0		1	1	1	0	1	X
1		0	0	0	1	X	1
1		0	1	1	0	X	0
1		1	0	1	0	X	0
1		1	1	1	1	X	0

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

Serial Adder with JK F-F

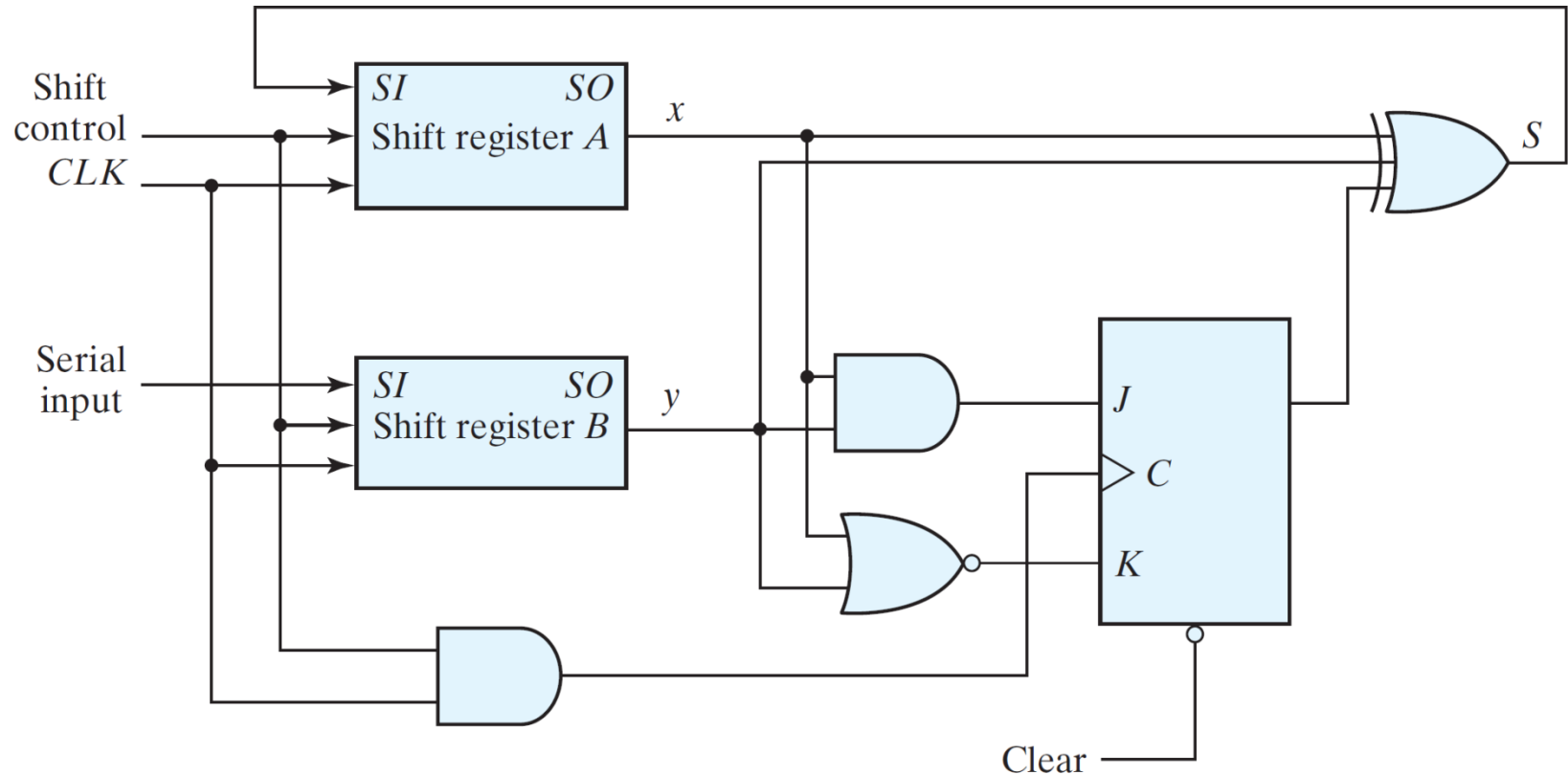


Universal Shift Register


❑ Capabilities (or requirements)

- Extracting intermediate flip-flop outputs
- Parallel load
- Bidirectional(left / right) shift operation
- Preservation of register contents for some clock ticks
- Clear

S_0S_1	control
00	Preserving
01	Shift right
10	Shift left
11	Parallel load

 

Four-bit Universal Shift Register

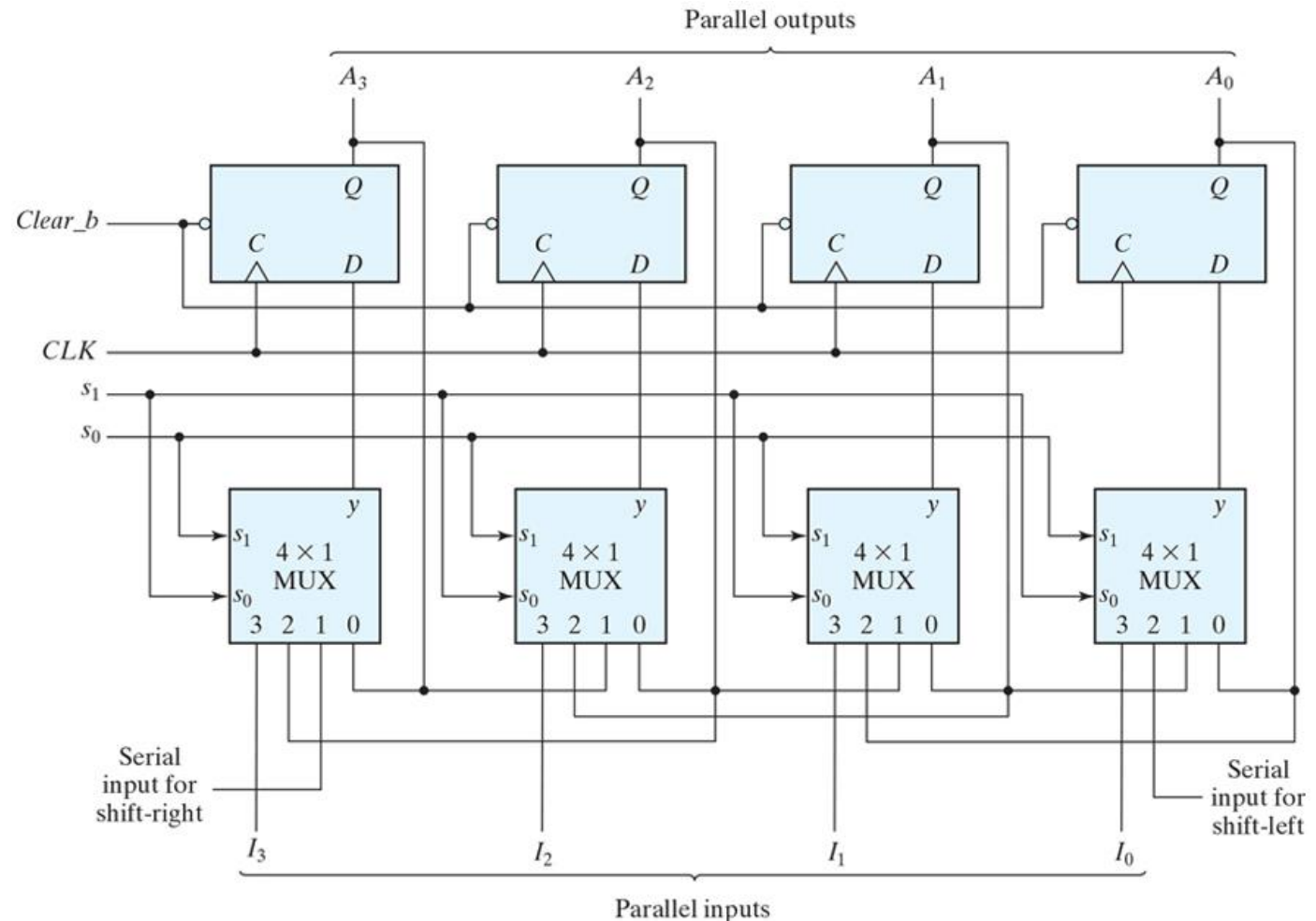

S_0S_1	control
00	Preserving
01	Shift right
10	Shift left
11	Parallel load

Binary Ripple Counter

❑ Binary count-up ripple counter

- A serie of complementing flip-flops
- Negative-edge clock triggering

❑ Binary count-down ripple counter

- A serie of complementing flip-flops
- Positive-edge clock triggering

count-up


A3	A2	A1	A0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1
0	0	0	0

count-down

A3	A2	A1	A0
0	0	0	0
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0


Four-bit Binary Ripple Counter

- Implementation with T F-F and D F-F

 


BCD Ripple Counter

□ State transition diagram

 


BCD Ripple Counter

❑ Block diagram

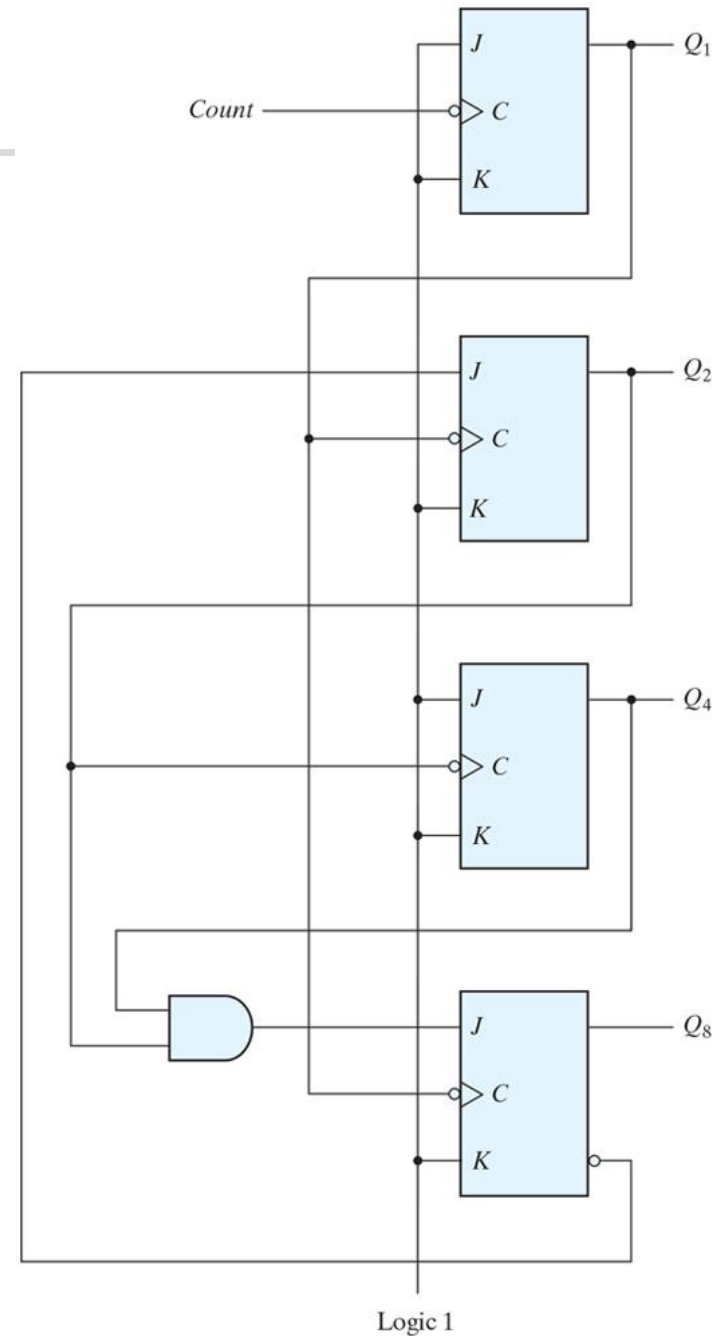

Three-digit BCD Counter

❑ Block diagram

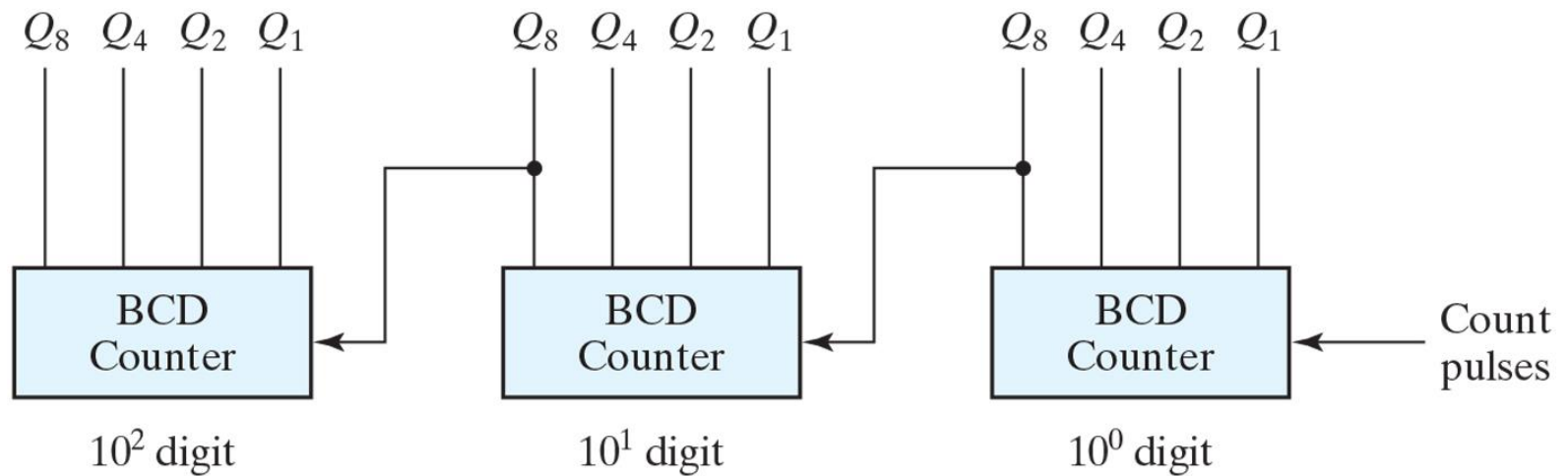



Synchronous Counter

❑ Synchronism

- A common clock triggers all flip-flops simultaneously in synchronous counters
- c.f. : One flip-flop is triggered at a time in succession in a ripple counter

❑ Design of synchronous counters

- Determine the number of bits and number system (binary, BCD, gray, ...)
- State diagram
- State table
- Flip-flop input equations
- Logic diagram of the counter



Synchronous Binary Counter

- ❑ Main idea for the design of sync. binary counter
 - The flip-flop in the least significant position is complemented with every counter pulse.
 - A flip-flop in any other position is complemented when all the bits in the lower significant positions are equal to 1.
- ❑ Implementation with JK flip-flops
 - The first state A_0 has its J and K equal to 1 if the counter is enabled
 - The other J and K inputs are equal to 1 if all previous least significant state are equal to 1 and the count is enabled.



Sync. Count Down Binary Counter

❑ Main idea


- The bit in the least significant position is complemented with each down counter pulse.
- A bit in any other position is complemented if all lower significant bits are equal to 0.

❑ Implementation with JK flip-flops

- Complement output of a flip-flop is provided to J and K inputs of the next flip-flop through AND gate.

Sync. Binary Counter

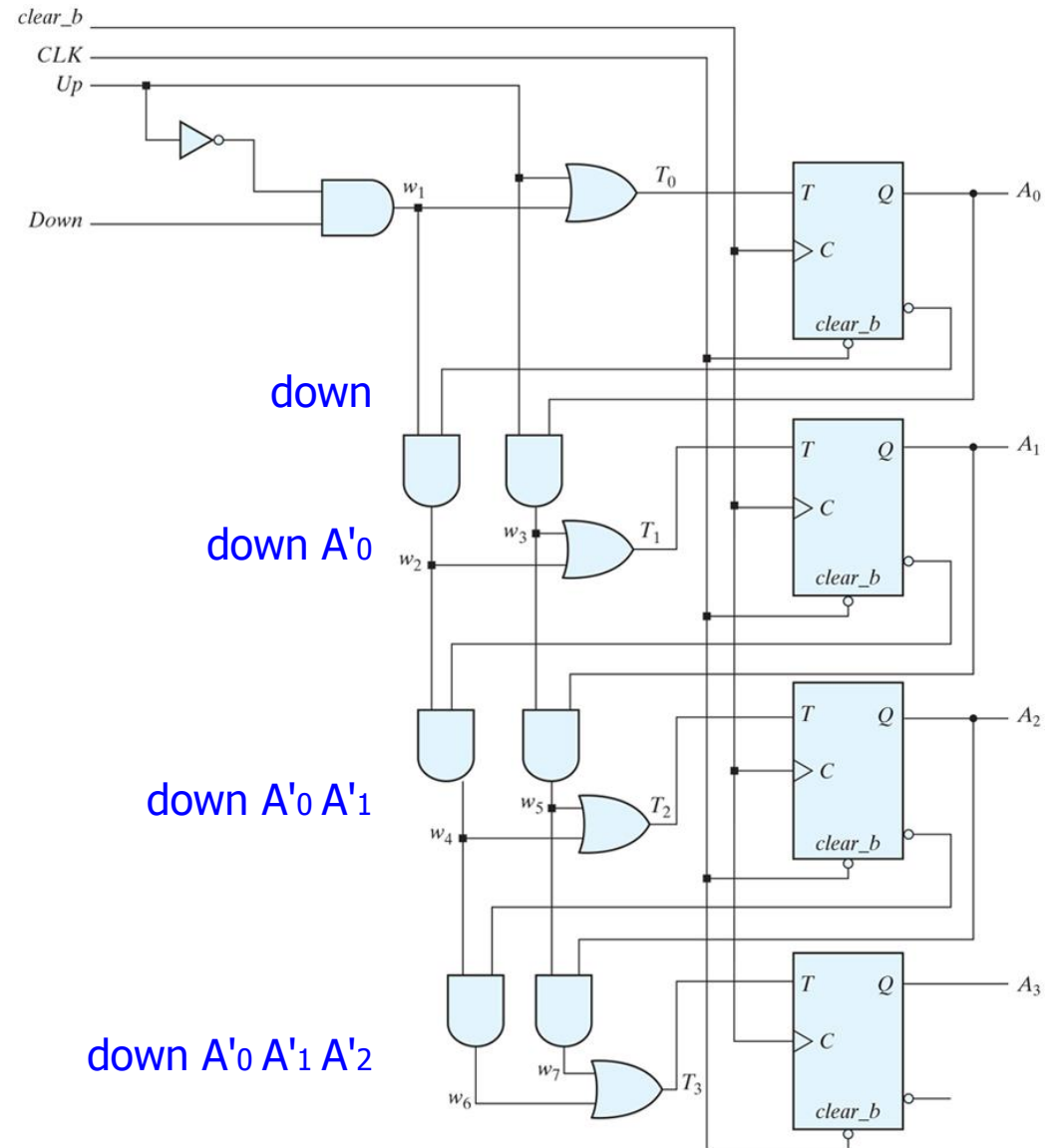- ❑ Four-bit up/down binary counter block diagram



Sync. Binary Counter

□ State table

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	T_{Q8}	T_{Q4}	T_{Q2}	T_{Q1}
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

□ Simplified functions

$$T_{Q1} = 1$$

$$T_{Q2} = Q'_8 Q_1$$


$$T_{Q4} = Q_2 Q_1$$

$$T_{Q8} = Q_8 Q_1 + Q_4 Q_2 Q_1$$

$$y = Q_8 Q_1$$


Sync. Binary Counter with Parallel Load

□ Conceptual diagram

 

Sync. Binary Counter with Parallel Load

Block diagram

 



Sync. Binary Counter with Parallel Load


❑ Function table

Clear_b	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change


- count input is inhibited when the load input is enabled.
- load input priority > count input priority

Alternate Implement of Sync. BCD Cnter

□ Using a counter with parallel load

 

(a) Using the load input

 

(b) Using the clear input



Self-Correcting Counter

❑ Definition

- If the counter happens to be in one of the **unused states**, eventually reaches the ***normal count sequence*** after one or more clock pulses

❑ Unused states

- Don't care condition for simplifying the input equations
- Redundant states for self-correcting




Self-correcting Counter

□ State table

Present State			Next State			Flip-Flop Inputs					
<i>A</i>	<i>B</i>	<i>C</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>J_A</i>	<i>K_A</i>	<i>J_B</i>	<i>K_B</i>	<i>J_C</i>	<i>K_C</i>
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

Self-correcting counter

□ State diagram

 


Self-correcting Counter

□ Block diagram

$$J_A = B \quad K_A = B$$

$$J_B = C \quad K_B = 1$$


$$J_C = B' \quad K_C = 1$$

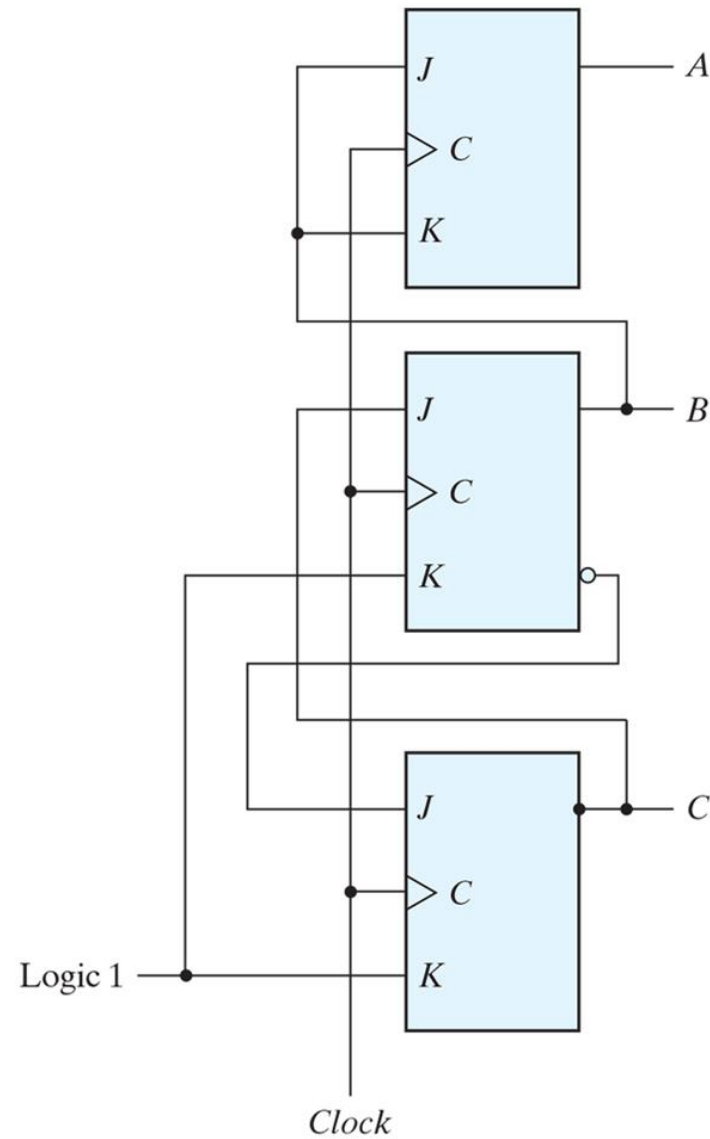

 (a) Logic circuit diagram


Ring Counter

- Objectives : generating multichanneled timing signal




➡ Circulation of a single bit among the flip-flops to provide several distinguishable state

- Alternative implementations

 

 
Regi (a) Ring-counter (initial value = 1000)



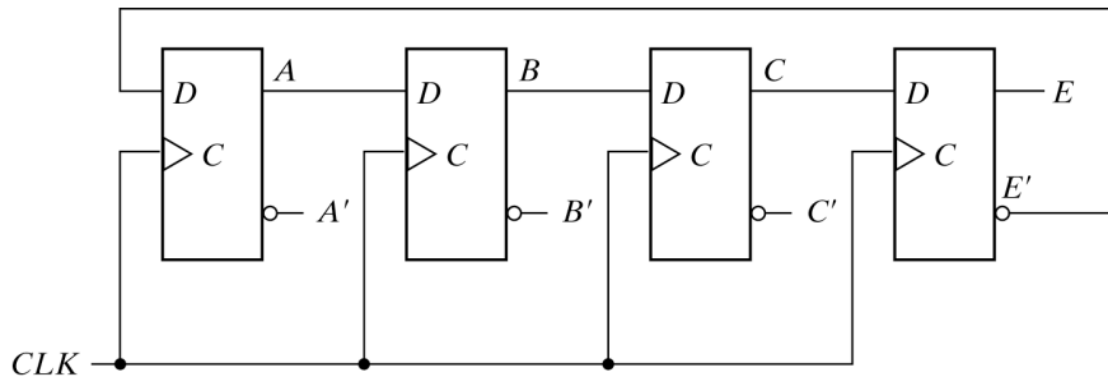(b) Counter and decoder

Johnson Counter

- Objective : Doubling the number of states of ring counter



Core of the 8-states Johnson counter except decoding circuits

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding



Discussion ~ ~ ~