
 


Synchronous Sequential Logic

 


2019. 4. 15.

K-S. Sohn




Contents

 - ☐ Sequential circuits
- ☐ Latches
- ☐ Flip-flops
- ☐ Analysis of clocked sequential circuits
- ☐ State reduction and assignment
- ☐ Design of sequential circuits




Introduction

 - ❑ Combinational circuits
 - neither memory element nor feedback
 - $\langle \text{output} \rangle = F(\langle \text{input} \rangle)$




Sequential circuits

❑ Block diagram of sequential circuit

 

- feedback path
- memory element

 

Sequential Circuits

□ State


- the binary information stored in the memory element at any given time defines the state of the sequential circuit at that time.
- $\langle \text{output} \rangle = F(\langle \text{state} \rangle, \langle \text{input} \rangle; \langle \text{control signal} \rangle)$

□ Synchronounous

- the transition happens at discrete instants of time


□ Asynchronous

 - the transition happens at any instant of time




Sequential Circuits

 - ❑ Asynchronous sequential circuits
 - having only feedback path (or with the "pseudo-memory")
 - $\langle \text{output} \rangle = F(\langle \text{state} \rangle, \langle \text{input} \rangle)$
 - difficult to avoid instability in design




Synchronous Sequential Circuits

 - ❑ Clock generator
 - a master-clock generator to generate a periodic train of clock pulses
 - the clock pulses are distributed throughout the system
- ❑ clocked sequential circuits
 - most commonly used
 - no instability problems
- ❑ clock speed
 - limited by the operational speed of the combinational circuit




Synchronous Sequential Circuits

 - ❑ the memory elements: flip-flops
 - binary cells capable of storing one bit of information
 - two outputs: one for the normal value and one for the complement value
 - maintain a binary state indefinitely until directed by an input signal to switch states



Synchronous Sequential Circuits


❑ Synchronous clocked sequential circuit

 

(a) Block diagram




(b) Timing diagram of clock pulses

 


Latches

 - ❑ asynchronous sequential circuits
 - binary state (0 or 1)
 - $Q(t+1) = F(Q(t), \text{<input>})$
- ❑ Level sensitive circuits
 - the next state is determined by the level of inputs and the current state
 - can not be used for synchronous sequential circuits,
 - but, building blocks of flip-flop



SR Latch

 
- Two NOR gates with cross-coupled connection



(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

(b) Function table

 


SR Latch

- ❑ Most fundamental building block
 - more complicated types can be built upon this SR latch
- ❑ Functional characteristics
 - $(S,R) = (0,0)$: no operation (usual position of the level of inputs)
 - $(S,R) = (0,1)$: reset ($Q=0$, the clear state)
 - $(S,R) = (1,0)$: set ($Q=1$, the set state)
 - $(S,R) = (1,1)$: indeterminate state ($Q=Q'=0$, out of SR rules)



SR Latch

 - ❑ NAND implementation
 - complement of the NOR version
 - S'R' latch



(a) Logic diagram

S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)


(b) Function table



SR Latch

❑ SR latch with control input

 - $En = 0$, no change
- $En = 1$, enable input



(a) Logic diagram

En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table


D Latch

□ Design objectives

- eliminate the undesirable conditions of the indeterminate state in the SR latch by using an inverter and tied inputs

□ 'D' comes from:

 
- $Q = \text{input data}$, transparent latch



(a) Logic diagram



En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

(b) Function table

 


Graphic Symbols

□ SR latches

  

□ D latch

 

Flip-Flops

□ Trigger

- the momentary change of control inputs
- the state of a latch or flip-flop is switched by a change of the control input

□ Level triggered: latch



(a) Response to positive level

□ Edge triggered: F-F



(b) Positive-edge response




(c) Negative-edge response

Flip-Flop

❑ Why F-F as the memory element in the S.S.L.?

○ If a latch used:

 


○ the feedback path may cause instability problem

❑ Edge-triggered F-Fs

○ the state transition happens only at the edge

 
○ eliminate the multiple-transition problem




Edge-triggered D Flip-Flop

❑ Master-slave D flip-flop

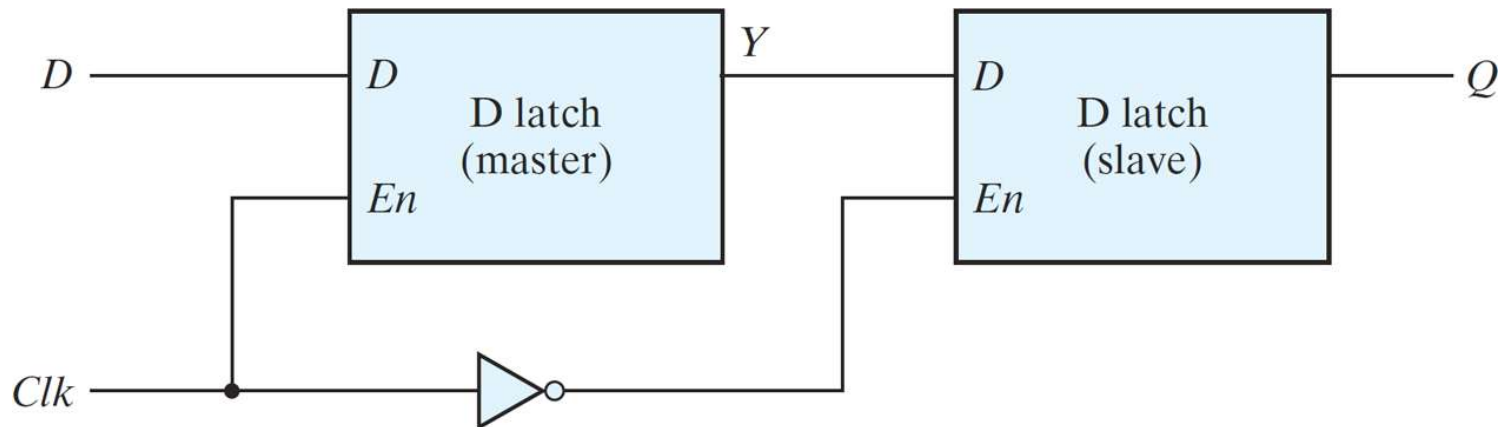- two separate D latches and an inverter
- master latch (triggered during clk's positive level)
- slave latch(triggered during clk's negative level)




 
- triggered at negative or positive edge?
- how to reverse the direction of triggering edge?



Edge-triggered D Flip-Flop

- ❑ D type positive-edge triggered F-F

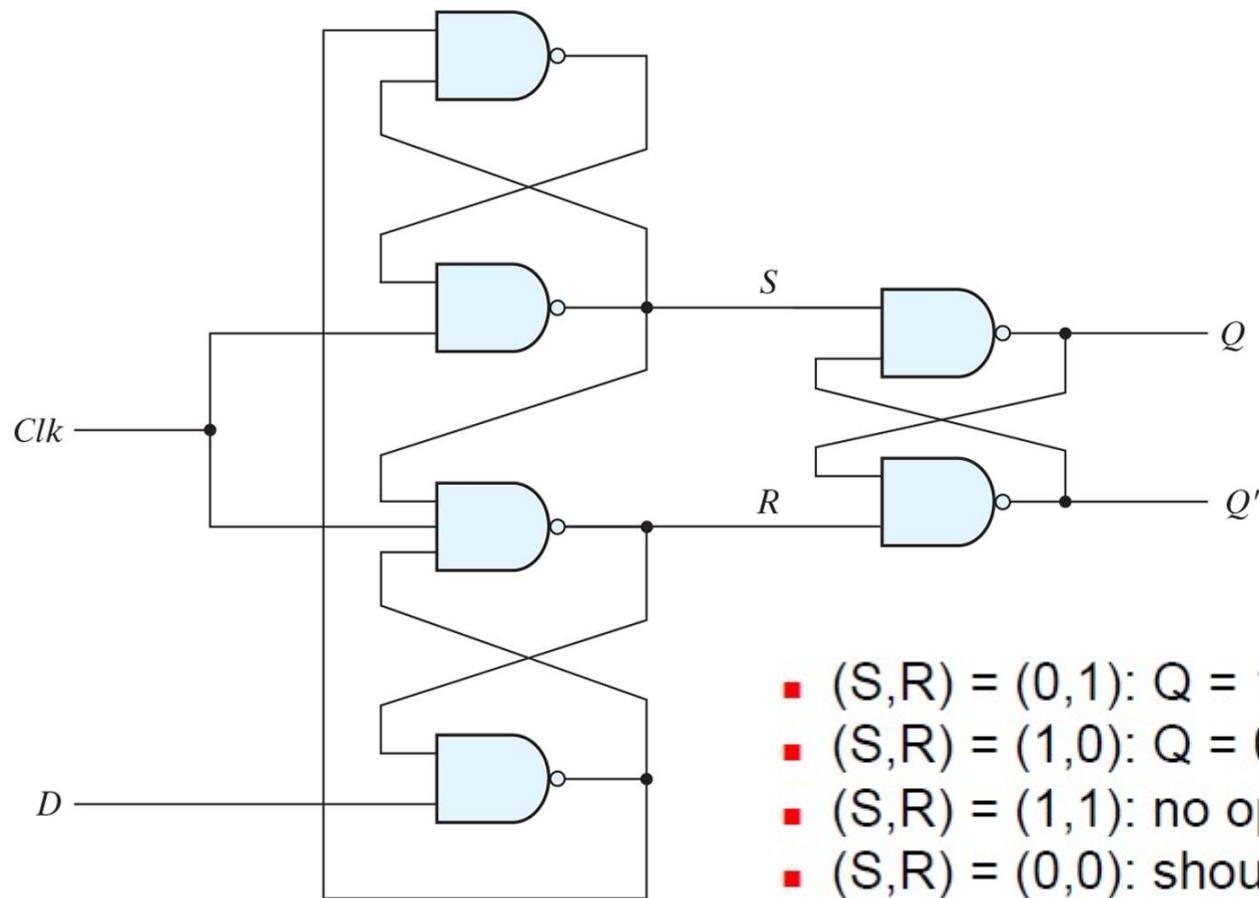


 

Edge-triggered D Flip-Flop


□ In sum.

 - CP=0: (S,R) = (1,1), no state change
- CP=↑: state change once
- CP=1: state holds
- eliminate the feedback problems in sequential circuits




Graphic Symbols of D F-F

 - ❑ The edge-triggered D F-F
 - the most economical and efficient
 - positive-edge and negative-edge



(a) Positive-edge

 

(b) Negative-edge


Specifications of Flip-Flop


❑ Setup time

- A minimum time for which the D input must be maintained at a constant value prior to the occurrence of the clock transition

❑ Hold time

 - A minimum time for which the D input must not change after the application of the positive transition of the clock




 


Specification of Flip-Flop

□ Time contribution analysis

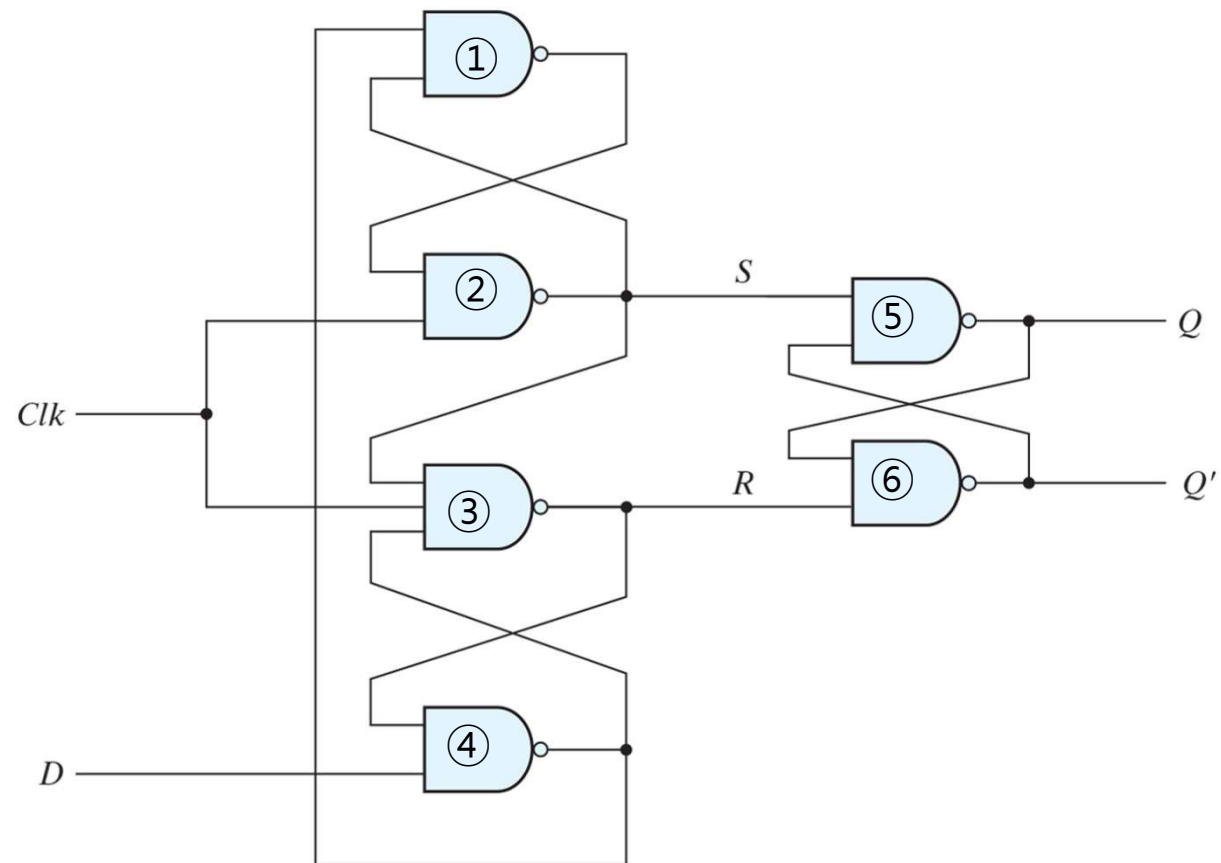- setup time $> td1 + td4$
- hold time $> td3$



 


JK Flip-Flop


□ Operational requirements

- Set: $J=1, K=0, Q(t+1)=1$
- Reset: $J=0, K=1, Q(t+1)=0$
- Complement: $J=1, K=1, Q(t+1)=Q'(t)$
- No change: $J = K = 0, Q(t+1)=Q(t)$

□ Constraints

 - Use D F-F and some logic gates including inverters



 


JK Flip-Flop

□ Front logic


○ $D = JQ' + K'Q$

○ How?


□ Logic diagram and graphical symbol

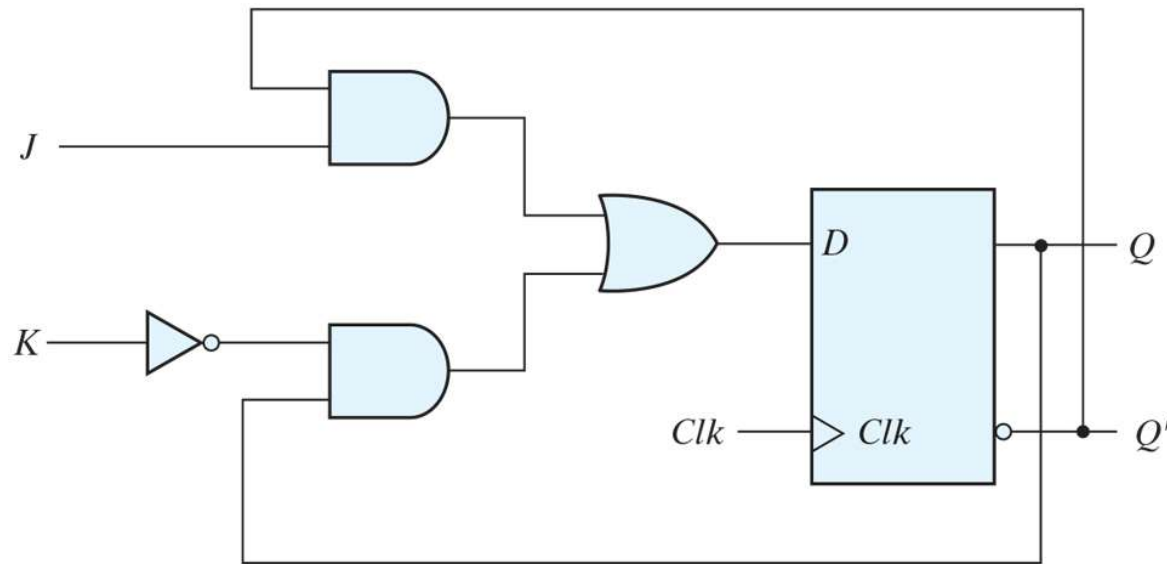

(a) Circuit diagram

 

(b) Graphic symbol

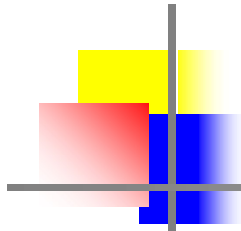


T Flip-Flop


□ Functional requirements

- toggle output with a T input
- $T=0, Q(t+1)=Q(t)$
- $T=1, Q(t+1)=Q'(t)$

□ Constraints

- Use D F-F and some logic gates

 

 


T Flip-Flop

□ Front logic


- $D = TQ' + T'Q$

- Why?


□ Logic diagram and graphic symbol

 


(a) From JK flip-flop

 

(b) From D flip-flop

 

(c) Graphic symbol

 

Characteristics Tables

□ t

- a period of the clock pulse
- $(t+1)$ means the next clock pulse period

□ $Q(t)$

- present state


□ $Q(t+1)$

- next state

<i>JK</i> Flip-Flop			
<i>J</i>	<i>K</i>	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

<i>D</i> Flip-Flop		
<i>D</i>	$Q(t + 1)$	
0	0	Reset
1	1	Set

<i>T</i> Flip-Flop		
<i>T</i>	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

 

Characteristic Equations

- D flip-flop

- $Q(t+1)=D$

- JK flip-flop


- $Q(t+1)=JQ'+K'Q$

- T flip-flop


- $Q(t+1)=TQ'+T'Q$

Direct Inputs

❑ Asynchronous set and/or reset

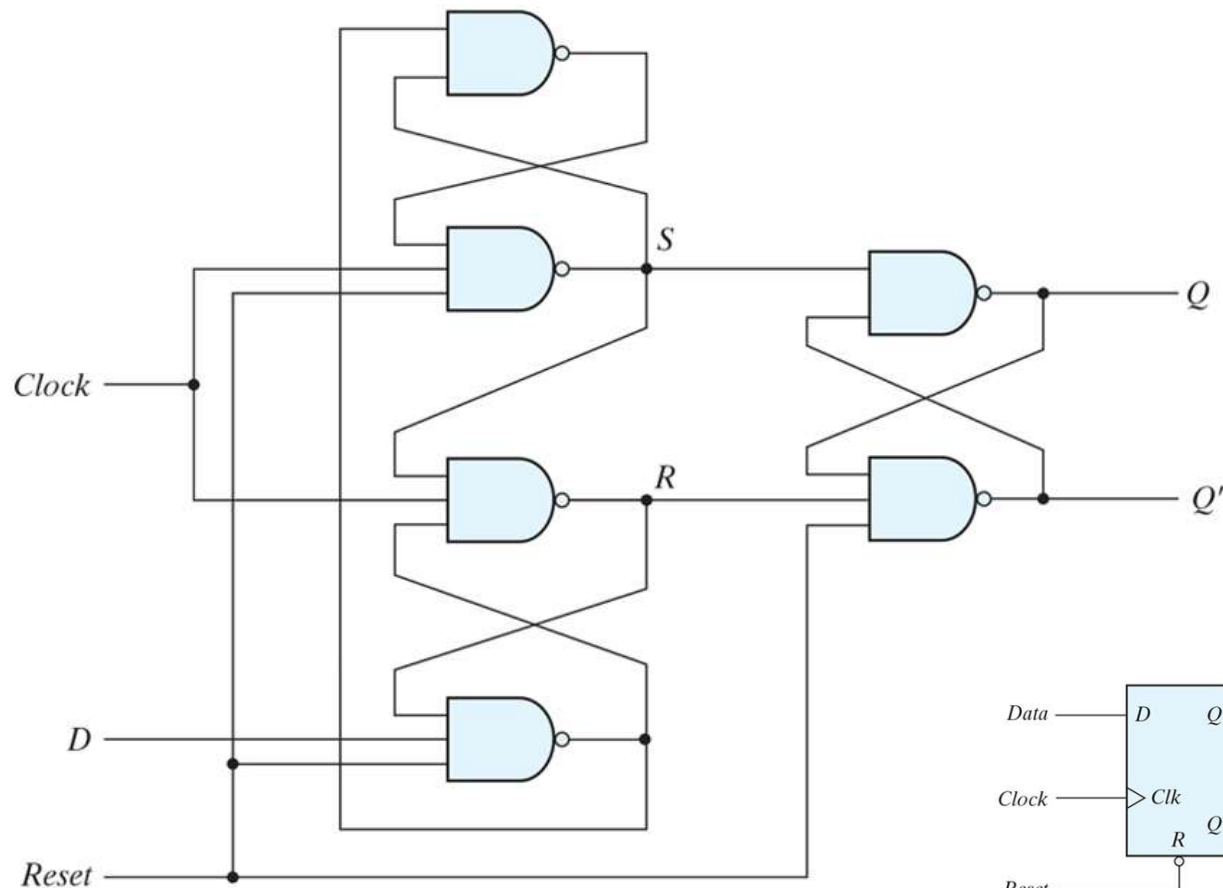


(a) Circuit diagram

 

(b) Graphic symbol

R	Clk	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

(c) Function table

 

Discussion ~ ~ ~