




ECE201-Digital Design

(Ch.08 Register Transfer Level)

3 June 2019


by

Kyu-Seek Sohn

 

Contents

 - ▣ Digital system = control logic + datapath
- ▣ Register Transfer Level
- ▣ Algorithmic State Machine
- ▣ Design Example : Binary Multiplier
- ▣ Home Work



A Digital System

□ Control logic + datapath model



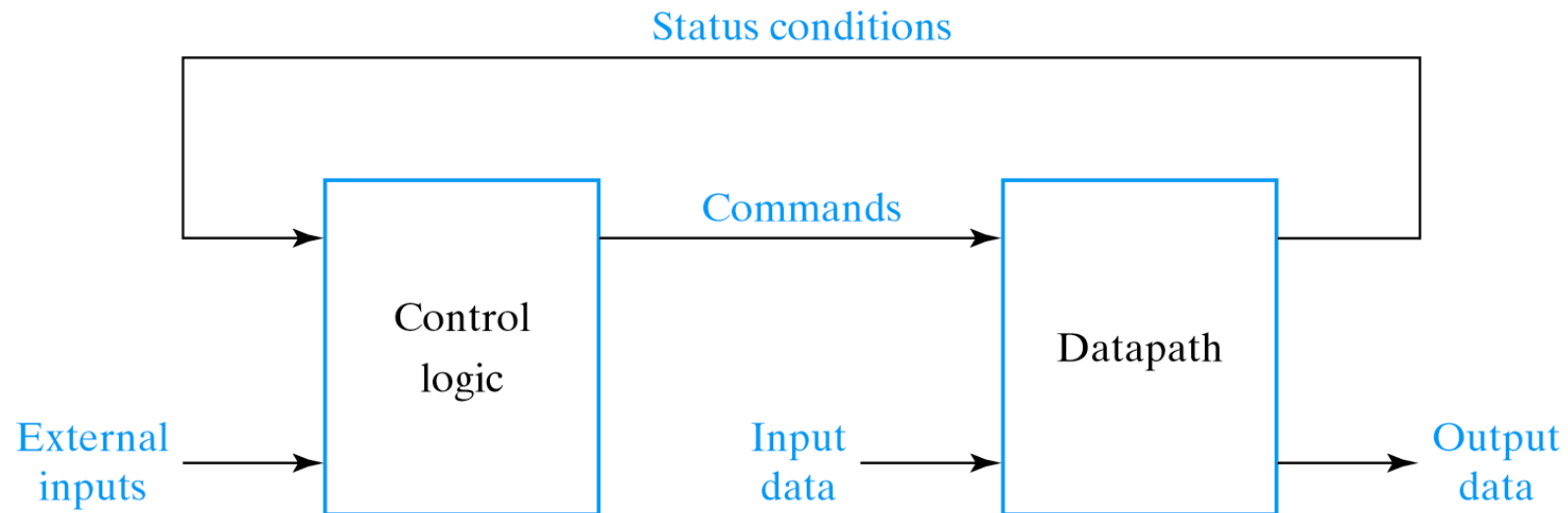


Fig. 8-2 Control and Datapath Interaction

 


Control Logic

 - Sequencing the operations in the datapath
 - ◆ Command : signals generated by the control logic
- A sequential circuit
 - ◆ Internal state dictate the control command for the system
- Inputs
 - ◆ External inputs
 - ◆ Status conditions from the datapath
- Outputs
 - ◆ Commands to the datapath




Datapath

 - Data processing path
 - ◆ Series of registers along which data is manipulated
- Operations manipulating data
 - ◆ Transfer operations
 - ◆ Arithmetic operations
 - ◆ Logic operations (bit-wise)
 - ◆ Shift operations
- Outputs
 - ◆ Output data
- Inputs
 - ◆ Input data



Register Transfer Level(RTL)

 - Register is :
 - ◆ Basic unit of data processing in the datapath
 - ◆ Basic component of datapath
- Operations executed on registers
 - ◆ Transfer operations
 - ◆ Arithmetic operations
 - ◆ Logical operations
 - ◆ Shift operations
 - ◆ Relational operations



Algorithmic State Machines(ASM)

■ Definition

- ◆ A special flowchart that defines digital hardware algorithms

■ Use of ASM

- ◆ To specify accurately the control sequence and datapath operations in a digital system

■ Meaning of ASM

- ◆ Timing relationship between the state of the states of a sequential control logic
- ◆ Event causing the state transition

Components of ASM

State box

 


Fig. 8-3 State Box

Decision box

 


Fig. 8-4 Decision Box

Conditional box

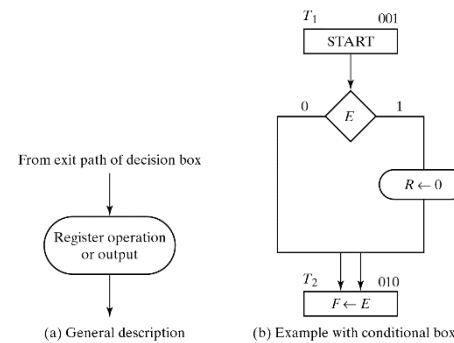


Fig. 8-5 Conditional Box



State Box

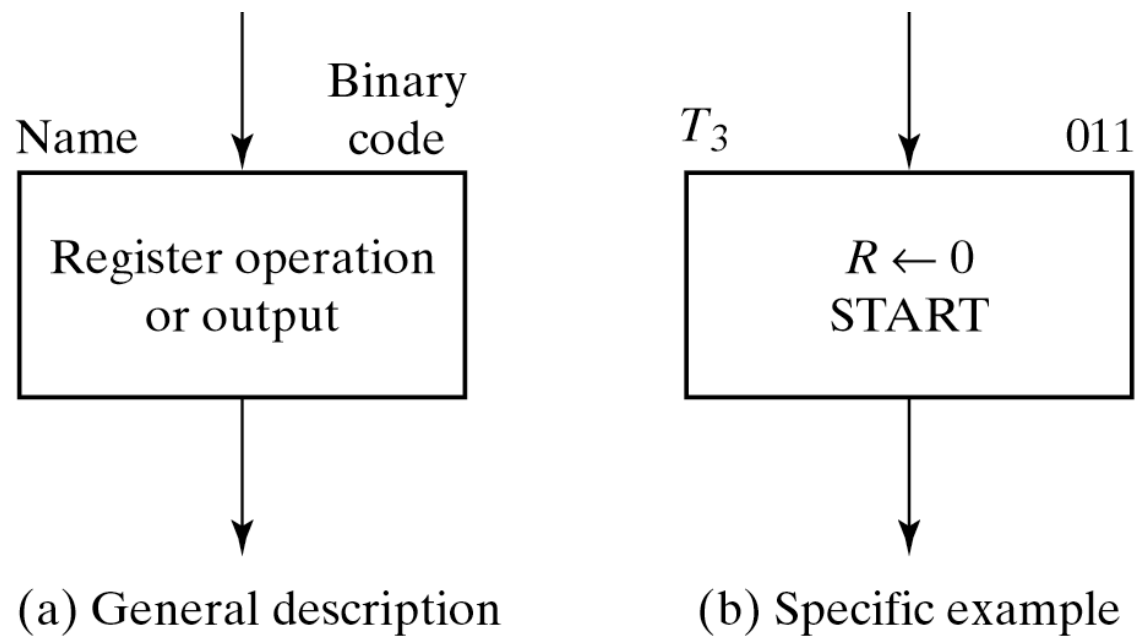


Fig. 8-3 State Box



Decision Box


 



Fig. 8-4 Decision Box

Conditional Box

From exit path of decision box

 

(a) General description

 

(b) Example with conditional box

Fig. 8-5 Conditional Box
Ch.08 Register Transfer Level



ASM Block

The operational unit
executing datapath
function in one time
clock


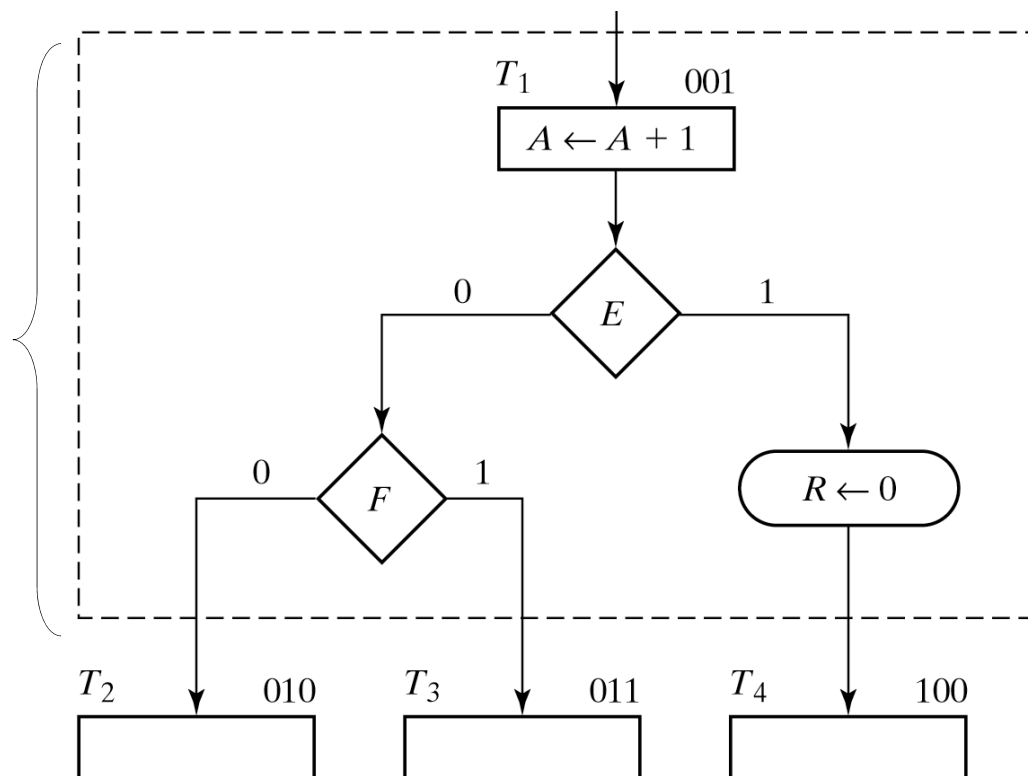


Fig. 8-6 ASM Block

 

Register Configuration

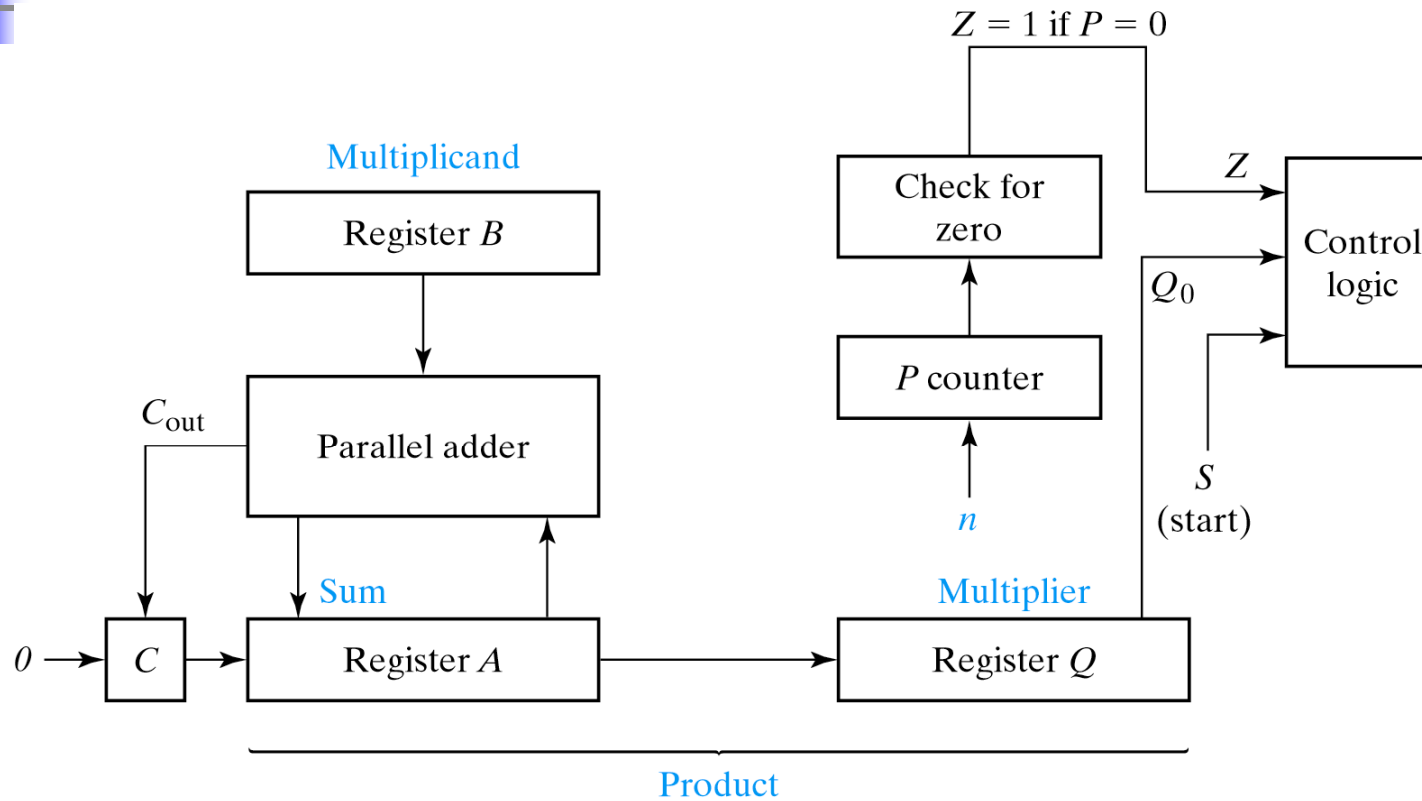


Fig. 8-13 Block Diagram of Binary Multiplier

ASM Chart of The Binary Multiplier

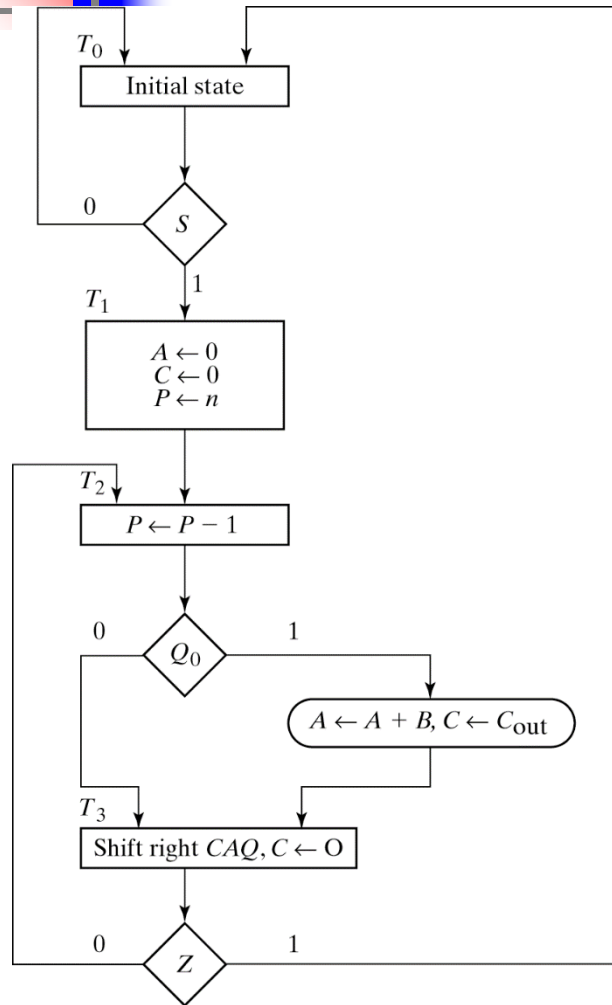


Fig. 8-14 ASM Chart for Binary Multiplier

h.08


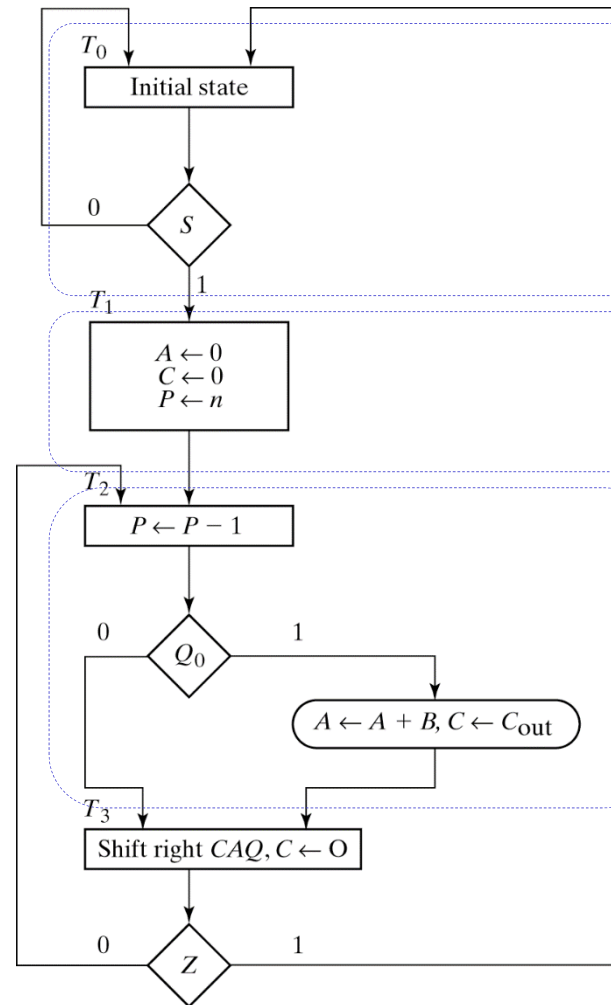


Fig. 8-14 ASM Chart for Binary Multiplier

ASM block

Control Logic State Diagram

 

T_0 : Initial state

T_1 : $A \leftarrow 0, C \leftarrow 0, P \leftarrow n$

T_2 : $P \leftarrow P - 1$

if $(Q_0) = 1$ then $(A \leftarrow A + B, C \leftarrow C_{out})$

T_3 : shift right $CAQ, C \leftarrow 0$

(b) Register transfer operations

Fig. 8-15 Control Specifications for Binary Multiplier



Control Block Diagram

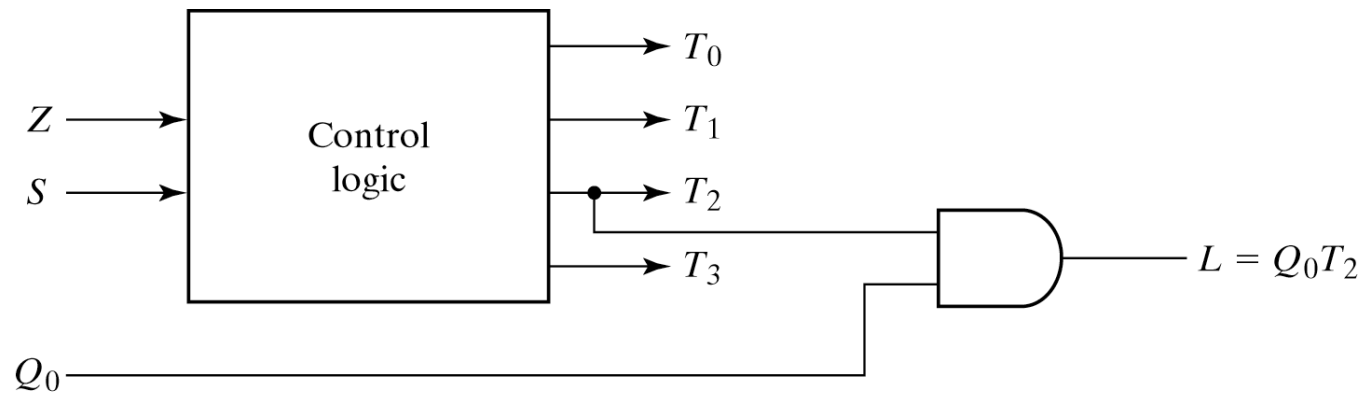


Fig. 8-16 Control Block Diagram

Sequence Register and Decoder

State table for control circuits

Table 8-3
State Table for Control of Fig. 8-10

Present-State Symbol	Present State		Inputs			Next State		Outputs		
	G_1	G_0	S	A_3	A_4	G_1	G_0	T_0	T_1	T_2
T_0	0	0	0	X	X	0	0	1	0	0
T_0	0	0	1	X	X	0	1	1	0	0
T_1	0	1	X	0	X	0	1	0	1	0
T_1	0	1	X	1	0	0	1	0	1	0
T_1	0	1	X	1	1	1	1	0	1	0
T_2	1	1	X	X	X	0	0	0	0	1

$$D_{G1} = T_1 + T_2 + T_{3Z}' \quad D_{G0} = T_0 S + T_2$$

Control Logic Diagram

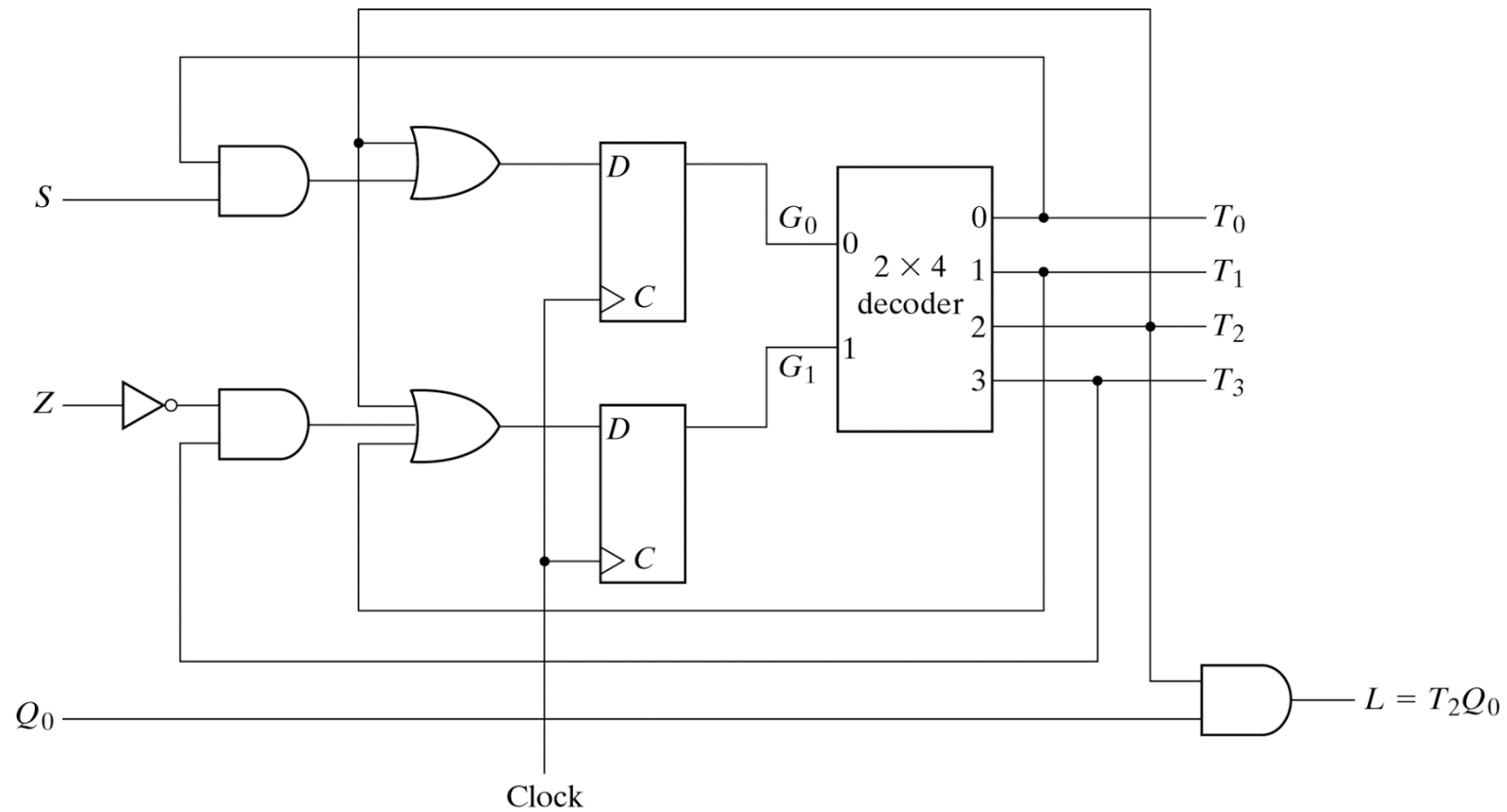


Fig. 8-17 Logic Diagram of Control for Binary Multiplier Using a Sequence Register and Decoder

One Flip-Flop per State

- State diagram \Rightarrow F-F input equations

