



# Gate Level Minimization

---

2019. 3. 18.

K-S. Sohn



# Contents

---

- ❑ The map method
- ❑ Four-variable map
- ❑ Product-of-sums simplification
- ❑ Don't care conditions
- ❑ NAND-NOR Implementation
- ❑ Other two-level implementation
- ❑ XOR function



# Introduction

---

## ❑ Gate-level minimization

- Gate-level minimization is the design task of finding an optimal gate-level implementation of Boolean functions describing a digital circuit.

## ❑ Importance

- CAD can minimize Boolean equations efficiently and quickly.
- Nevertheless, designer should understand the underlying mathematical description and solution of the problem



# The Map Method

---

- ❑ The complexity of the digital logic gates
  - the complexity of the algebraic expression
- ❑ Logic minimization
  - algebraic approaches: lack specific rules
  - the Karnaugh map (or K-map)
    - a simple straight forward procedure
    - a pictorial form of a truth table
    - applicable if the # of variables  $< 7$
- ❑ A diagram made up of squares
  - each square represents one minterm



# Boolean Function


---

- ❑ Standard form of a Boolean function
  - sum of product
  - product of sum
- ❑ Simplest algebraic expression
  - a minimum number of terms
  - a minimum number of literals in each term
  - The simplified expression may not be unique
- ❑ K-map (Karnaugh map)
  - a diagram made up of squares with each square representing one minterm of the Boolean function to be minimized



 
# Two-Variable K-Map

- ❑ A two-variable Boolean function
  - four minterms
- ❑ A two-variable map
  - four squares, one for each minterm
  - $x' = \text{row } 0$ ;  $x = \text{row } 1$
  - $y' = \text{column } 0$ ;  $y = \text{column } 1$



(a)

 

(b)


# Two-Variable K-Map

## □ Representation of functions in the K-map


○ map a row of a truth table into square located by (x,y) in the diagram

○  $xy$

○  $x+y$

 

(a)  $xy$

 

(b)  $x + y$

# Three-Variable Map

## ❑ Three-variable Boolean function

- eight minterms

## ❑ Three-variable K-map

- minterms arranged in a Gray code sequence
- any two adjacent squares in the map differ by only one variable
  - primed in one square and unprimed in the adjacent one

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

		$y$			
		$yz$			
		00	01	11	10
$x$	0	$m_0$ $x'y'z'$	$m_1$ $x'y'z$	$m_3$ $x'yz$	$m_2$ $x'yz'$
	1	$m_4$ $xy'z'$	$m_5$ $xy'z$	$m_7$ $xyz$	$m_6$ $xyz'$
		$z$			






# Three-Variable K-Map

## □ Adjacency of squares

- in row, in column, and rotation is permitted in each dimension
 
## □ Example


- An adjacent pair  $m_5$  and  $m_7$  can be simplified
- $m_5 + m_7 = xy'z + xyz = xz (y' + y) = xz$



# Three-Variable K-Map
 
## □ Example 3.1


○  $F(x,y,z) = \sum(2,3,4,5) \rightarrow F = x'y + xy'$



# Simplifying with Two Adjacent Squares
 
## □ Example of adjacency


- $m_0$  and  $m_2$  ( $m_4$  and  $m_6$ ) are adjacent
- $m_0 + m_2 = x'y'z' + x'yz' = x'z' (y' + y) = x'z'$
- $m_4 + m_6 = xy'z' + xyz' = xz' (y' + y) = xz'$



# Simplifying with Two Adjacent Squares

## Example 3.2

$F(x,y,z) = \sum(3,4,6,7) = yz + xz'$

 

Note:  $xy'z' + xyz' = xz'$




# Four Adjacent Squares
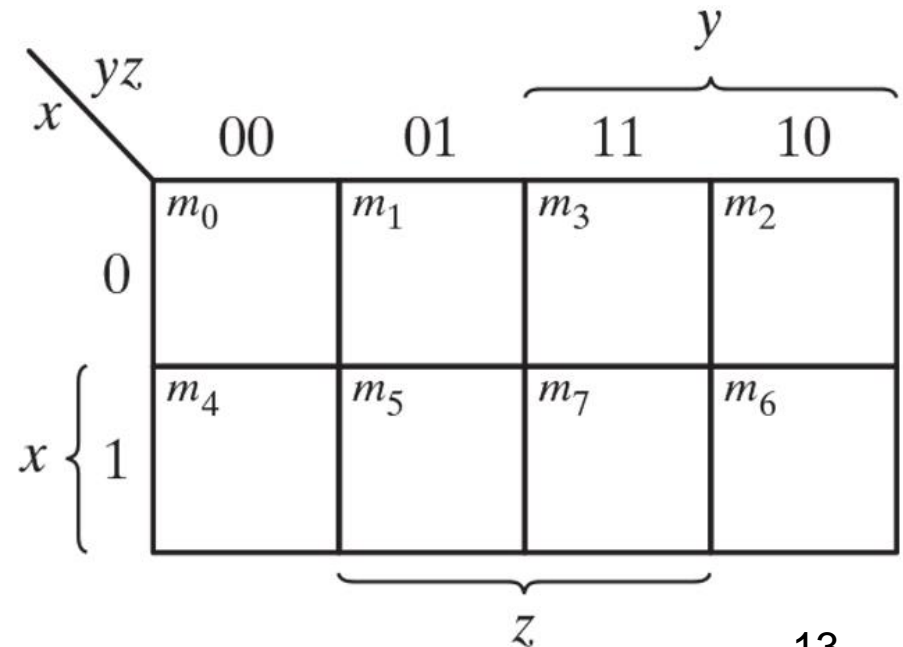
## □ Simplification in Boolean function

$$\begin{aligned} \bigcirc F &= m_0 + m_2 + m_4 + m_6 = x'y'z' + x'yz' + xy'z' + xyz' \\ &= x'z'(y' + y) + xz'(y' + y) \\ &= x'z' + xz' = z' \end{aligned}$$

$$\begin{aligned} \bigcirc F &= m_1 + m_3 + m_5 + m_7 = x'y'z + x'yz + xy'z + xyz \\ &= x'z(y' + y) + xz(y' + y) \\ &= x'z + xz = z \end{aligned}$$




$x \backslash yz$	$y$			
	00	01	11	10
0	$m_0$	$m_1$	$m_3$	$m_2$
1	$m_4$	$m_5$	$m_7$	$m_6$

# Simplifying on Four Adjacent Squares
 
## Example 3.3

$F(x,y,z) = \sum (0,2,4,5,6) \rightarrow F = z' + xy'$




Note:  $y'z' + yz' = z'$

# Simplifying on Four Adjacent Squares
 
## □ Example 3.4

- $F = A'C + A'B + AB'C + BC$
- express it in sum of minterms
- find the minimal sum of products expression



# Four-Variable K-Map

❑ Four-variable K-map diagram

○ 16 minterms

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$


		$y$			
		$yz$	00	01	11 10
$w$	00	$m_0$ $w'x'y'z'$	$m_1$ $w'x'y'z$	$m_3$ $w'x'yz$	$m_2$ $w'x'yz'$
	01	$m_4$ $w'xy'z'$	$m_5$ $w'xy'z$	$m_7$ $w'xyz$	$m_6$ $w'xyz'$
	11	$m_{12}$ $wxy'z'$	$m_{13}$ $wxy'z$	$m_{15}$ $wxyz$	$m_{14}$ $wxyz'$
	10	$m_8$ $wx'y'z'$	$m_9$ $wx'y'z$	$m_{11}$ $wx'yz$	$m_{10}$ $wx'yz'$



# Use 16, 8, 4, and 2 Adjacent Squares A. P.
 
## □ Example 3.5

○  $F(w,x,y,z) = \sum (0,1,2,4,5,6,8,9,12,13,14) \rightarrow F = y' + w'z' + xz'$




Note:  $w'y'z' + w'yz' = w'z'$   
 $xy'z' + xyz' = xz'$

# Use 16, 8, 4, and 2 Adjacent Squares A. P.
 
## Example 3.6

$$F = A'B'C' + B'CD' + A'BCD' + AB' \rightarrow B'D' + B'C' + A'CD'$$



Notes:

$$A'B'C'D' + A'B'CD' = A'B'D'$$

$$AB'C'D' + AB'CD' = AB'D'$$

$$A'B'C' + AB'C' = B'C'$$



# Simplification Procedure

---

## ❑ Simplification criteria

- all the minterms of the function are covered by terms
- the number of terms in the expression is minimized
- there are no redundant terms(i.e., minterms already covered by other terms)

## ❑ Systematic choice of adjacent squares

- Find **essential prime implicants** first, and then find **prime implicants** those which cover the given Boolean function.



# Prime Implicants

---

## □ Implicant

- a product term which, when true(i.e., 1), always implies that the given Boolean function is true(i.e., 1).
- $F(w,x,y,z) = wx + xy + z \rightarrow$  implicants of  $F$ :  $wx, xy, z, wxy, zx, \dots$
- then how about  $w, x, y$ , or  $wy$ ?

## □ Prime implicant

- a P.I. is a product term obtained from the map by combining all possible maximum numbers of squares
- a single 1's represents a P.I. if it is not adjacent to any other 1's.
- Two adjacent 1's form a P.I if they are not within a group of four adjacent 1's. Four adjacent 1's form a P.I if they are not within a group of eight adjacent 1's, and so on.



# Prime Implicants

---

## ❑ Essential prime implicant

- prime implicants that cover an output of the function that no combination of other prime implicants is able to cover
- one or more minterms in a square are covered by only that one prime implicant
- the essential P.I. must be included in the minimized expression



# Prime Implicants

□ Example: considering essential P.I. and P.I.

○  $F(A, B, C, D) = \sum (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$


AB \ CD	CD			
	00	01	11	10
00	1		1	1
01		1	1	
11		1	1	
10	1	1	1	1

# Prime Implicants

□ Example: considering essential P.I. and P.I.

○  $F(A, B, C, D) = \sum (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

○ essential P.I. :  $BD; B'D'$

 

Note:

$$A'B'C'D' + A'B'CD' = A'B'D'$$

$$AB'C'D' + AB'CD' = AB'D'$$

$$A'B'D' + AB'D' = B'D'$$


# Prime Implicants

□ Example: considering essential P.I. and P.I.

○  $F(A, B, C, D) = \sum (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

○ P.I. :  $CD, B'C, AD, \text{ and } AB'$

 ○  $F = BD + B'D' + CD + AD$   
 $= BD + B'D' + CD + AB?$   
 $= BD + B'D' + B'C + AD$   
 $= BD + B'D' + B'C + AB'$





# Five-Variable K-Map

- ❑ Divide and re-combine the map
  - map for more than four variable becomes complicated
  - five-variable map  $\Rightarrow$  divide  $\Rightarrow$  two four-variable map

$A = 0$

		$DE$		$D$	
		00	01	11	10
$BC$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$E$

$C$

$A = 1$

		$DE$		$D$	
		00	01	11	10
$BC$	00	16	17	19	18
	01	20	21	23	22
	11	28	29	31	30
	10	24	25	27	26



$E$

$C$

# Five-Variable K-Map

  
## Example

$$F = \sum (0,2,4,6,9,13,21,23,25,29,31) = A'B'E' + BD'E + ACE$$



# Five-Variable K-Map

## Example

 



# Product of Sums Simplification

---

## ❑ Backgrounds

- The minimized Boolean function expressed in the product-of-sums can be derived from the map.
- The minterms not included in the standard sum-of-product form of  $F$  denote  $F'$ .


## ❑ Procedure

- mark squares by 1's for  $F$  on the K-map.
- mark the remaining squares by 0's for  $F'$
- obtain minimized  $F'$  with combining adjacent 0's-squares in sum-of-product form
- obtain  $F$  in product-of-sum from  $F'$  by using such as DeMorgan theorem

# Product of Sums Simplification
 
## □ Example 3.7


$$\begin{aligned} \circ F(A, B, C, D) &= \sum(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D \\ &= (A' + B')(C' + D')(B' + D). \end{aligned}$$




# Product of Sums Simplification
 
## □ Example 3.7

○ Gate implementation of the function  $F$



(a)  $F = B'D' + B'C' + A'C'D$

 


(b)  $F = (A' + B')(C' + D')(B' + D)$

# Product of Sums Simplification

□ Given  $F$  as product-maxterms (canonical form)

○ an example

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

○  $F = \sum(1,3,4,6)$

○  $F' = \sum(0,2,5,7)$

○  $F = \prod(0,2,5,7)$

$$F = x'z + xz'$$

$$F' = xz + x'z'$$

$$F = (x' + z')(x + z)$$



# Don't-Care Conditions

---

## ❑ Don't care condition

- If we can don't care what value is assumed by the function for an unspecified minterms, we call them as "don't-care conditions."

## ❑ Don't-care minterm

- a don't-care minterm is a combination of variables whose logical value is not specified.
- the square of the don't-care minterm is marked as 'X' in the K-map.



# Don't-Care Conditions

## □ Example 3.8

○  $F(w,x,y,z) = \sum(1,3,7,11,15)$

○  $d(w,x,y,z) = \sum(0,2,5)$

		$y$			
	$yz$	00	01	11	10
$wx$	00	$m_0$ X	$m_1$ 1	$m_3$ 1	$m_2$ X
	01	$m_4$ 0	$m_5$ X	$m_7$ 1	$m_6$ 0
	11	$m_{12}$ 0	$m_{13}$ 0	$m_{15}$ 1	$m_{14}$ 0
	10	$m_8$ 0	$m_9$ 0	$m_{11}$ 1	$m_{10}$ 0

(a)  $F = yz + w'x'$

		$y$			
	$yz$	00	01	11	10
$wx$	00	$m_0$ X	$m_1$ 1	$m_3$ 1	$m_2$ X
	01	$m_4$ 0	$m_5$ X	$m_7$ 1	$m_6$ 0
	11	$m_{12}$ 0	$m_{13}$ 0	$m_{15}$ 1	$m_{14}$ 0
	10	$m_8$ 0	$m_9$ 0	$m_{11}$ 1	$m_{10}$ 0

(b)  $F = yz + w'z$



# Don't-Care Conditions


## □ Example 3.8

wxyz	$w'x' + yz$	$w'z + yz$
-----		
0000	1	0
0001	1	1
0010	1	0
0011	1	1
0100	0	0
0101	0	1
0110	0	0
0111	1	1
1000	0	0
1001	0	0
1010	0	0
1011	1	1
1100	0	0
1101	0	0
1110	0	0
1111	1	1
-----		

# NAND nad NOR Implementation
 
## □ NAND


- A universal gate  $\Rightarrow$  any logic circuit can be implemented




# Graphic Symbols for a NAND Gate

- Two graphic symbols for a three input NAND gate

- AND-invert

 

- invert-OR

 


# NAND-NAND Two-level Implementation

## ❑ Original function

○ sum of products

## ❑ Example: $F = AB + CD$


○ AND-OR

 


$$F = ((AB)'(CD)')' = AB + CD$$

○ NAND-invert-OR

$\Rightarrow$

 

NAND-NAND

 



# NAND-NAND Implementation

---


## □ Example 3.9

- Implement  $F$  with NAND gates
- $F(x,y,z) = (1,2,3,4,5,7)$

 
## □ Procedure

- simplified in the form of sum of products
- a NAND gate for each product term; the inputs to each NAND gate are the literals of the term
- a single NAND gate for the second sum term
- a single literal requires an inverter in the first level


❑ Simplification:  $F(x,y,z) = \sum(1,2,3,4,5,7) = xy' + x'y + z$



(a)

 

(b)

 

(c)


# Multilevel NAND Circuits

## □ Common procedure

- Implement circuit in terms of AND, OR, and NOT gates
- convert into an all-NAND circuit
 
## □ $F = A(CD + B) + BC'$

- omit simplification for illustration
- AND-OR gates






# Multilevel NAND Circuits

□  $F = A(CD + B) + BC'$

○ NAND gates

 


## □ Procedure of AND-OR to all-NAND

1. Convert all AND gates to NAND gates with AND-invert graphic symbols.
2. Convert all OR gates to NAND gates with invert-OR graphic symbols.
3. Check all the bubbles in the diagram. For every bubble that is not compensated by another small circle along the same line, insert an inverter (a one-input NAND gate) or complement the input literal.


# An Example for The Conversion Procedure

□  $F = (AB' + A'B)(C + D')$

○ Implement AND-OR circuit directly

 

 
○ Then convert it to all-NAND circuit along the procedure



# NOR Implementation
 
## □ NOR


- the dual of the NAND operation
- the NOR gate is also universal




# Graphic Symbols for a NOR Gate

- Two graphic symbols for a three input NOR gate

- OR-invert (c.f. AND-invert)

 

- invert-AND (c.f. invert-OR)

 


# Example of Two-level NOR Circuit

□  $F = (A + B)(C + D)E$

○ OR-AND

○ NOR-inverted-AND


⇒ NOR-NOR

 


# Example of Multilevel NOR Circuit

□  $F = (AB' + A'B)(C + D)$

○ AND-OR-AND circuit

 

○ NOR-NOR-NOR circuit

 



# Wired Logic

## ❑ Wired-AND

- the function performed by tying outputs of two open-collector TTL NAND gates
  
## ❑ Wired-OR


- OR function performed by tying outputs of two ECL NOR gates



## AOI with Wired AND

- Two level implementation with NAND-wired-AND

- $F = (AB)'(CD)'$

 


- $F = (AB + CD)' \Rightarrow$  AND-OR-INVERT (i.e., AOI) function



# OAI with Wired-OR

## □ Two-level implementation with NOR-wired-OR

○  $F = (A + B)' + (C + D)'$

 

○  $F = ((A + B)(C + D))' \Rightarrow$  OR-AND-INVERT (i.e., OAI ) function



# Nondegenerate Forms

- ❑ 16 possible combination of two-level forms
  - $\{\text{AND, OR, NAND, NOR}\} \times \{\text{AND, OR, NAND, NOR}\}$
- ❑ Degenerate form
  - 8 degenerate form = a single operation
  - ex.:  $\text{AND-AND} \Rightarrow \text{AND}$ ;  $\text{OR-OR} \Rightarrow \text{OR}$
- ❑ Nondegenerate form
  - 8 nondegenerate form = sum of products or product of sums

○ AND-OR	OR-AND
○ NAND-NAND	NOR-NOR
○ NOR-OR	NAND-AND
○ OR-NAND	AND-NOR

in each line, left form and right one are dual to each other



# Nondegenerate Form



---

- ❑ Sum of product
  - AND-OR, NAND-NAND
- ❑ Product of sum
  - OR-AND, NOR-NOR
- ❑ AOI
  - AND-NOR, NAND-AND
  - complement of AOI  $\Rightarrow$  sum of product
- ❑ OAI
  - OR-NAND, NOR-OR
  - complement of OAI  $\Rightarrow$  product of sum


# OAI(OR-AND-INVERT) Implementation

□  $F = (AB + CD + E)'$

○ AND-NOR

  



○ NAND-AND

 


# OAI(OR-AND-INVERT) Implementation

□  $F = ((A + B)(C + D)E)'$

○ OR-NAND

  

○ NOR-OR

 



# Implementation with Other Two-level Forms

## □ Tabular summary

Equivalent Nondegenerate Form		Implements the Function	Simplify $F'$ into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	$F$
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	$F$

\*Form (b) requires an inverter for a single literal term.

## Example 3.10

□ Given function presentation


$x \backslash yz$		$y$			
		00	01	11	10
$x' \{$	0	$m_0$ 1	$m_1$ 0	$m_3$ 0	$m_2$ 0
	1	$m_4$ 0	$m_5$ 0	$m_7$ 0	$m_6$ 1

- $F = x'y'z' + xyz'$
- $F' = (x + y + z)(x' + y' + z)$  (product-of-sums form)
- $F' = x'y + xy' + z$  (sum-of-products form)


## Example 3.10

□ Implement  $F$  in terms of AOI form

○  $F' = x'y + xy' + z$

 

AND-NOR

 


NAND-AND




## Example 3.10

□ Implement  $F$  in terms of OAI form

○  $F' = (x + y + z)(z' + y' + z)$

 

OR-NAND

 

NOR-OR



# Exclusive-OR Function

---

## ❑ Exclusive-OR

- $x \oplus y = x'y + xy'$

## ❑ Exclusive-NOR

- $(x \oplus y)' = xy + x'y'$

## ❑ Identities in XOR operation

- $x \oplus 0 = x$

- $x \oplus 1 = x'$

- $x \oplus x = 0$

- $x \oplus x' = 1$

- $x \oplus y' = x' \oplus y = (x \oplus y)'$



# Exclusive-OR Functions

---

## □ Commutativity

- $A \oplus B = B \oplus A$
- what is the physical meaning?


## □ Associativity

- $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$
- what is the physical meaning?

# XOR Implementation


□  $x \oplus y = x'y + xy'$

○ NOT, AND, OR gates

 

□  $x \oplus y = (xy)'x + (xy)'y$

○ NAND gates

 



# Odd Function

## □ 3 variable XOR function

○  $A \oplus B \oplus C = \sum (1, 2, 4, 7)$

$A \backslash BC$		$B$			
		00	01	11	10
$A$	0	$m_0$	$m_1$ 1	$m_3$	$m_2$ 1
	1	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$

$C$

## □ Definition: odd function

- Multi-variable XOR function is equal to 1 if the number of variables that are equal to 1 is odd.



# Even Function


## □ Definition

- complement of the multi-variable XOR function is equal to 1 if the number of variables that are equal to 1 is even.
- $(A \oplus B \oplus C)' = \sum(0, 3, 5, 6)$


$A \backslash BC$		$B$			
		00	01	11	10
$A$	0	$m_0$ 1	$m_1$	$m_3$ 1	$m_2$
	1	$m_4$	$m_5$ 1	$m_7$	$m_6$ 1

# Implementation of 3-variable XOR

## ❑ Odd function

 

## ❑ Even function

 

# Four-variable XOR function

□ Odd function

$$\bigcirc A \oplus B \oplus C \oplus D$$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$	$m_1$ 1	$m_3$	$m_2$ 1
	01	$m_4$ 1	$m_5$	$m_7$ 1	$m_6$
	11	$m_{12}$	$m_{13}$ 1	$m_{15}$	$m_{14}$ 1
	10	$m_8$ 1	$m_9$	$m_{11}$ 1	$m_{10}$
		D			

Even function

$$(A \oplus B \oplus C \oplus D)'$$

AB \ CD		C			
		00	01	11	10
A	00	$m_0$ 1	$m_1$	$m_3$ 1	$m_2$
	01	$m_4$	$m_5$ 1	$m_7$	$m_6$ 1
	11	$m_{12}$ 1	$m_{13}$	$m_{15}$ 1	$m_{14}$
	10	$m_8$	$m_9$ 1	$m_{11}$	$m_{10}$ 1
		D			




# Parity Generation


## □ Even parity generator for 3-bit message

### ○ Truth table

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

 ○  $P$  is an odd function  $\Rightarrow P = x \oplus y \oplus z$




# Parity Checker

## □ Even parity checker for 3-bit message

○ Truth table

○  $C(x,y,z,P)$  is an odd function

 

Four Bits Received				Parity Error Check
$x$	$y$	$z$	$P$	$C$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0



---

# Discussion ~ ~ ~