



Ch. 07. Memory and Programmable Logic

2019. 5. 20.

K-S. Sohn




Contents

- ❑ Memory unit
 - RAM, ROM
- ❑ Programmable logic devices
- ❑ Combinational PLDs
 - PROM, PAL, PLA
- ❑ Sequential PLDs
 - SPLD, CPLD, FPGA



Introduction

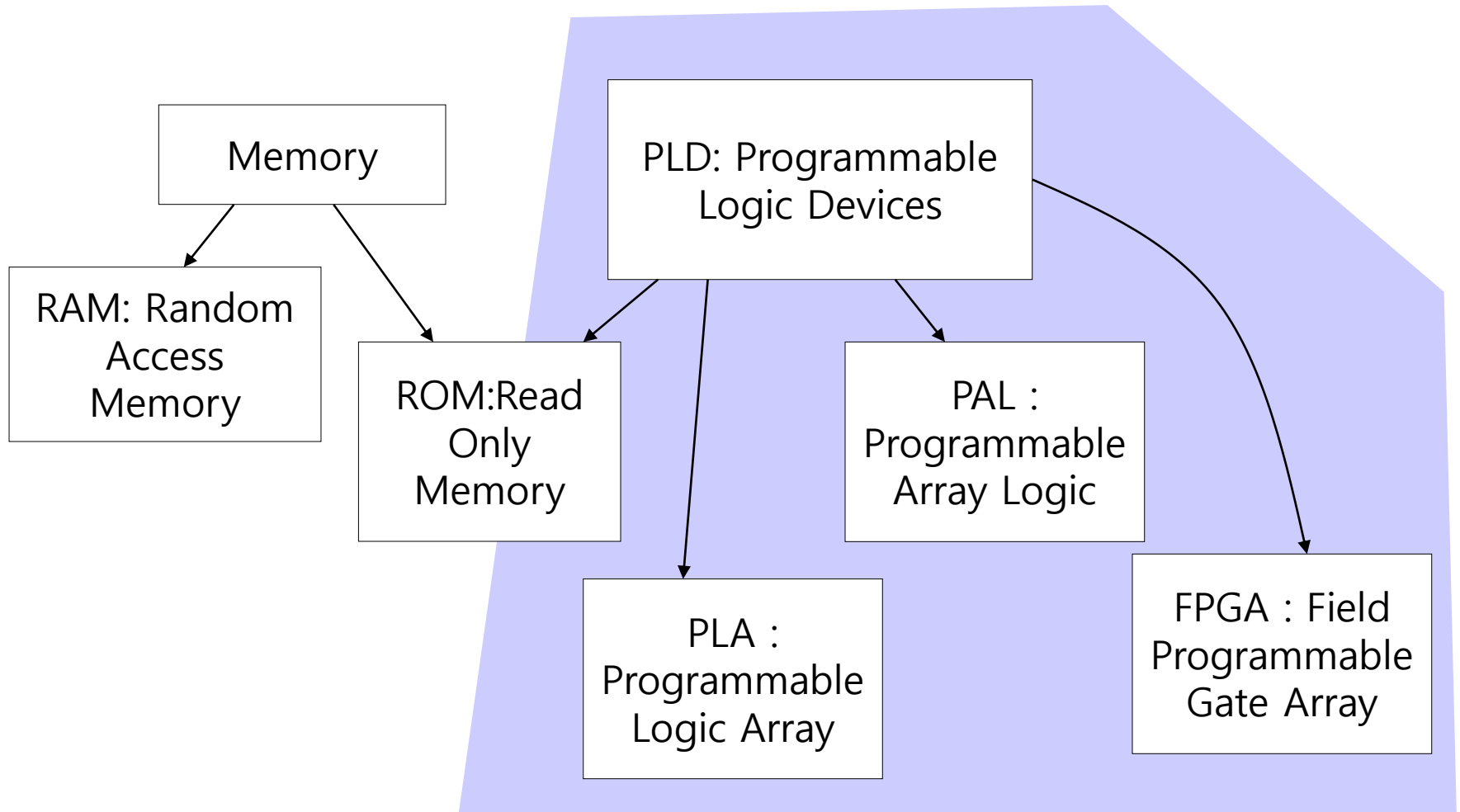




Icons for Array Logic Diagram



❑ Objectives

- To represent the complex internal logic of programmable logic devices in a concise form.

❑ Examples

 

(a) Conventional symbol

  

(b) Array logic symbol


Block Diagram of Memory Unit

❑ Memory Unit

- An electronic device that writes/reads n -bit word located by k -bit address

❑ Word

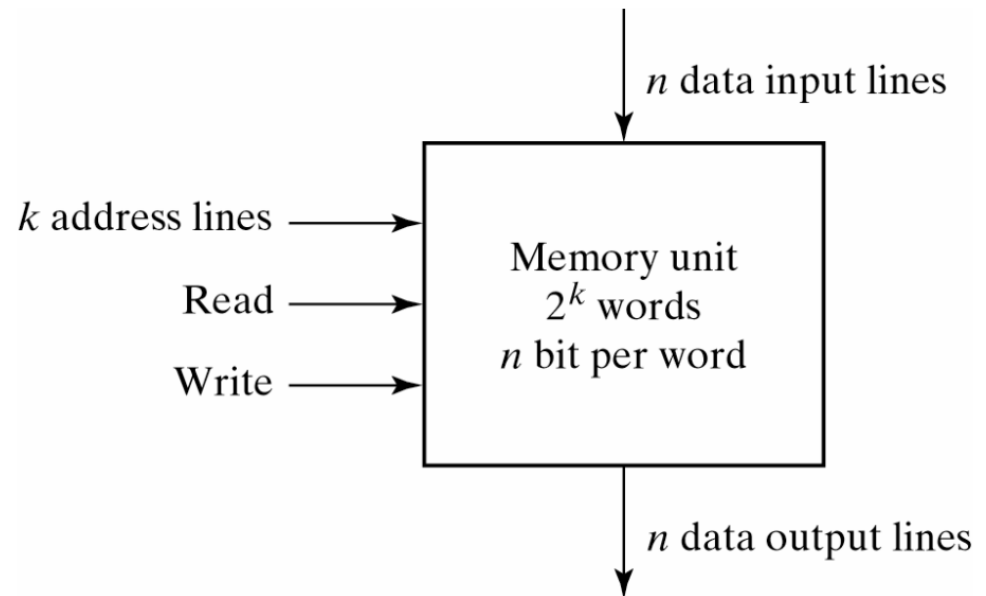- The unit of data written/read to/from the memory unit
- c.f. : byte, octet





Structure of Memory Unit

Memory address		Memory content
Binary	decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	•	•
	•	•
	•	•
	•	•
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101



Operations of Memory Units

❑ Procedure of WRITE operation

- Apply the address
- Apply the data
- Activate the '*Write*' input line

❑ Procedure of READ operation

- Apply the address
- Activate the '*Read*' input line



Control Inputs to Memory Unit


- ❑ Control inputs
 - Memory Enable
 - Read/Write

Table 7-1
Control Inputs to Memory Chip

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

Memory Operation in Timing Diagram

❑ WRITE operation

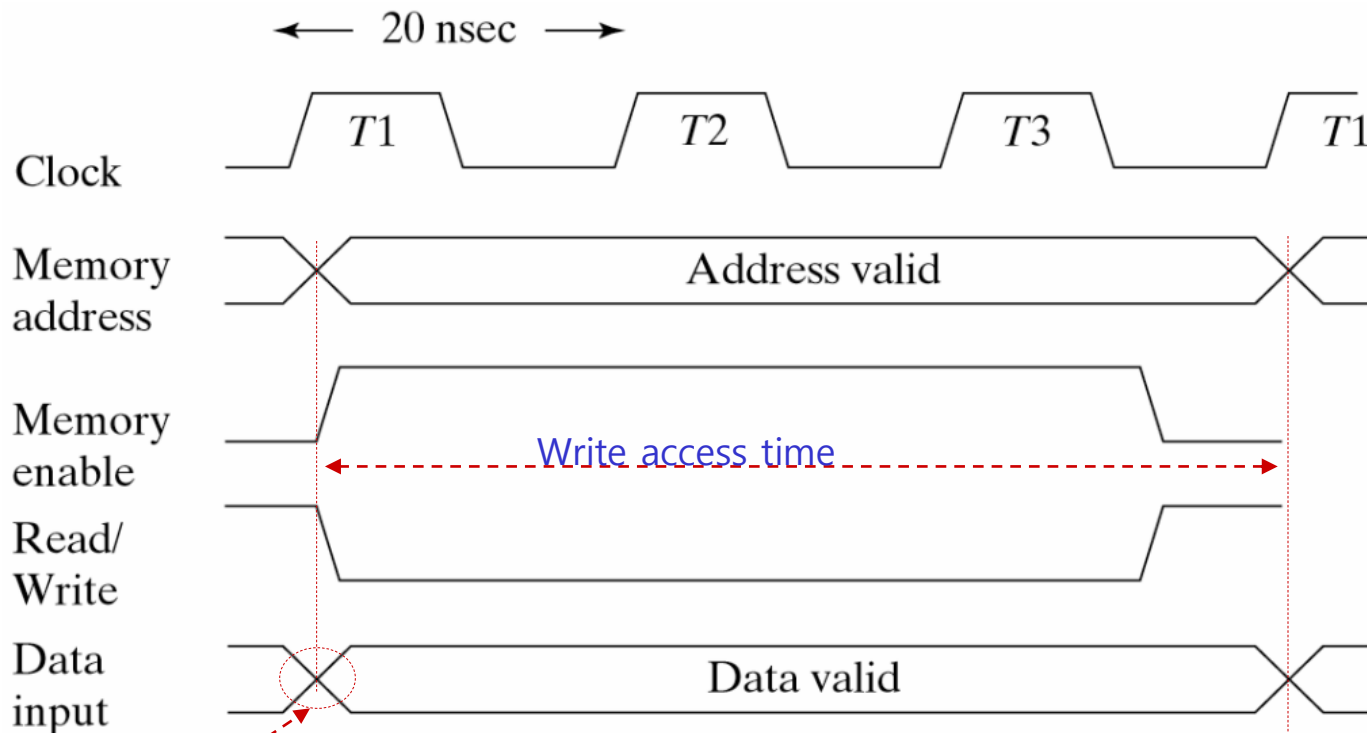


(a) Write cycle

Possible change in value of the multiple lines

Memory Operation in Timing Diagram

□ READ operation

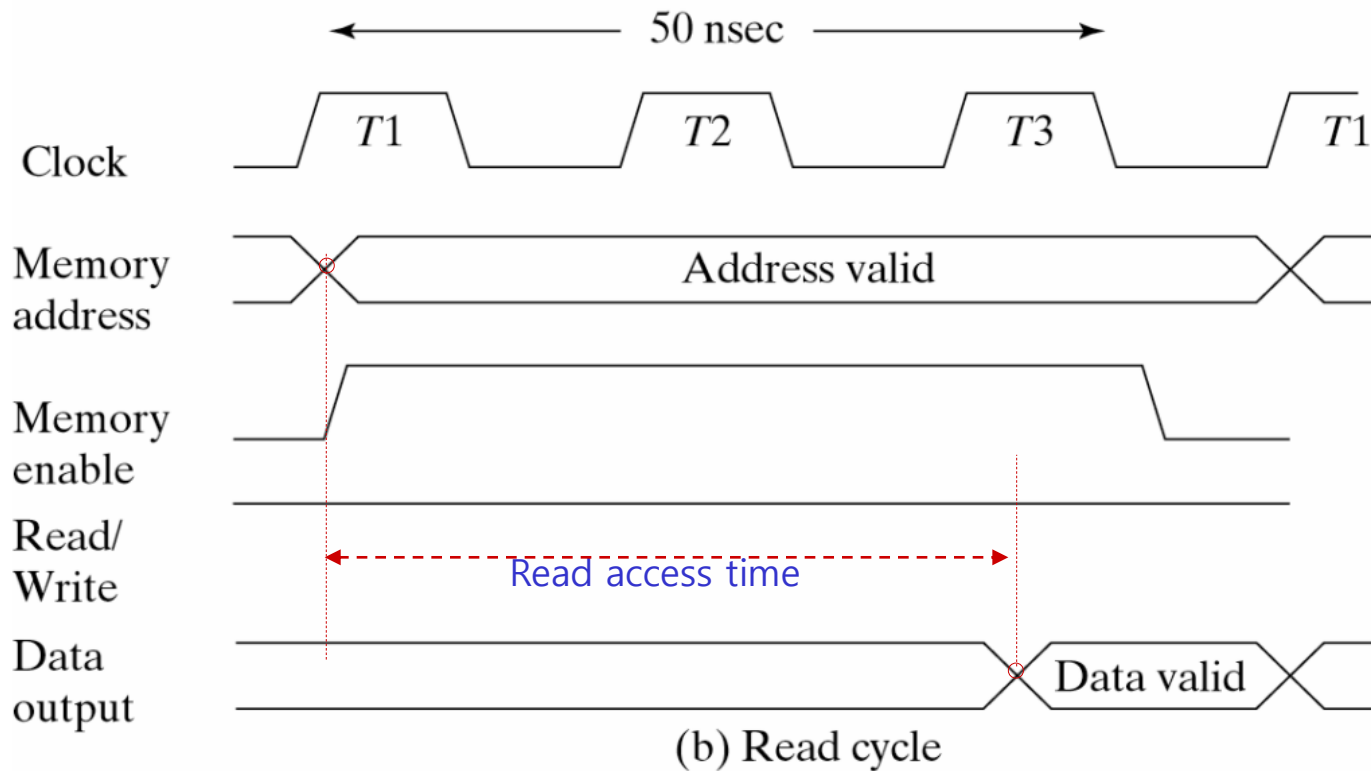



Types of Memories



- ❑ SRAM : static RAM
 - Fast
- ❑ DRAM : dynamic RAM
 - Slower but smaller space required (1/4 of SRAM)
 - Lower power discipation
 - MOSFET and capacitor
 - Refreshing (recharging the internal capacitor)
- ❑ ROM : read only memory
 - Nonvolatile memory

Memory Cell

❑ Block diagram

- Select : generated by address decoding
- Input, Output : 1-bit data lines

❑ Logic diagram

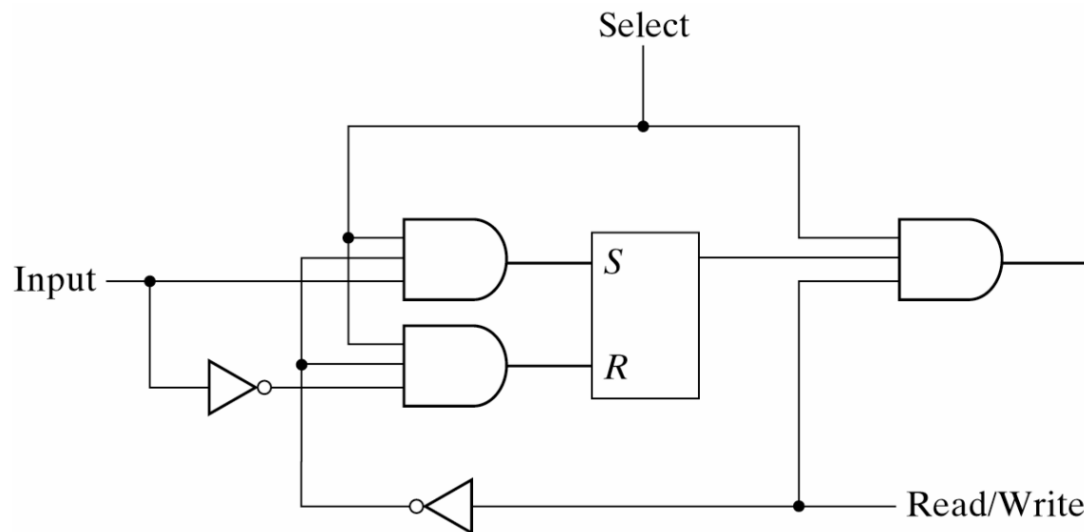 




Coincident Address Decoding

Objectives

 - To reduce the size of the address decoder by space multiplexing




Address Multiplexing

❑ Objectives


- To reduce the size of address decoder
- To reduce the number of pins in the IC package

❑ Operational description

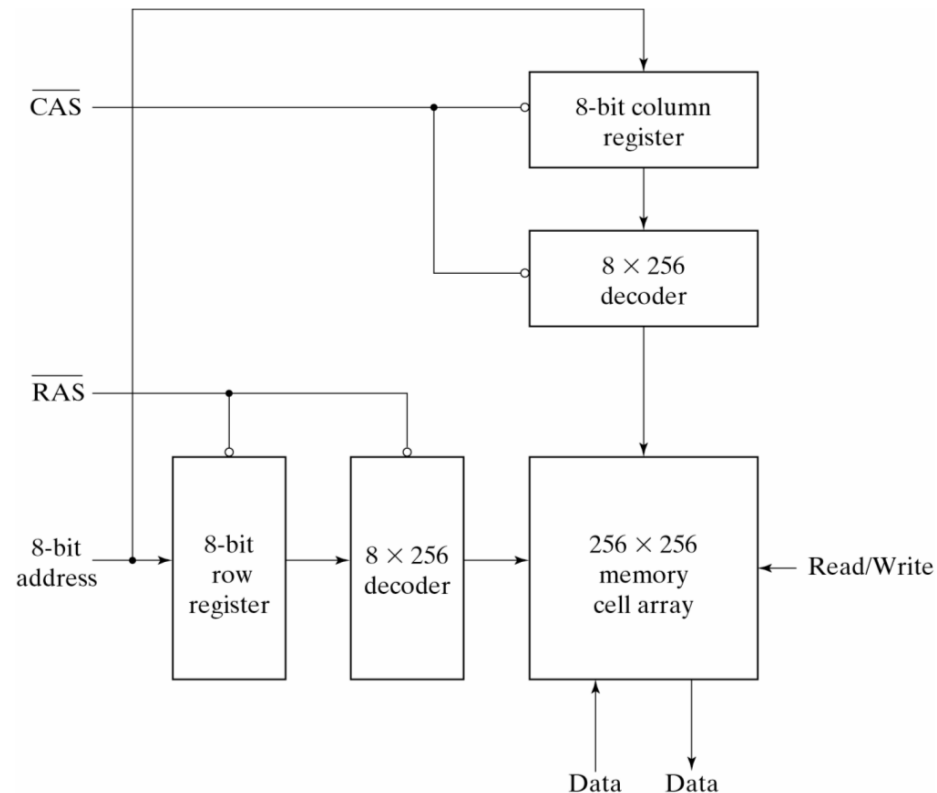- Addressing with a time lag
- Time division multiplexing version of the coincident addressing
- CAS(column address strobe) first, and then, RAS(row address strobe)



Error Detection And Correction

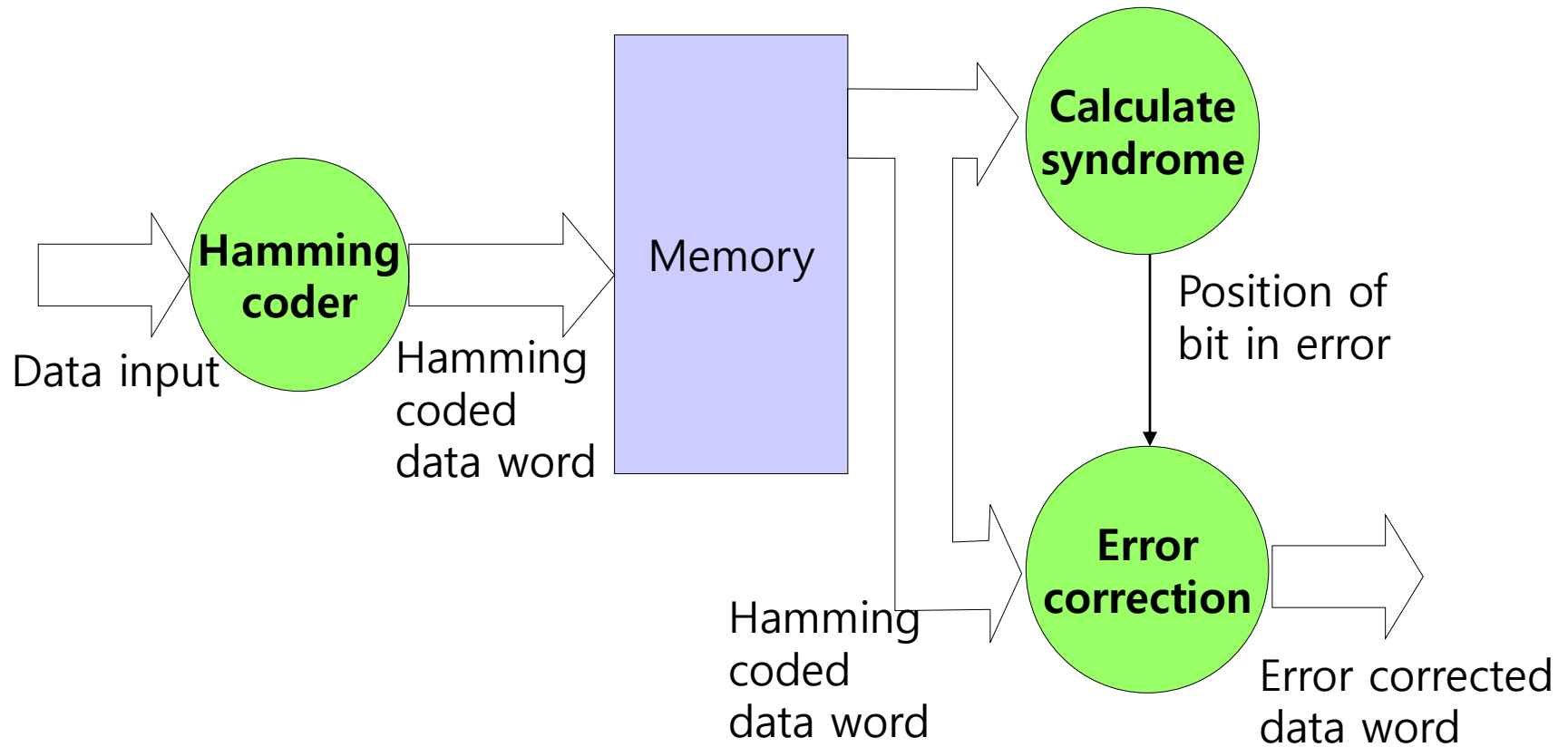



Bit Error Syndrome

□ Assumption

- Bit position number : $1, 2, \dots, n+k$, where n is the number of data bits and k is the number of parity bits.

□ Syndrome

- A binary number designating the position of the bit being in error
- $S = S_{k-1} \dots S_0 \Rightarrow$ A syndrome S is a k -bit binary number (Ex. $S = 3_{(10)}$ indicates that the 3rd bit of the checked word is in error.)
- If $S_i = 0$, all bits whose positions are numbered by the binary number in which the i -th significant bit is 1 are correct
- If $S_i = 1$, one or more such a bits are in error.



Hamming Code

❑ Assumption

- k parity bits(p_1, p_2, \dots, p_{k-1}) are added to an n -bits data word

❑ Coding scheme

- The bit positions are numbered in sequence from 1 to $n+k$
- Those positions numbered as a power of 2 are reserved for the parity bits
- $p_i = \text{XOR of bits that the } i\text{-th significant bits of their position number is 1}$

❑ Example

- 8-bit data word : 11000100
- Hamming code of 1100011 : **00**1**1**100**1**0100




Syndrome of Hamming Code

- ❑ Evaluation of syndrome from a Hamming Coded memory word
 - S_i = XOR of bits p_i and the data bits that the i -th significant bit of their position number is 1.
- ❑ Example
 - $k=4$, $n=8$, hamming coded word=001110010100
 - S_0 =XOR of bits(1,3,5,7,9,11)
 - S_1 =XOR of bits(2,3,6,7,10,11)
 - S_2 =XOR of bits(4,5,6,7,12)
 - S_3 =XOR of bits(8,9,10,11,12)


Read Only Memory (ROM)

❑ Permanent storage

○ Block diagram of ROM

 

○ Internal logic of ROM (Ex.: 32x8 ROM)

 

ROM

❑ Programming the ROM as the permanent storage


ROM Truth Table (Partial)

Inputs					Outputs							
I4	I3	I2	I1	I0	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮					⋮					
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

ROM programmer

generating high voltage signal to blow out fuse of the contact point corresponding to '0' value.

List of 32 8-bit words

 

Combinational Circuit Implementation with ROM

□ Reinterpretation of the ROM truth table

ROM Truth Table (Partial)

Inputs						Outputs							
I4	I3	I2	I1	I0		A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	m_0	1	0	1	1	0	1	1	0
0	0	0	0	1	m_1	0	0	0	1	1	1	0	1
0	0	0	1	0	m_2	1	1	0	0	0	1	0	1
0	0	0	1	1	m_3	1	0	1	1	0	0	1	0
		⋮			...			⋮					
1	1	1	0	0	m_{28}	0	0	0	0	1	0	0	1
1	1	1	0	1	m_{29}	1	1	1	0	0	0	1	0
1	1	1	1	0	m_{30}	0	1	0	0	1	0	1	0
1	1	1	1	1	m_{31}	0	0	1	1	0	0	1	1

List of minterm

$$A_7 = \Sigma(0, 2, 3, \dots, 29)$$

$$A_1 = \Sigma(0, 3, \dots, 29, 30, 31)$$

Types of ROM

- ❑ Mask ROM


- ❑ PROM(Programmable ROM)

- ❑ EPROM(Erasable PROM)

 - Erase = to discharge the internal floating gate with U.V. light

- ❑ EEPROM(Electrically EPROM)

  - Erase = to discharge the internal floating gate electrically





Types of Combinational PLDs


❑ PROM



❑ PAL (Programmable Array Logic)



❑ PLA (Programmable Logic Array)

 




PLA(Programmable Logic Array)

❑ PROM and PLA

PROM	PLA
Decoder	Array of AND gates
Full minterms	Partial minterms
Full decoding of the variables	Partial decoding of the variables

Internal Logic of a PLA

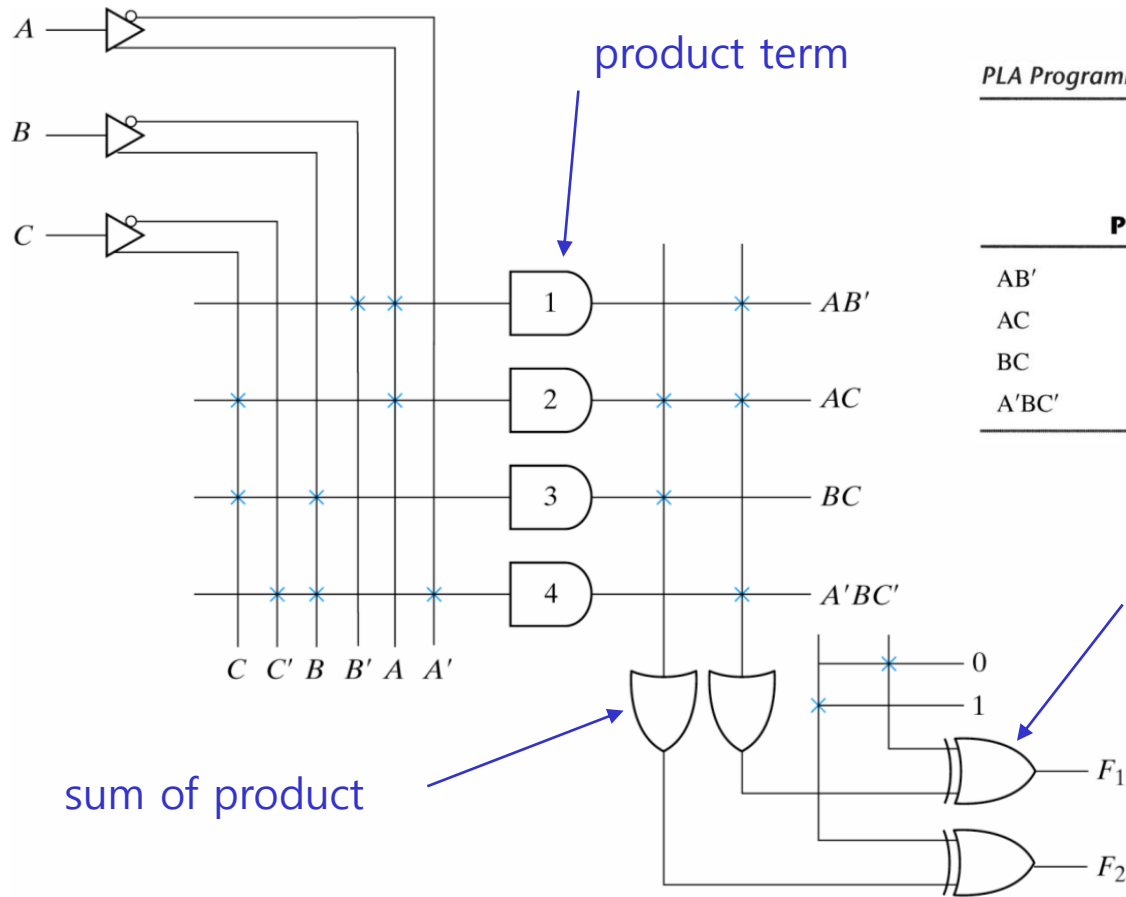

PLA Programming Table

		Inputs			Outputs	
					(T)	(C)
	Product Term	A	B	C	F ₁	F ₂
AB'	1	1	0	–	1	–
AC	2	1	–	1	1	1
BC	3	–	1	1	–	1
A'BC'	4	0	1	0	1	–


true or complement
of the boolean function

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

PAL(Programming Logic Array)

Section
3 AND, 1 OR gates

 

Array of sections

Section : A unit of programmable logic

PAL Programming

□ Requirement

- Boolean functions for required combinational circuits

$$w(A, B, C, D) = \sum(2, 12, 13)$$

$$x(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \sum(1, 2, 8, 12, 13)$$

□ Simplifying the circuit

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

□ PAL programming table

Product Term	AND Inputs				W	Outputs
	A	B	C	D		
1	1	1	0	–	–	$w = ABC' + A'B'CD'$
2	0	0	1	0	–	
3	–	–	–	–	–	
4	1	–	–	–	–	$x = A + BCD$
5	–	1	1	1	–	
6	–	–	–	–	–	
7	0	1	–	–	–	$y = A'B + CD + B'D'$
8	–	–	1	1	–	
9	–	0	–	0	–	
10	–	–	–	–	1	$z = w + AC'D' + A'B'C'D$
11	1	–	0	0	–	
12	0	0	0	1	–	

PAL Programming


□ PAL fuse map

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$
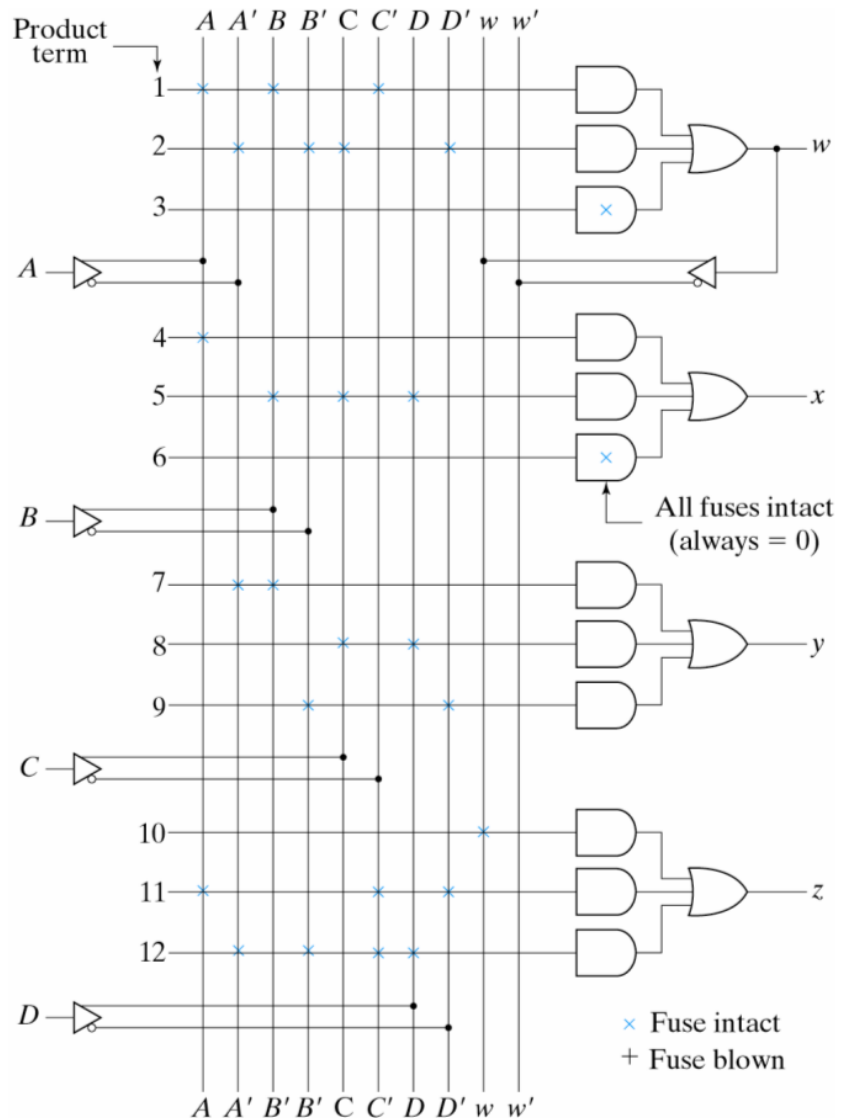
$$\begin{aligned} z &= ABC' + A'B'CD' + AC'D' + A'B'C'D \\ &= w + AC'D' + A'B'C'D \end{aligned}$$





Sequential PLD

❑ c.f. Combinational PLDs

- PROM, PAL, PLA

❑ Definition of SPLD


- The PLD that includes both gates and flip-flops

❑ Type of SPLD

- SPLD : Sequential(or Simple) programmable logic device
- CPLD : Complex programmable logic device
- FPLS : Field programmable logic sequencer
- FPGA : Field programmable gate array



Block Diagram of SPLD

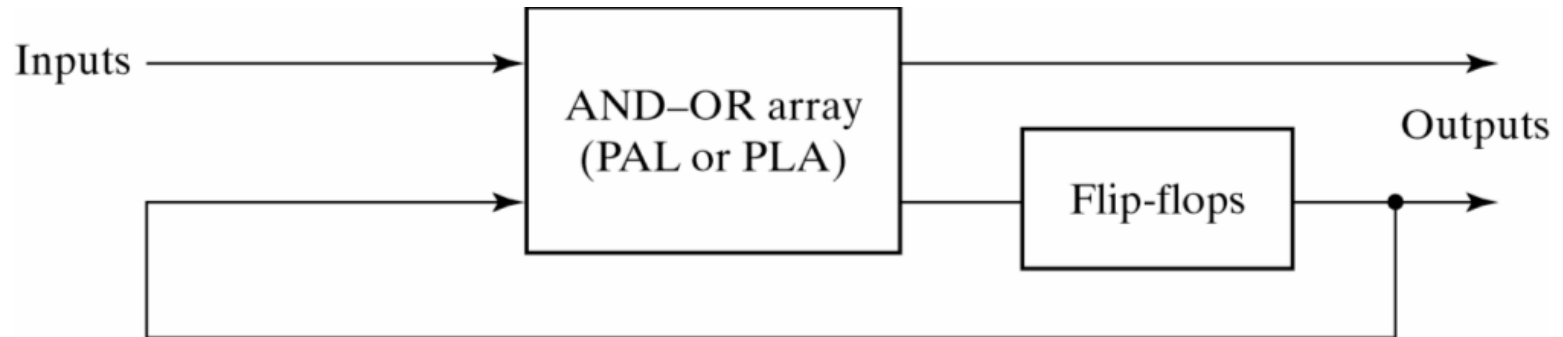


Macrocell

❑ Definition

- Each section of an SPLD
- Sum of product combinational logic + (optional) flip flop

❑ Basic logic diagram of macrocell

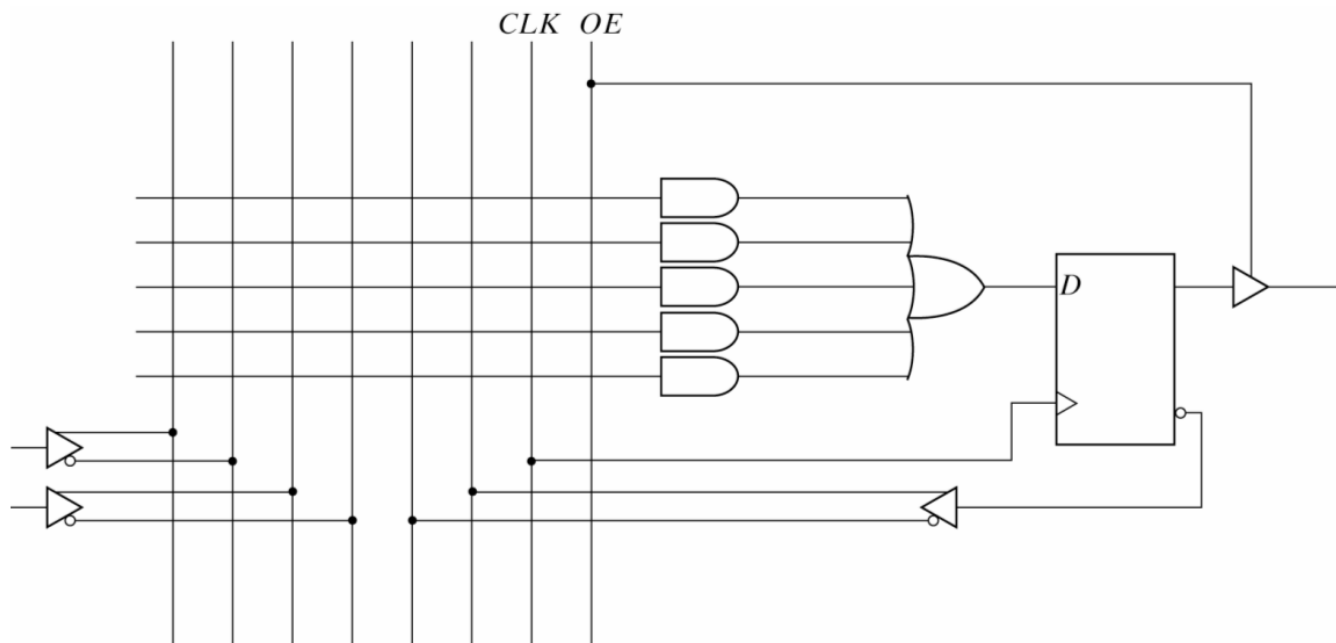


CPLD(Complex Programmable Logic Device)

❑ Definition

- A collection of individual PLDs connected through a programmable interconnection structure(e.g., switch) on a single IC

❑ Block diagram of CPLD

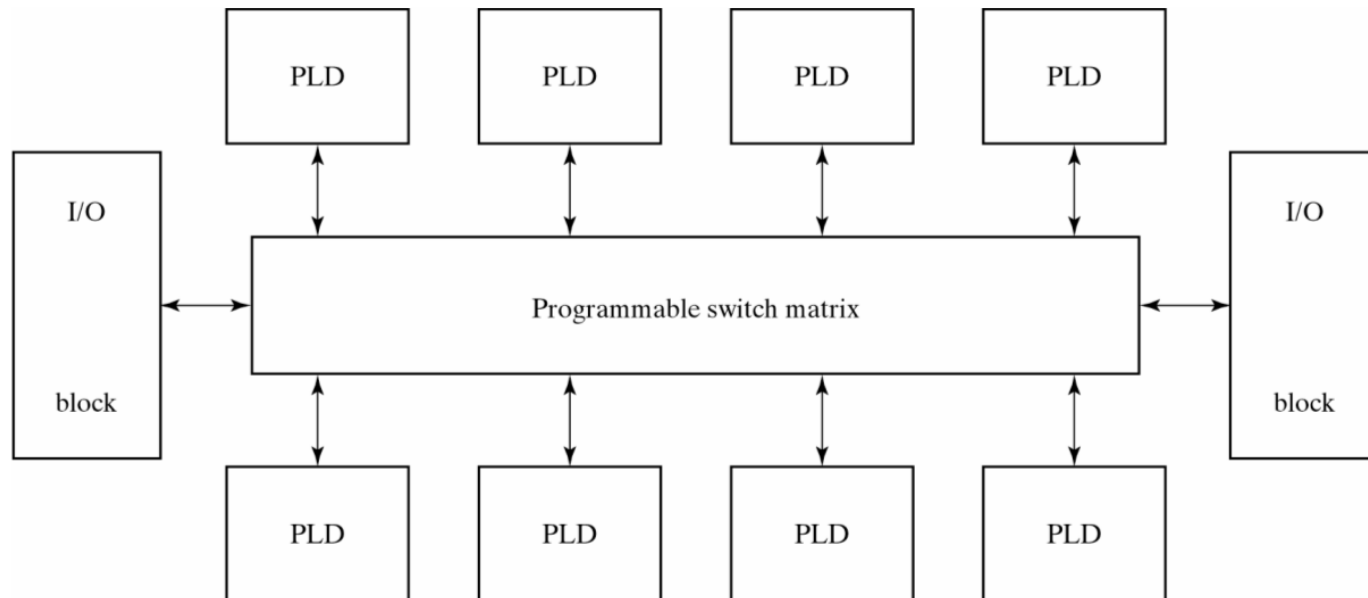



FPGA(Field Programmable Gate Array)

❑ Components of an FPGA

○ Logic block


- Lookup tables -- A truth table stored in an SRAM
- Multiplexers, Gates
- Flip-flops


○ Programmable I/O block


○ Programmable interconnection block


❑ Internal truth table

 
- Provides the combinational functions for the logic block
- The functions are realized from the truth table stored in the SRAM, similar to the manner that combinational circuit functions are implemented with ROM




 


 


 


 


 


 


 


 


 


 


 


 

 

 

 

 



Discussion ~ ~ ~