

Ch. 08. Design at the Register Transfer Level

2019. 6.10.

K-S. Sohn




Contents



Purposes of RTL Design

 - ❑ Describing and designing large, complex digital systems





Module of a Digital System

- ❑ Module = Registers + Operations
- ❑ 3 components of the specification of a module
 - registers
 - operations on registers (data)
 - control supervising the sequence of operations

Operations

□ Type of Operations

- Transfer
- Logical
- Arithmetic
- Shift


□ Operators

- Verilog operators

Operator Type	Symbol	Operation Performed	Priority Group
Arithmetic	+	addition	1 (unary), 4 (binary)
	-	subtraction	1 (unary), 4 (binary)
	*	multiplication	3
	/	division	3
	**	exponentiation	2
	%	modulus	2
Bitwise or Reduction	~	negation (complement)	1
	&, ~&	AND, NAND (reduction)	1
	, ~	OR, NOR (reduction)	1
	^, ~^	XOR, XNOR (reduction)	1
	^, ~^, ^~	XOR, XNOR (binary)	9
Logical	!	negation	1
	&&	AND (binary)	11
		OR (binary)	12
	&	AND (binary)	8
		OR (binary)	10
Shift	>>	logical right shift	5
	<<	logical left shift	5
	>>>	arithmetic right shift	5
	<<<	arithmetic left shift	5
Relational	>	greater than	6
	<	less than	6
	<=	less than or equal	6
	>=	greater than or equal	6
Equality	==	equality	7
	!=	inequality	7
	===	case equality	7
	!==	case inequality	7
Conditional	? :	ternary selection	13
Concatenation	{ } {}}	joins operands	14

Algorithmic State Machines (ASMs)

□ Digital system = Controller + Datapath

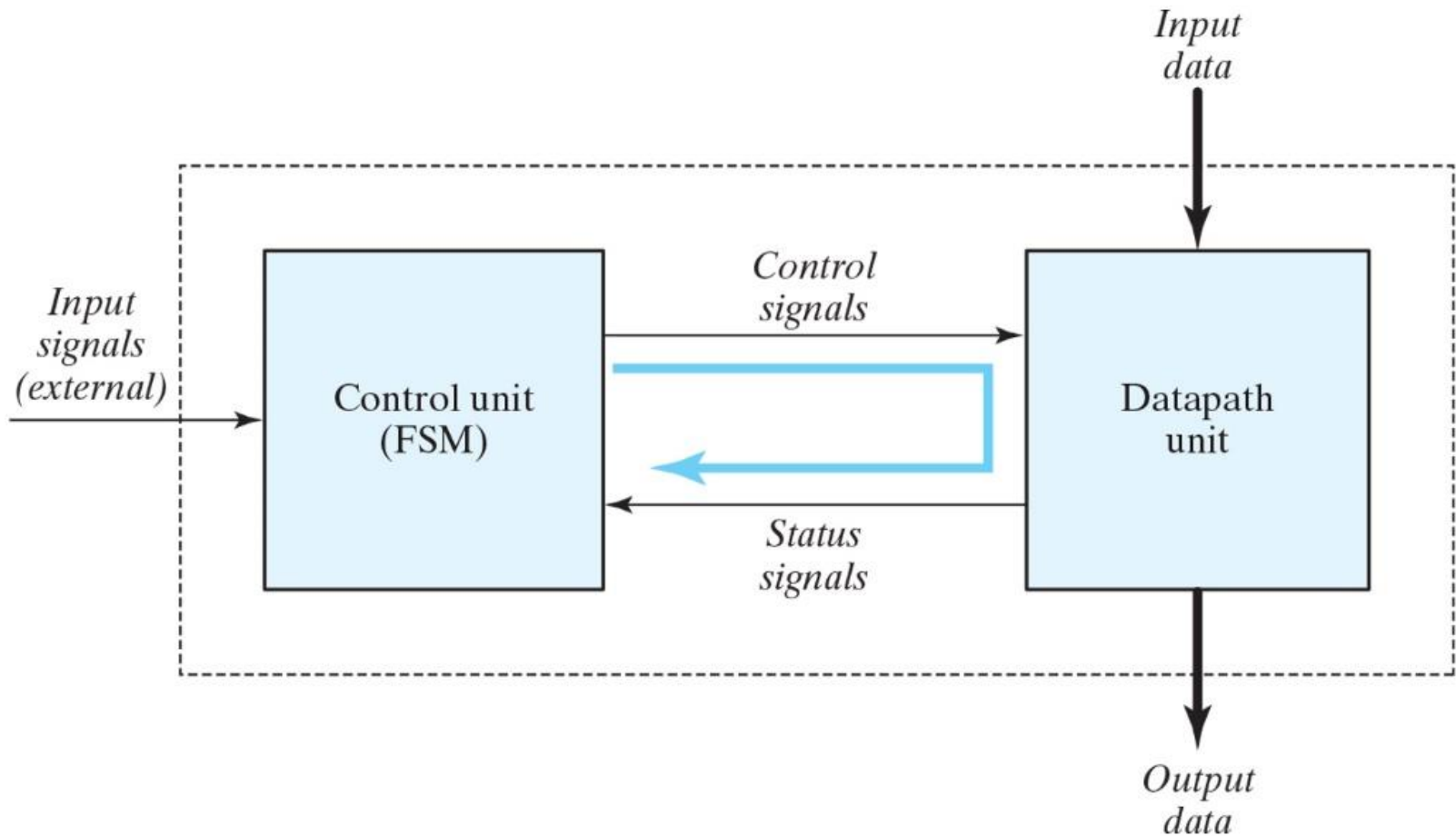



Algorithmic State Machines (ASMs)

❑ Controller


- Controls the operations in the datapath unit
- Described by ASM chart

❑ Datapath

- Executes operations on data
- Described by ASMD chart

ASM Chart Components

❑ State box

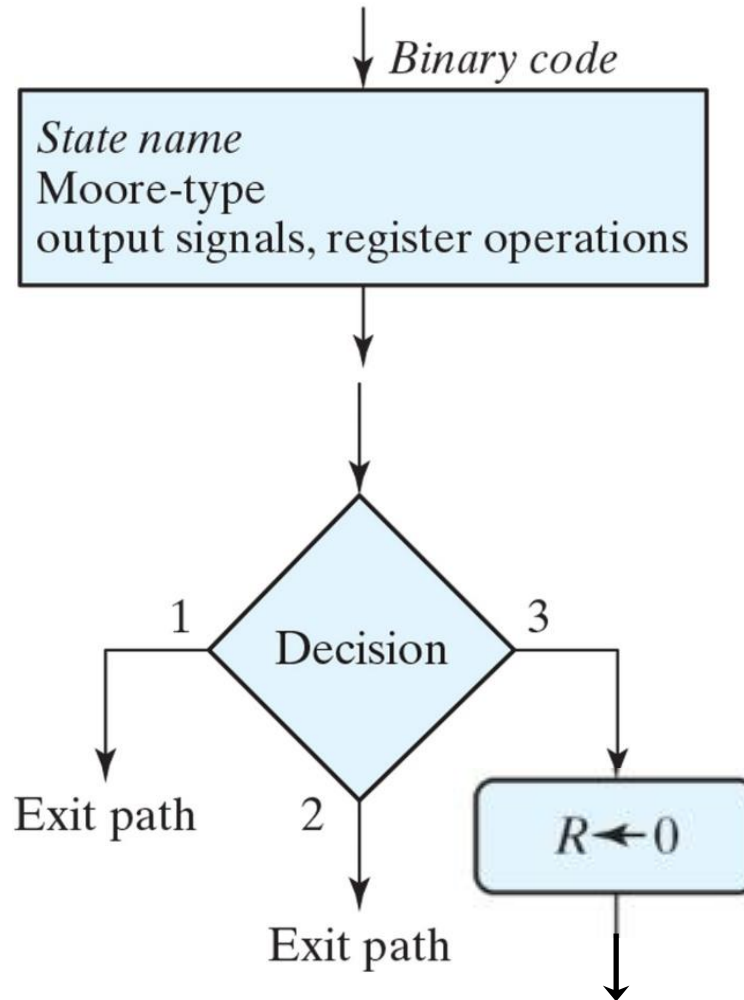

❑ Decision box

❑ Conditional box

ASM Chart Form


❑ State box

- state name, state code
- Moore type output signals
- unconditional reg. op.

❑ Decision box



❑ Conditional box

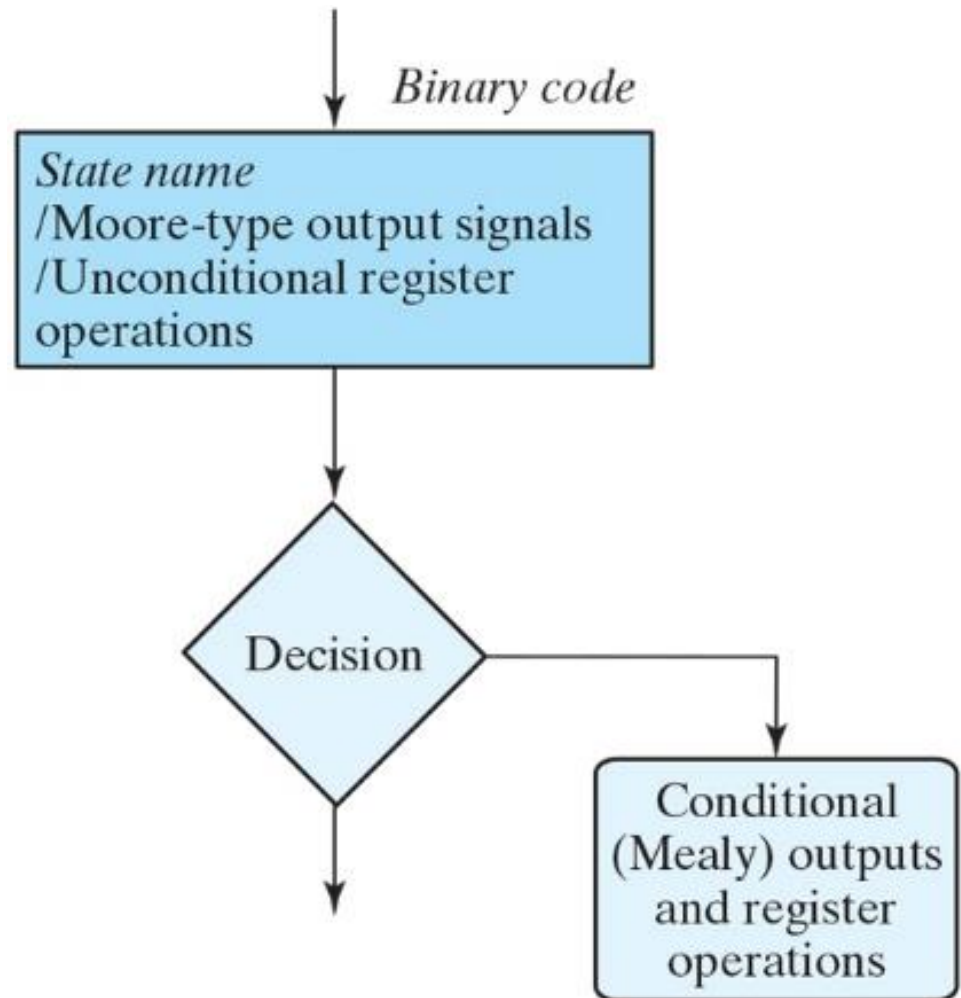- Mealy output signals
- conditional reg. op.



ASM Chart (Ex.)



- ASM with reg. op. and control signals

  

ASM Block


□ ASM block components

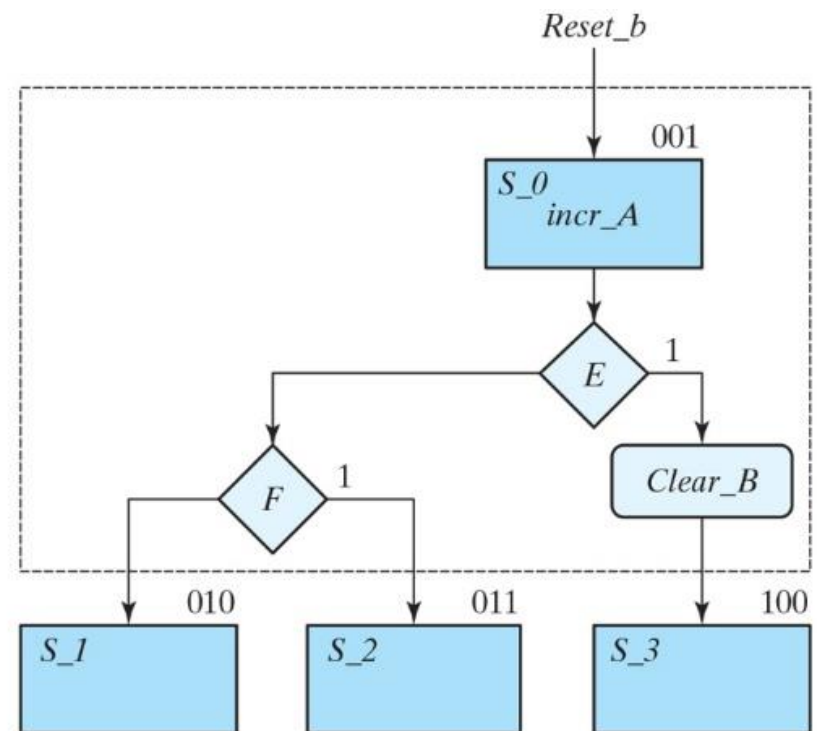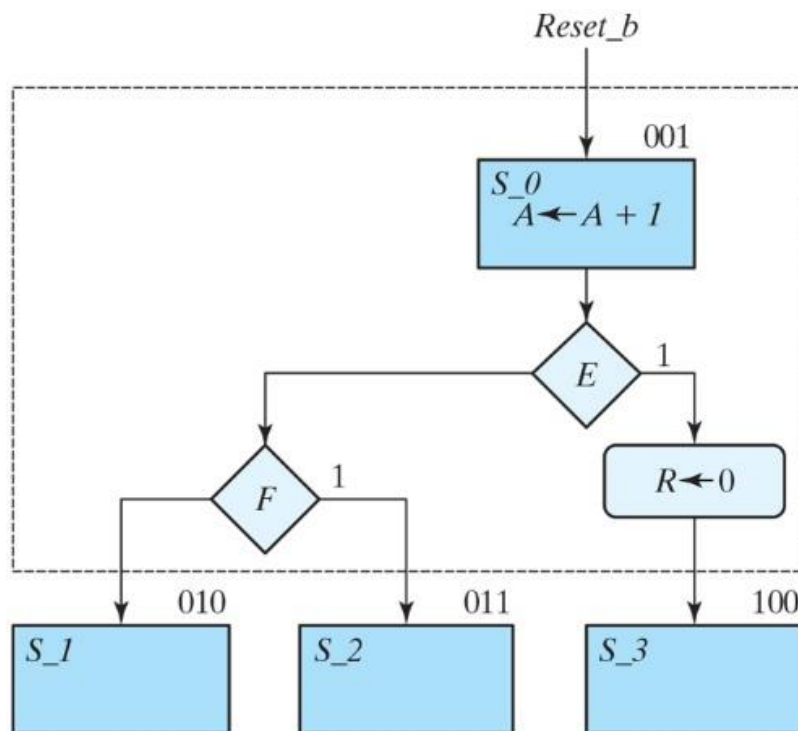- one state box
- optionally, decision box and conditional box




State Diagram vs. ASM Chart

 - ❑ State diagram equivalent to the ASM chart




Timing Considerations

□ State transition timing

 

ASM Chart (Practice 8.10)

- ASM chart for 3 consecutive 1 detector

 




ASMD(ASM and Datapath)

□ Example: Design requirements

- If $A2 = 0$,
 - E is cleared to 0 and the count continues.
- If $A2 = 1$,
 - E is set to 1;
 - then, if $A3 = 0$,
 - ❖ the count continues,
 - but if $A3 = 1$,
 - ❖ F is set to 1 on the next clock pulse and the system stops counting.
- Then, if $Start = 0$,
 - the system remains in the initial state,
- but if $Start = 1$,
 - the operation cycle repeats.


The Example

❑ Block diagram

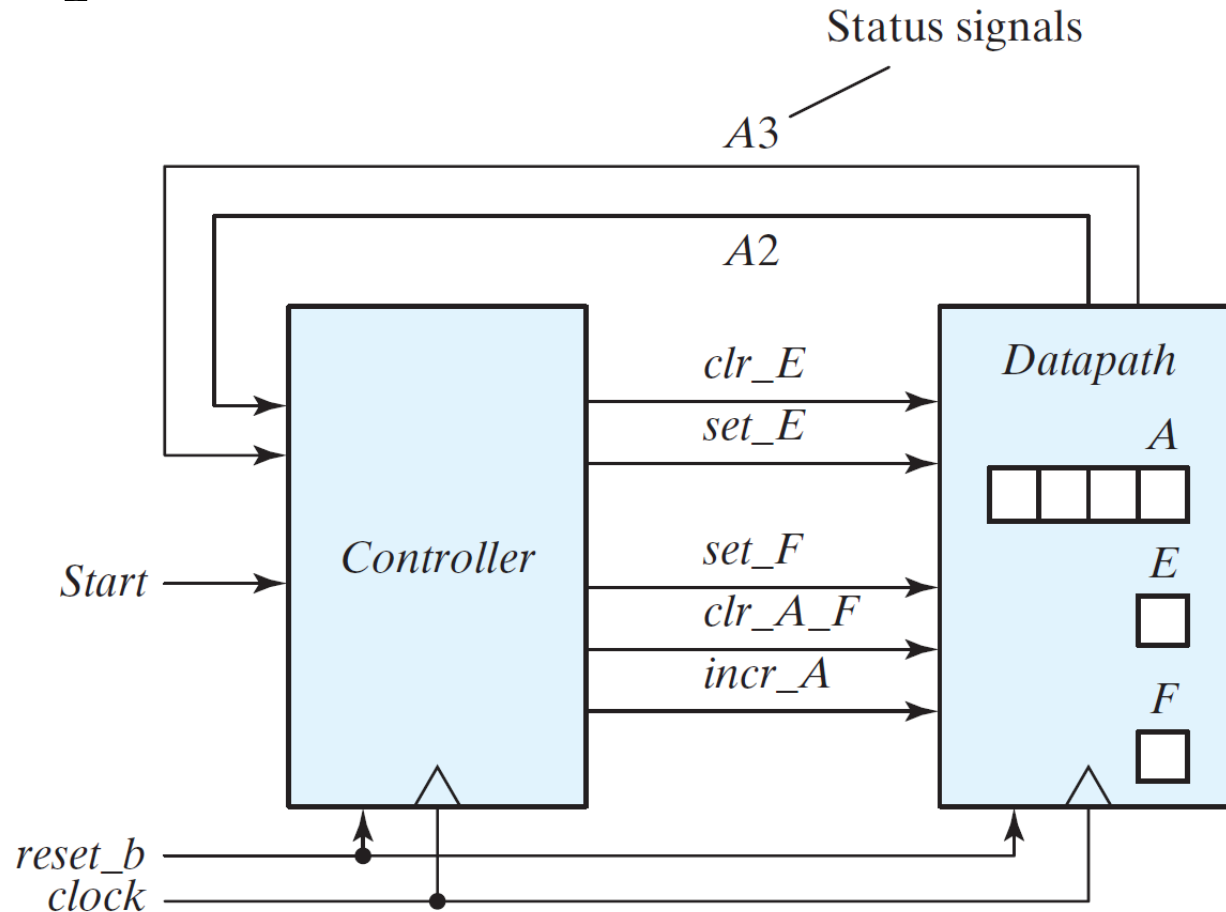


ASM of the Example

□ ASM chart

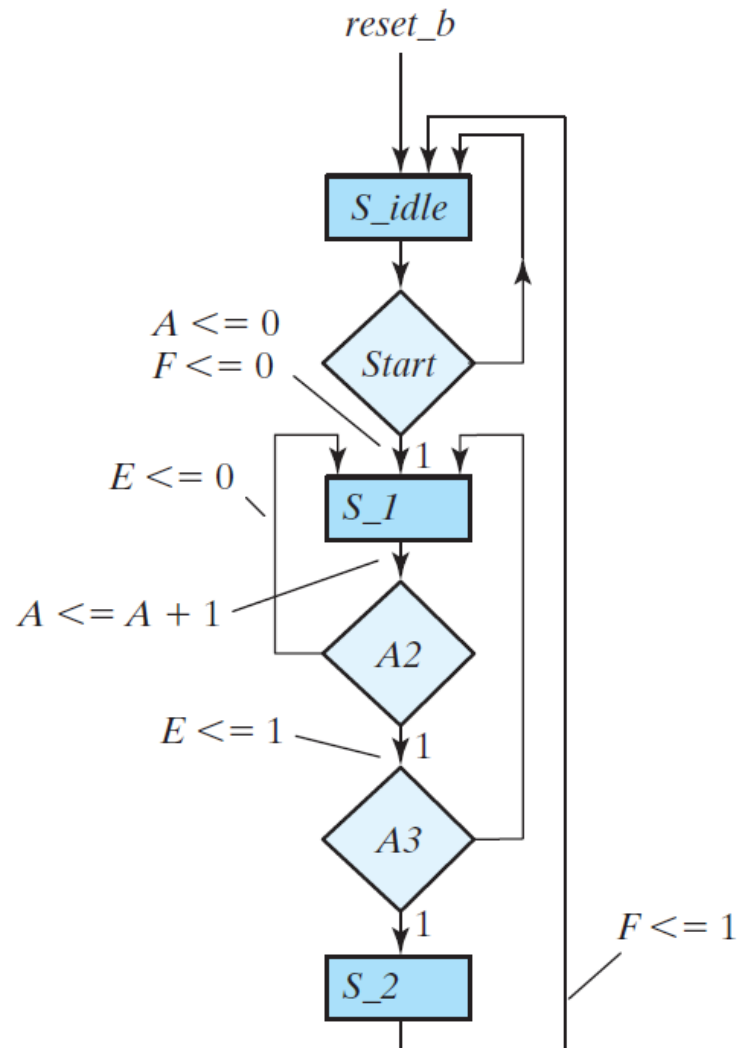

ASMD of the Example


ASMD chart

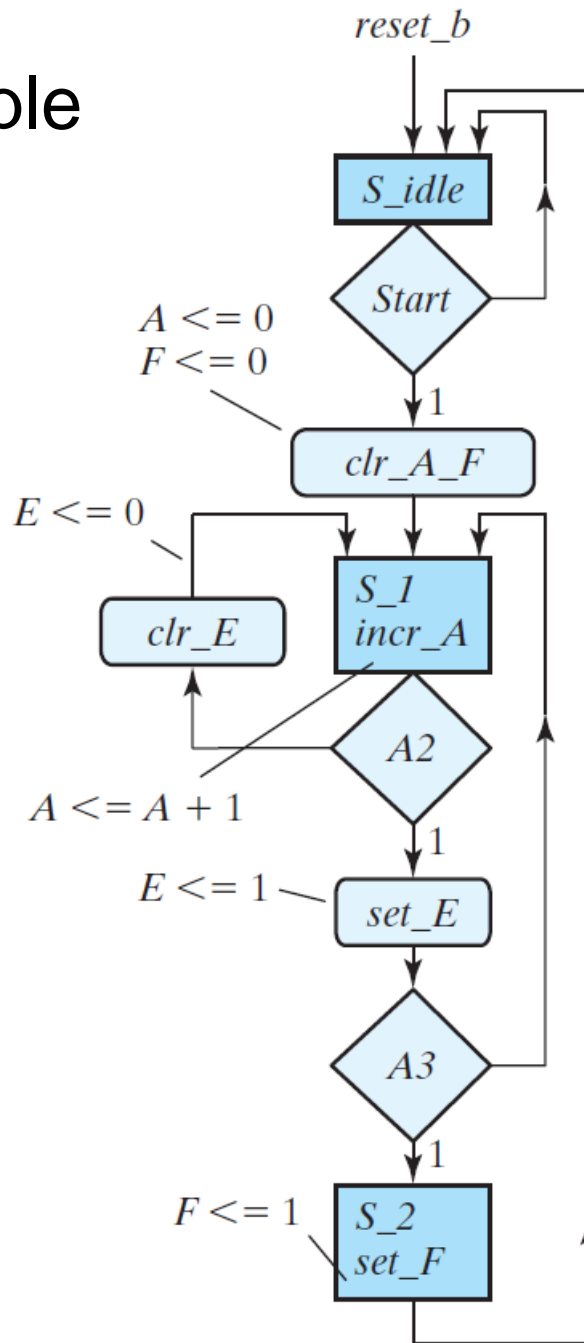


Sequence of Operations of the Example

Counter				Flip-Flops		Conditions	State
A_3	A_2	A_1	A_0	E	F		
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	S_1
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	
1	1	0	1	1	0		S_2
1	1	0	1	1	1		S_idle

Block Diagram of the Example

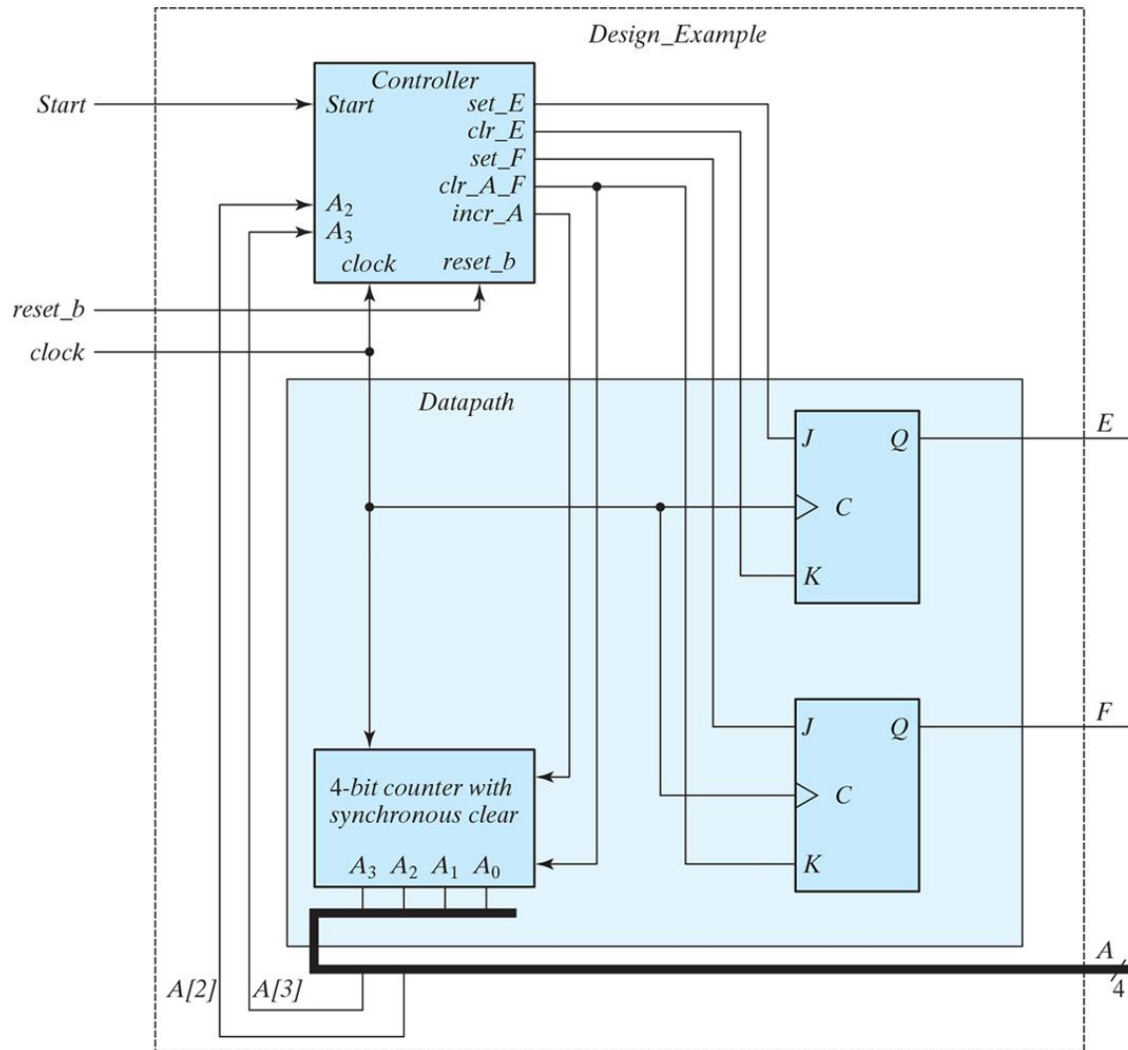


State Diagram from ASMD

 

RTL Description from ASMD

$S_idle \longrightarrow S_1, clr_A_F:$	$A \longleftarrow 0, F \longleftarrow 0$
$S_1 \longrightarrow S_1, incr_A:$	$A \longleftarrow A + 1$
$if (A_2 = 1) \text{ then } set_E:$	$E \longleftarrow 1$
$if (A_2 = 0) \text{ then } clr_E:$	$E \longleftarrow 0$
$S_1 \longrightarrow S_2, incr_A:$	$F \longleftarrow 1$
$S_2 \longrightarrow S_idle:$	$A \longleftarrow A + 1$

 


State Table from ASMD

	Present State		Inputs			Next State		Outputs				
Present-State Symbol	G₁	G₀	Start	A₂	A₃	G₁	G₀	set_E	clr_E	set_F	clr_A_F	incr_A
<i>S_idle</i>	0	0	0	X	X	0	0	0	0	0	0	0
<i>S_idle</i>	0	0	1	X	X	0	1	0	0	0	1	0
<i>S_1</i>	0	1	X	0	X	0	1	0	1	0	0	1
<i>S_1</i>	0	1	X	1	0	0	1	1	0	0	0	1
<i>S_1</i>	0	1	X	1	1	1	1	1	0	0	0	1
<i>S_2</i>	1	1	X	X	X	0	0	0	0	1	0	0


Logic Diagram of the Example

❑ Controller logic diagram

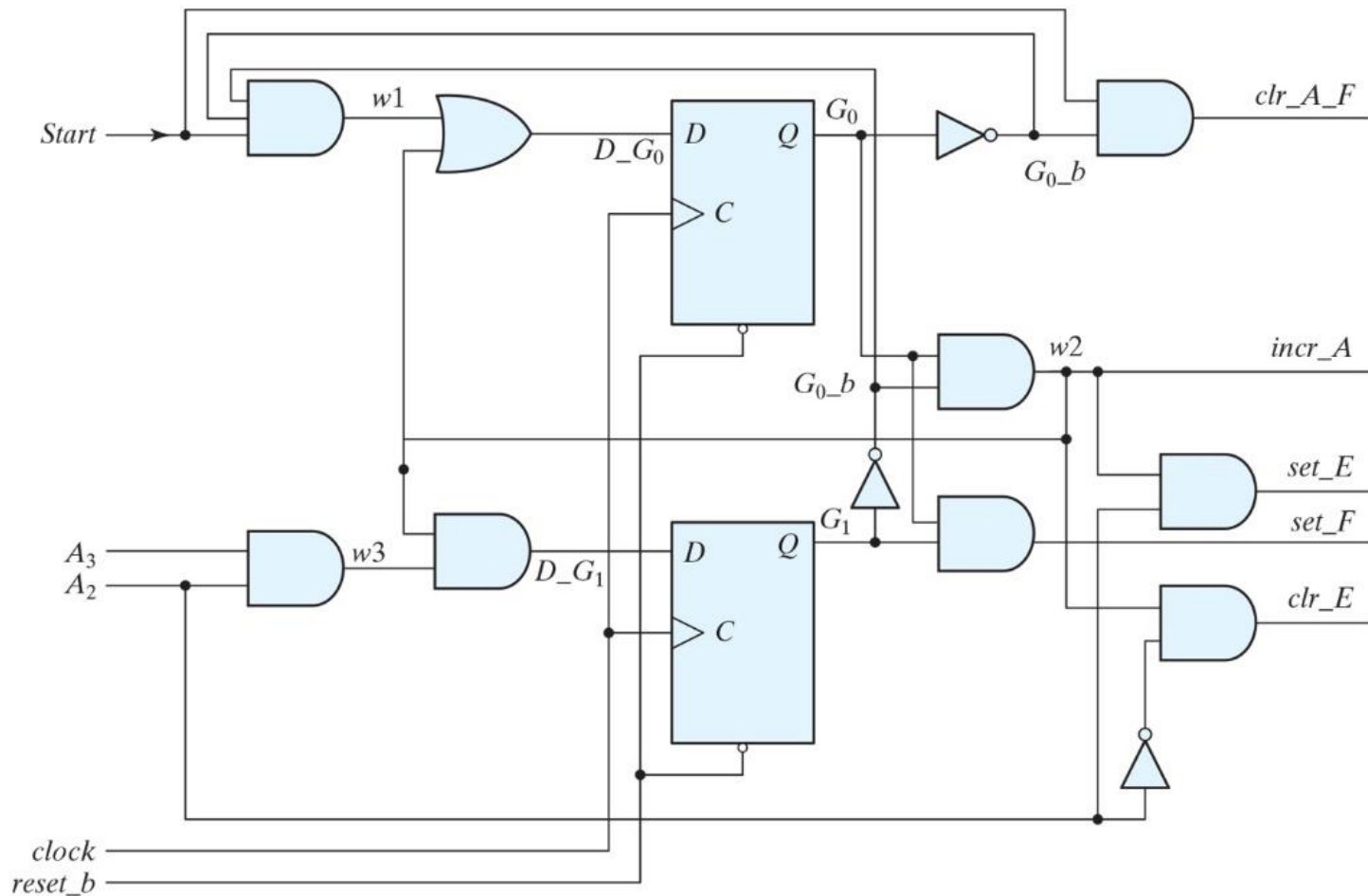

Binary Multiplier

ASMD chart

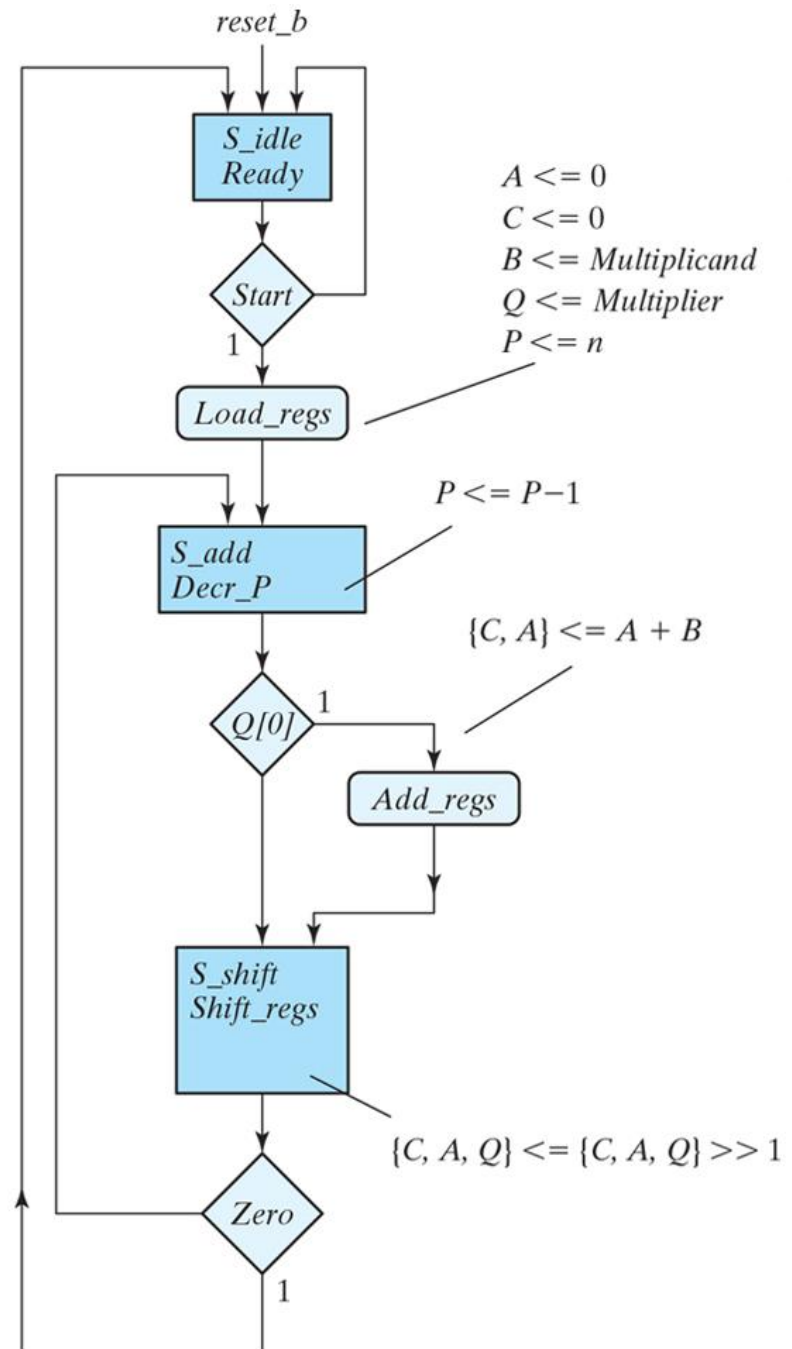


Numerical Examl of Binary Multiplier

Multiplicand $B = 10111_2 = 17_H = 23_{10}$ Multiplier $Q = 10011_2 = 13_H = 19_{10}$

	C	A	Q	P
Multiplier in Q	0	00000	10011	101
$Q_0 = 1$; add B		<u>10111</u>		
First partial product	0	10111		100
Shift right CAQ	0	01011	11001	
$Q_0 = 1$; add B		<u>10111</u>		
Second partial product	1	00010		011
Shift right CAQ	0	10001	01100	
$Q_0 = 0$; shift right CAQ	0	01000	10110	010
$Q_0 = 0$; shift right CAQ	0	00100	01011	001
$Q_0 = 1$; add B		<u>10111</u>		
Fifth partial product	0	11011		
Shift right CAQ	0	01101	10101	000
Final product in $AQ = 0110110101_2 = 1b5_H$				

State Diagram and RTL Description

 

(a)

State Transition		Register Operations
<u>From</u>	<u>To</u>	
<i>S_idle</i>		<i>Initial state</i>
<i>S_idle</i>	<i>S_add</i>	$A \leq 0, C \leq 0, P \leq dp_width$ $A \leq \text{Multiplicand}, Q \leq \text{Multiplier}$
<i>S_add</i>	<i>S_shift</i>	$P \leq P - 1$ if ($Q[0]$) then ($A \leq A + B, C \leq C_{out}$)
<i>S_shift</i>		shift right {CAQ}, $C \leq 0$

(b)




State Assignment for Control

State	Binary	Gray Code	One-Hot
<i>S_idle</i>	00	00	001
<i>S_add</i>	01	01	010
<i>S_shift</i>	10	11	100


State Table for Control Circuit

	Present State		Inputs			Next State		Outputs				
Present-State Symbol	G ₁	G ₀	Start	Q[0]	Zero	G ₁	G ₀	Ready	Load_regs	Decr_P	Add_regs	Shift_regs
<i>S_idle</i>	0	0	0	X	X	0	0	1	0	0	0	0
<i>S_idle</i>	0	0	1	X	X	0	1	1	1	0	0	0
<i>S_add</i>	0	1	X	0	X	1	0	0	0	1	0	0
<i>S_add</i>	0	1	X	1	X	1	0	0	0	1	1	0
<i>S_shift</i>	1	0	X	X	0	0	1	0	0	0	0	1
<i>S_shift</i>	1	0	X	X	1	0	0	0	0	0	0	1


Block Diagram

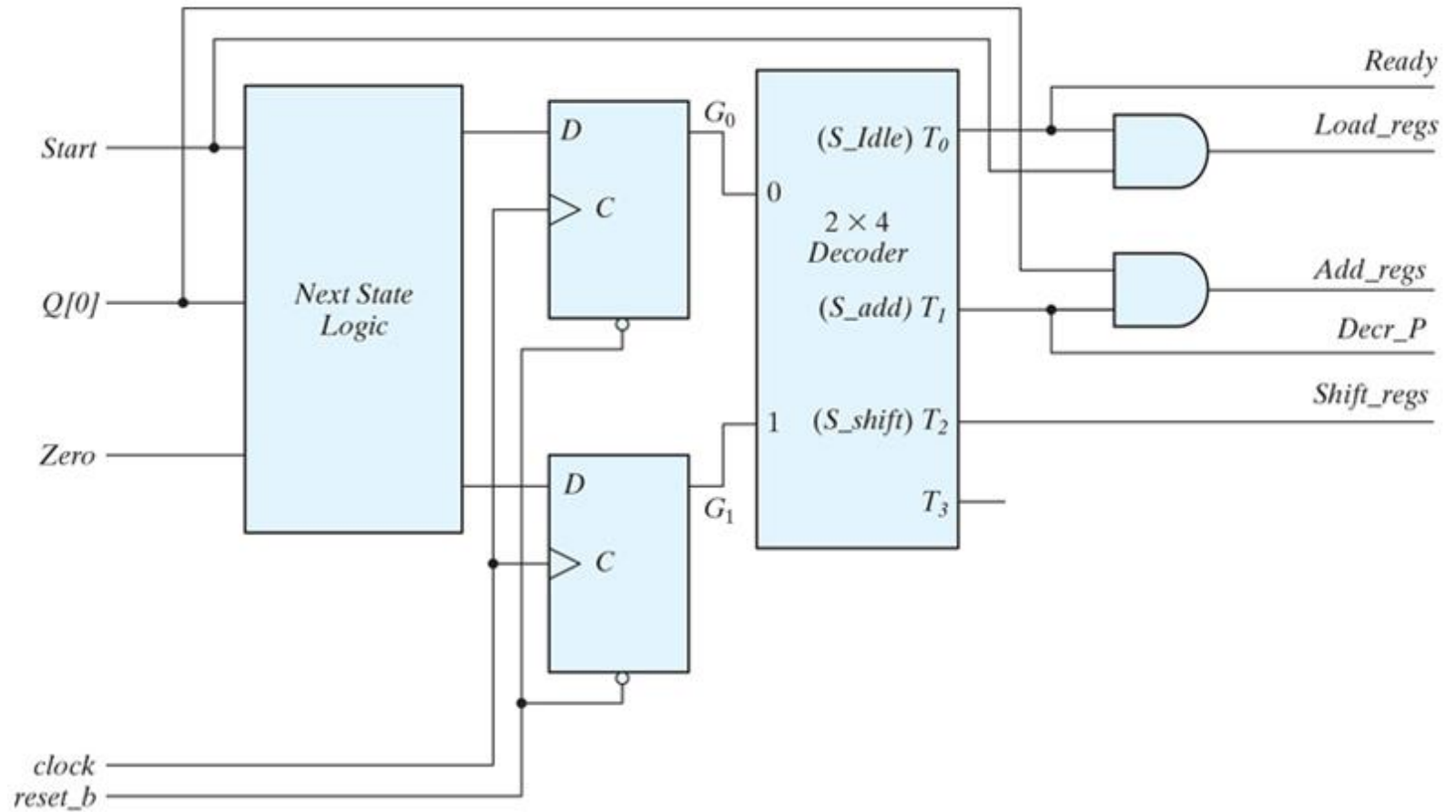



Logic Diagram

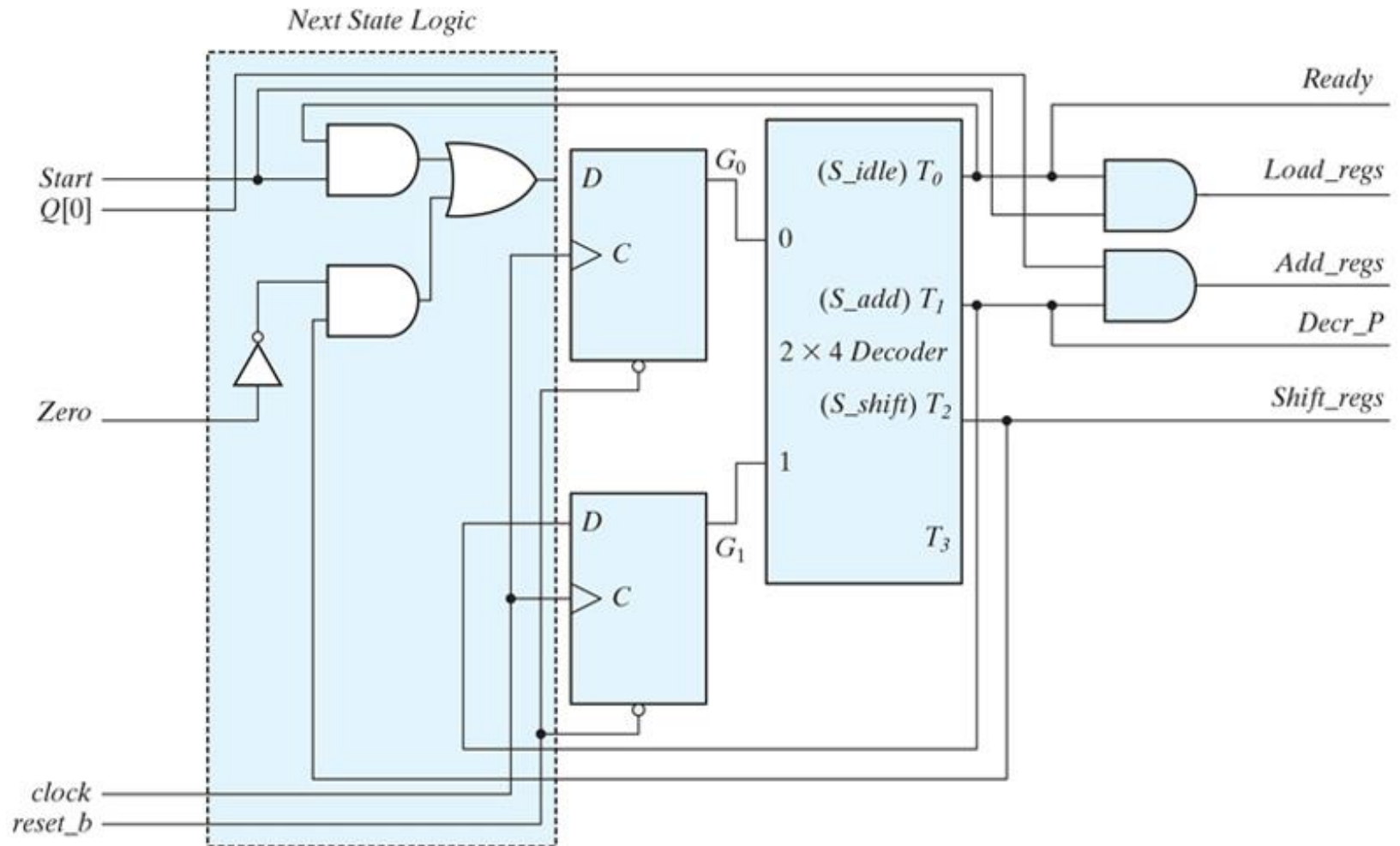


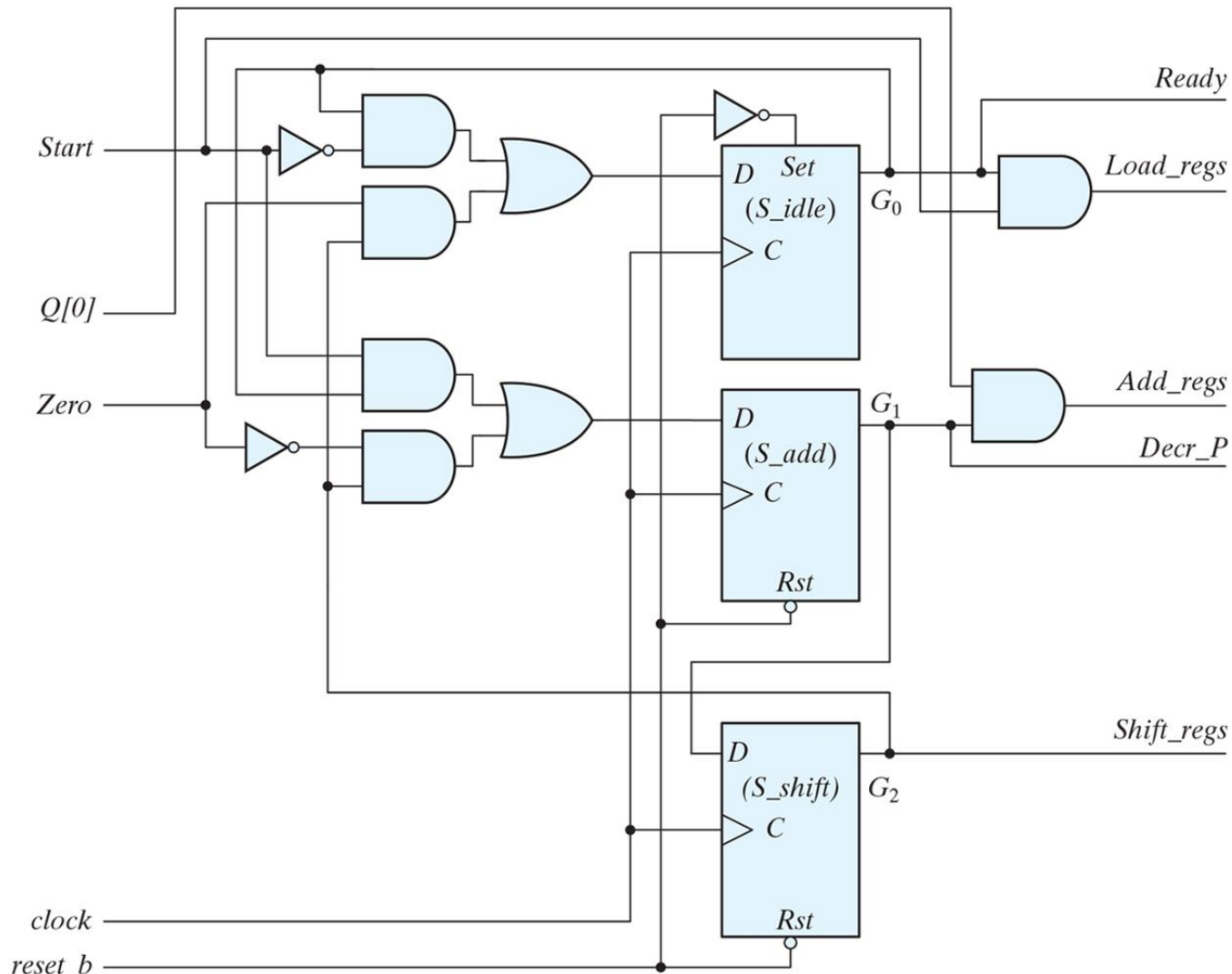
Logic Diagram for One-hot State Controller




 


 


 


 


 


 


 


 


 


 


 


 


 

 

 

 

 



Discussion ~ ~ ~