

# Big Picture

- ❑ Issue 1: Fundamental concepts and principles
  - What is computer, CSE, computer architecture?
- ❑ Issue 2: ISA (HW-SW interface) design
  - Ch. 1: computer performance
  - Ch. 2: language of computer; ISA
  - Ch. 3: data representation and ALU
- ❑ Issue 3: implementation of ISA (internal design)
  - Ch. 4: processor (data path, control, pipelining)
  - Ch. 5: memory system (cache memory)
- ❑ Short introduction to parallel processors

# Big Picture

## ❑ Part 3: implementation of ISA

“Given ISA, what is a good implementation?”

- Ch. 4: processor
    - Simplified version (fetch-decode-execution)
    - Pipelined version
  - Ch 5: memory system design
    - Cache memory (part of processor)
- ❖ 기능이 아니라 성능 (efficient implementation)

# Class Topics (클래스 홈페이지 참조)

- ❑ Part 1: Fundamental concepts and principles
- ❑ Part 2: 빠른 컴퓨터를 위한 ISA design
  - Topic 1 Computer performance and ISA design (Ch. 1)
  - Topic 2 RISC (MIPS) instruction set (Chapter 2)
  - Topic 3 Computer arithmetic and ALU (Chapter 3)
- ❑ Part 3: ISA 의 효율적인 구현 (pipelining, cache memory)
  - Topic 4 Processor design (Chapter 4)
    - Single cycle implementation
    - Pipelined implementation
  - Topic 5 Memory system design (Chapter 5)

## **Chapter 4**

### **The Processor (Implementing ISA)**

#### **Part 1: Single Cycle Design**

Some of authors' slides are modified

# Introduction

- ❑ High-level organization (and low-level circuits design)
  - Determine CPI (and clock cycle time)
    - ISA determines IC (and affect CPI and clock cycle)
- ❑ We will examine two MIPS implementations
  - Single cycle implementation
  - Multi-cycle implementation (concept only)
  - Pipelined implementation
- ❑ Datapath and control (VLSI chip design)

# Introduction

- ❑ Simple subset, shows most aspects
  - Memory-reference: **lw, sw**
  - Arithmetic-logical: **add, sub, and, or, slt**
  - Control transfer: **beq, j**
- ❑ Generic Implementation: repeat the following
  - Instruction fetch (IF) // 공통
  - Instruction decode (ID) // 공통
    - Use the instruction to decide exactly what to do
  - Instruction execute (EX)


# Instruction Execution (미리보기)

- ❑ **Fetch instruction:**  $PC \rightarrow \text{instruction memory}, PC \leftarrow PC + 4$
- ❑ **Decode instruction (opcode)**
  - Register numbers  $\rightarrow$  register file, read registers (?)
- ❑ **Execute instruction:** depend on instruction class
  - Use ALU to calculate
    - Arithmetic result
    - Memory address for load/store
    - Branch target address
  - Access data memory for load/store
  - $PC \leftarrow \text{target address or } PC + 4$

# MIPS CPU Overview




# CPU Overview (Schematic)

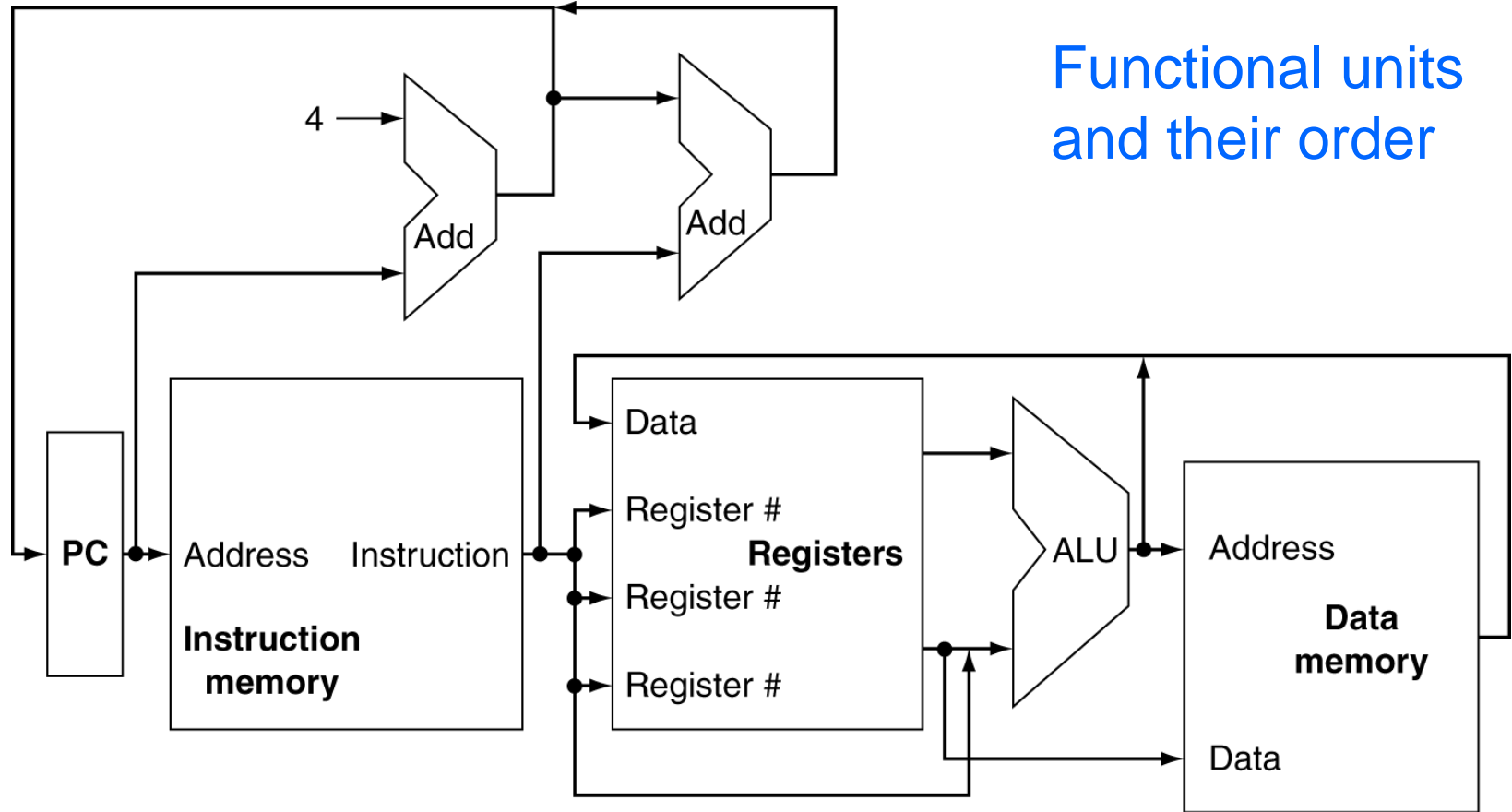

# CPU Overview

| op | rs | rt | rd | shamt | funct |
|----|----|----|----|-------|-------|
|----|----|----|----|-------|-------|


add \$t0, \$t1, \$t2 // R-type

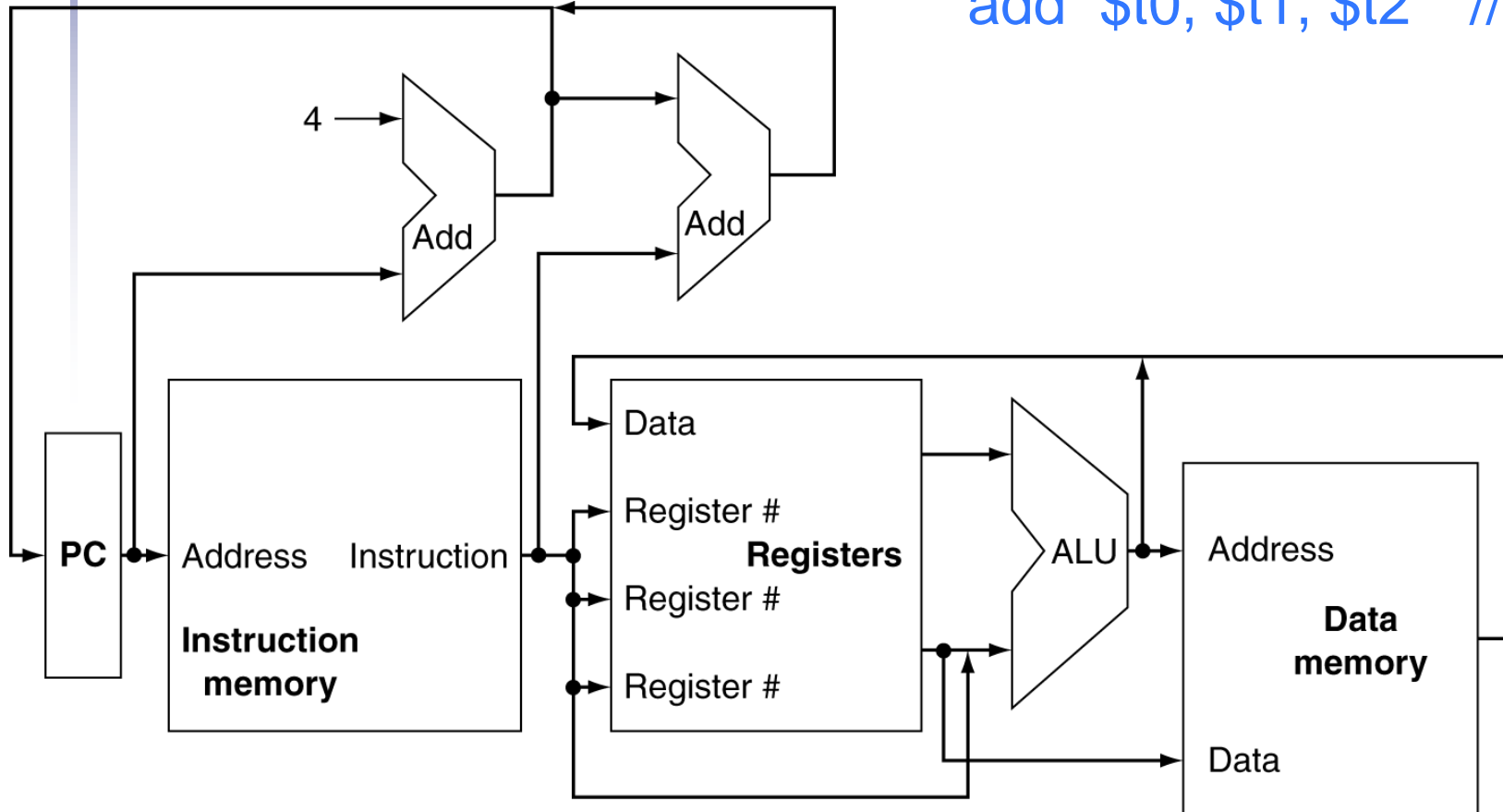

# CPU Overview

| op | rs | rt | 16 bit address |
|----|----|----|----------------|
|----|----|----|----------------|

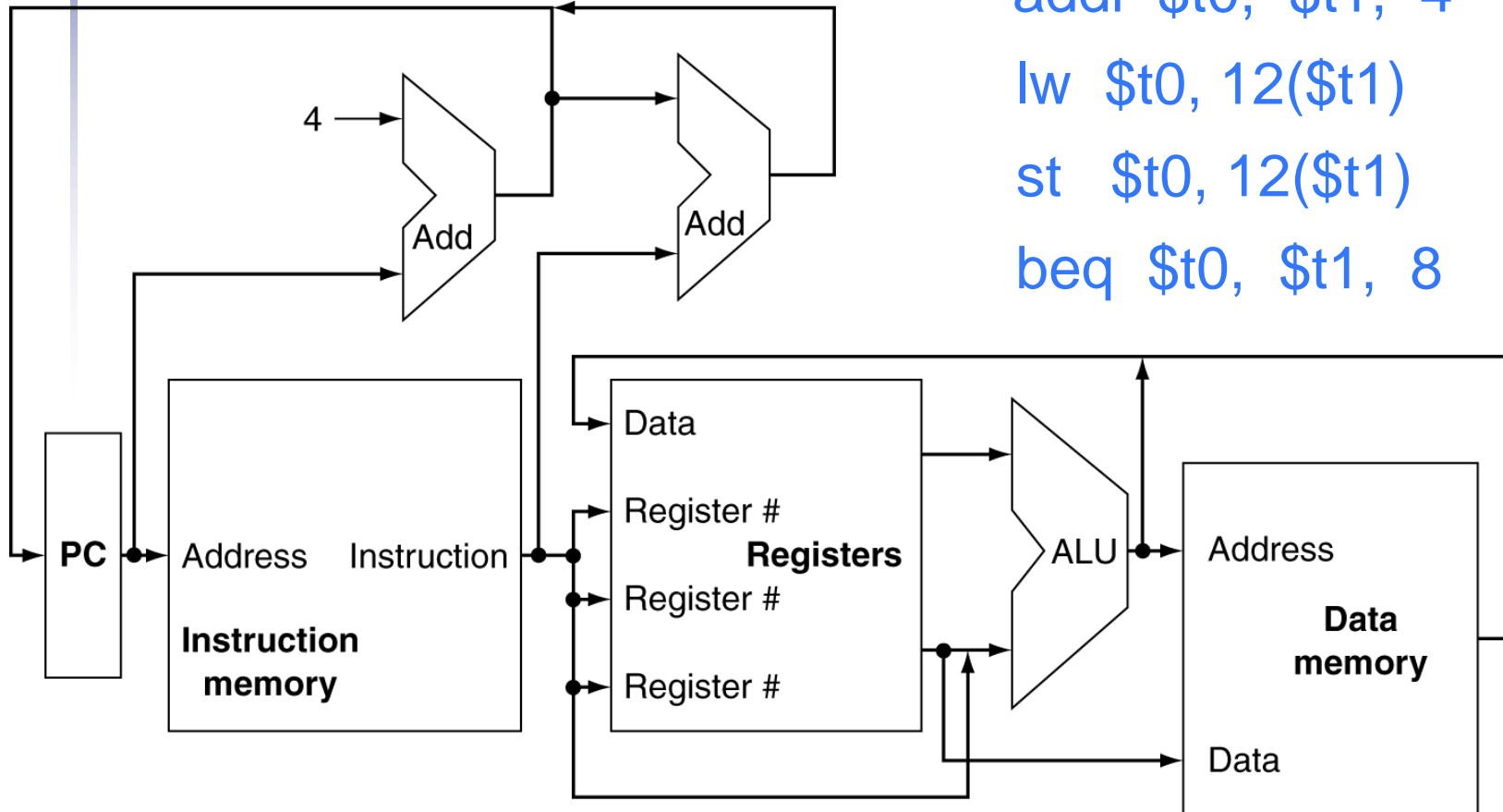addi \$t0, \$t1, 4 // I-type  
lw \$t0, 12(\$t1)  
st \$t0, 12(\$t1)  
beq \$t0, \$t1, 8



# Executing MIPS Instructions (부연)

## ❑ ALU

add \$t0, \$t1, \$t2 // R-type

addi \$t0, \$t1, 4 // I-type

## ❑ Data transfer

lw \$t0, 12(\$t1) // I-type


st \$t0, 12(\$t1)

## ❑ Branch

beq \$t0, \$t1, 8 // I-type

|   |    |                |    |               |       |       |
|---|----|----------------|----|---------------|-------|-------|
| R | op | rs             | rt | rd            | shamt | funct |
| I | op | rs             | rt | 16 bit offset |       |       |
| J | op | 26 bit address |    |               |       |       |

# High-Level Implementation (Schematic)

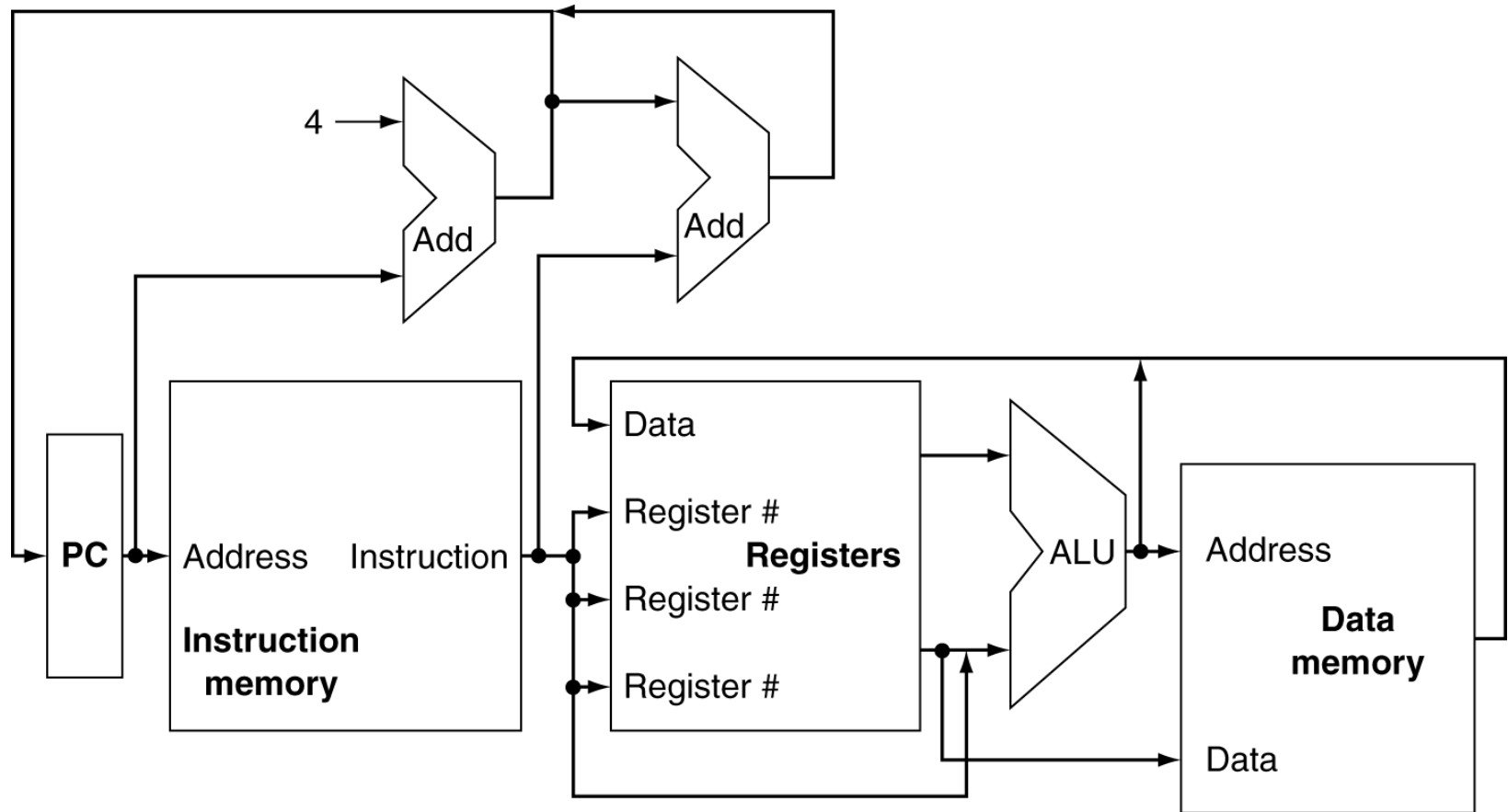


- ❑ Does this look familiar? (It's just ISA)
- ❑ ISA determines functional units and their order

# Instruction Decode

- ❑ Where is it in the datapath?
  - Not shown (will come back to it)

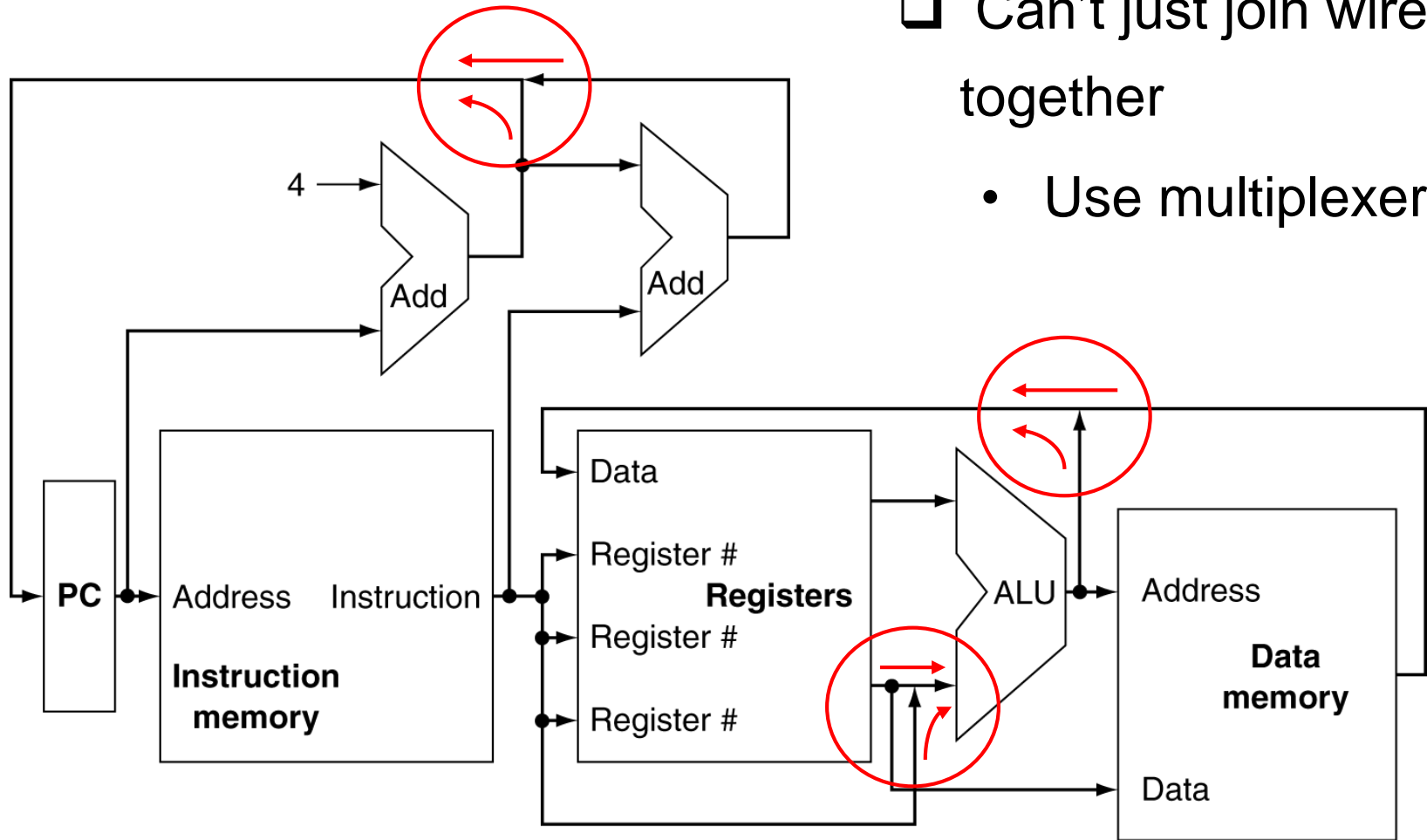
# Multiplexers

- ❑ Can't just join wires together
  - Use multiplexers



# Full Datapath (미리보기)



colored  
select  
signals

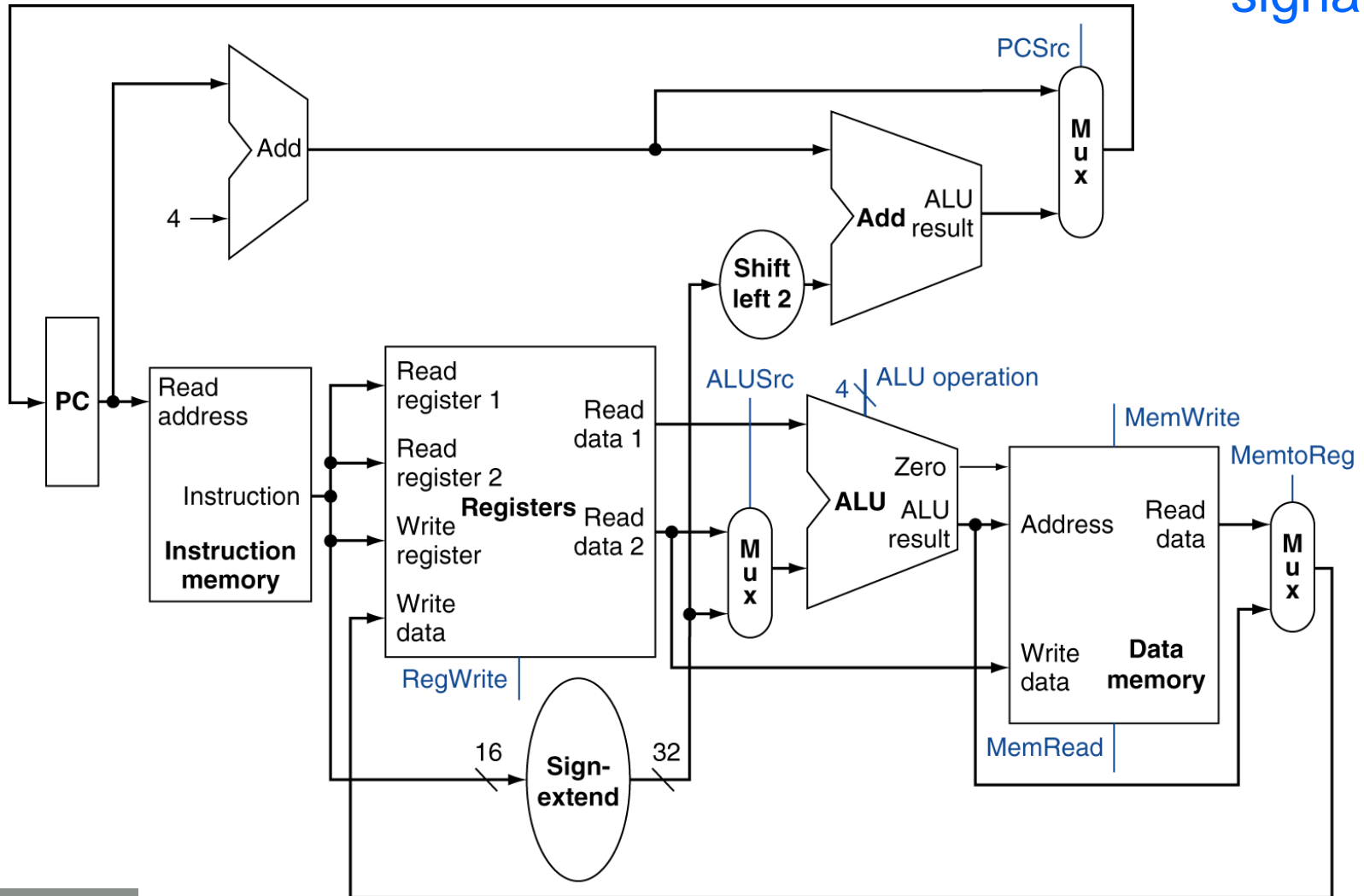





# Multiplexers (복습)

- ❑ 2-to-1 MUX, 4-to-1 MUX

  

# Multiplexers (복습)

- 32 of 2-to-1 mux

  


# Digital Logic Design (복습)

- ❑ Given: AND, OR, NOT
- ❑ Design
  - Combinational logic circuits
    - Decoders, mux, ..., ALUs
  - Sequential logic circuits
    - Latches, flip-flops, registers, counters, ..., CPUs
- ❑ Notion of abstraction
- ❑ VLSI 개발 환경 (비교: software 개발 환경)

# Synchronous Sequential Logic (복습)


- Meaning of single cycle implementation

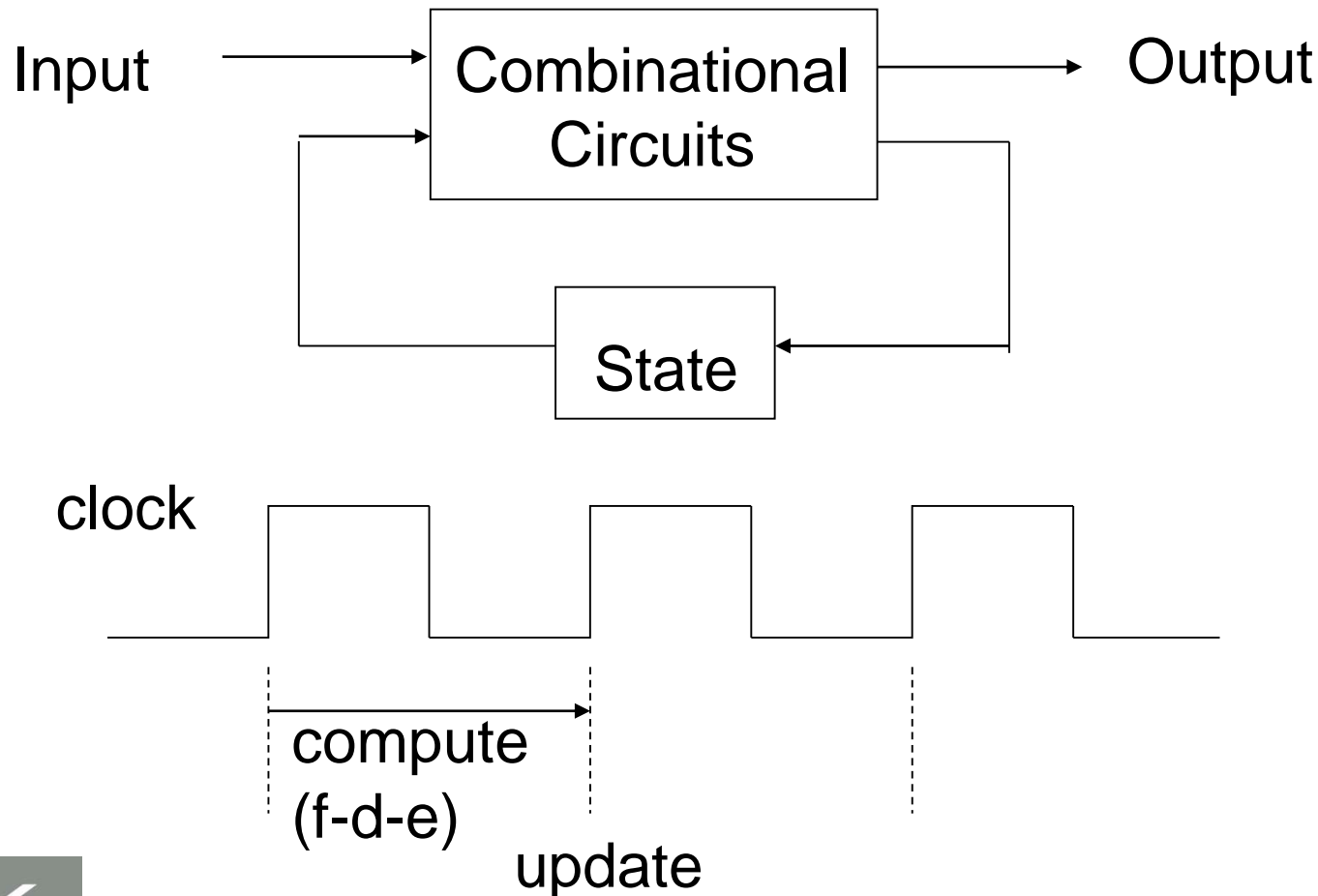

# CPU: Synchronous Sequential Logic


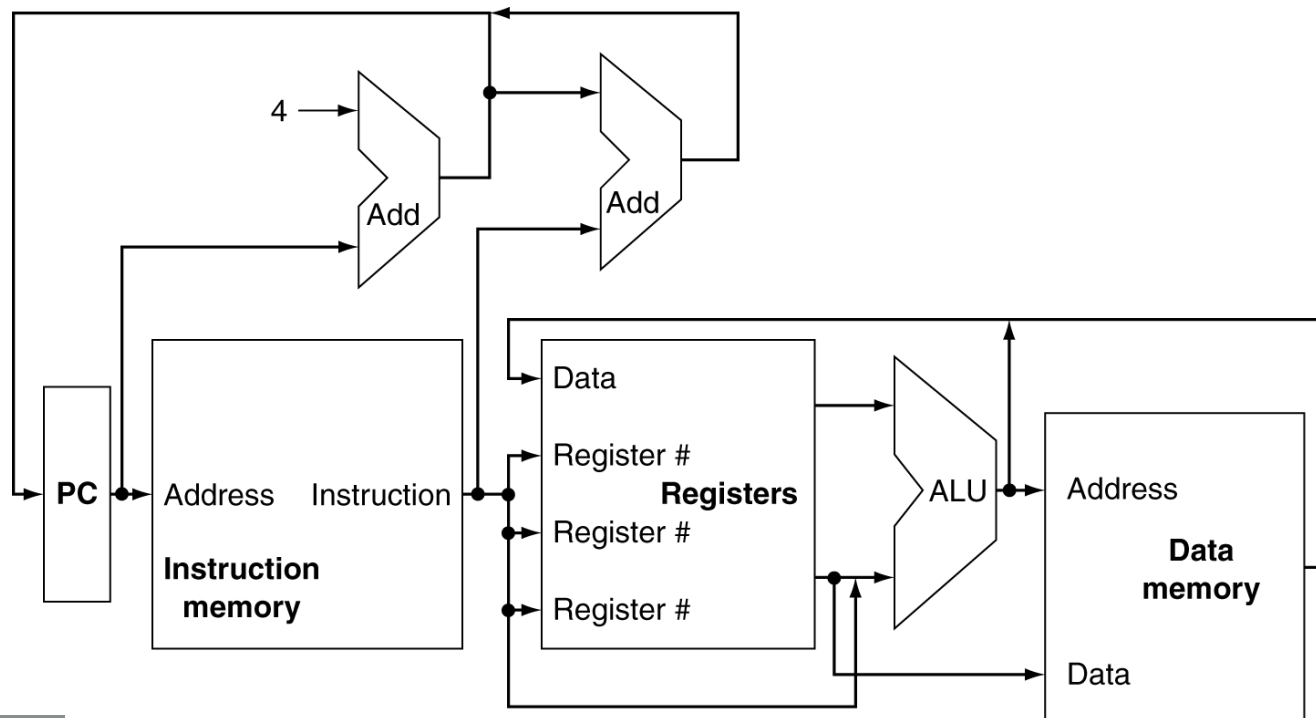
## ❑ What are the states?

- Result of “fetch-decode-execute” updated at the end of each clock cycle


  
# CPU: Providing Input at High Speed


- ❑ 1GHz (light speed); use PC to get new input by itself



**Let's Build a Datapath**  
which can execute MIPS instructions,  
  
using smaller building blocks

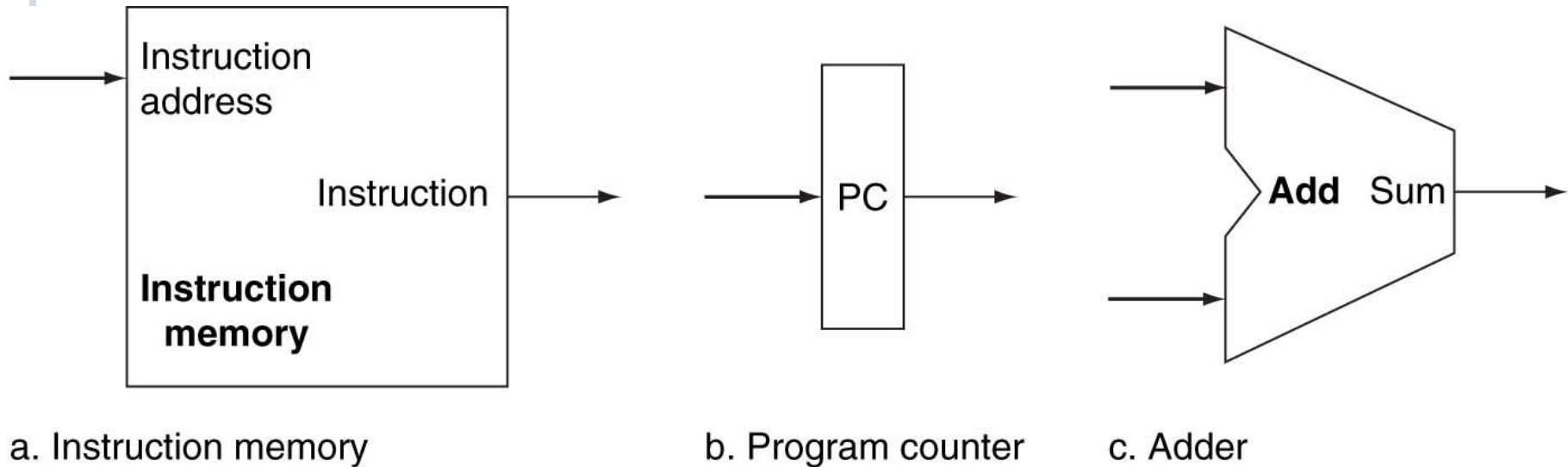
# Building Blocks for IF (1)

- ❑ Functional units (abstractions) we need for each instruction






# Instruction Memory

 


- ❑ 여기서는 프로그램이 고정되었다고 생각 (read only)
  - 변경 원하면, write 기능 추가
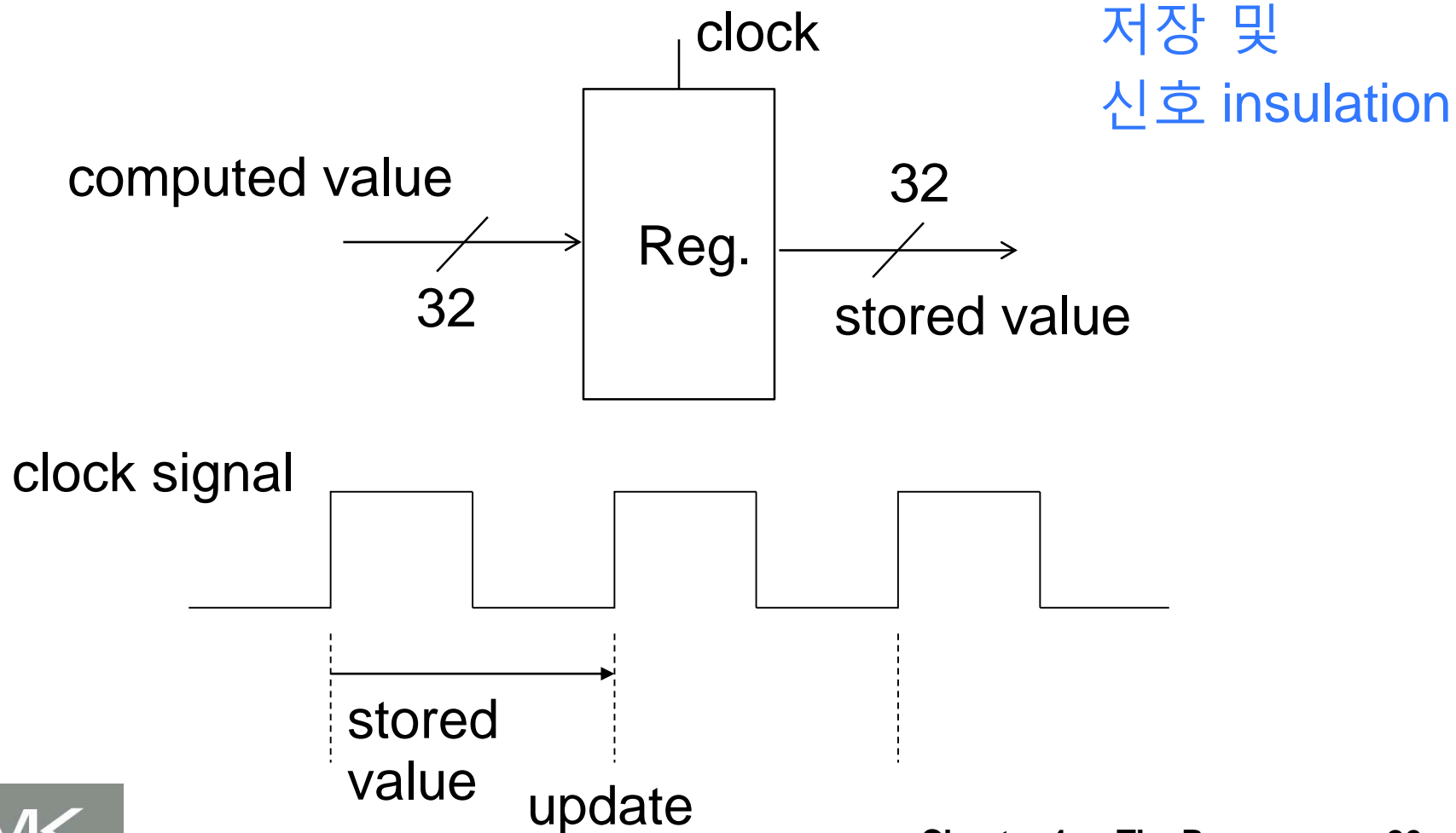
# Registers (including PC)

- ❑ Sequential blocks, has states, in sync with clock




# Instruction Fetch

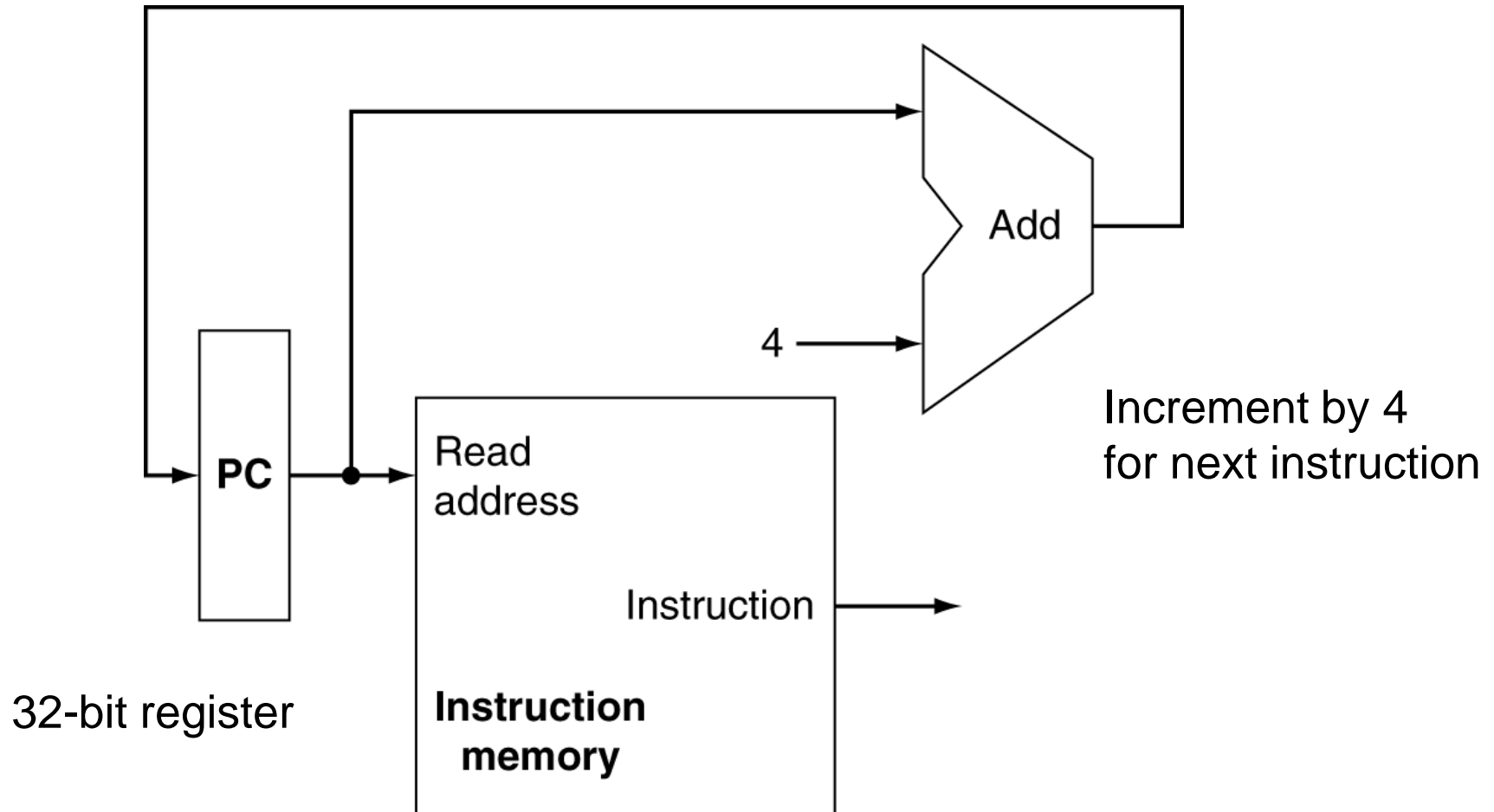


□ 모든 instruction 에 공통
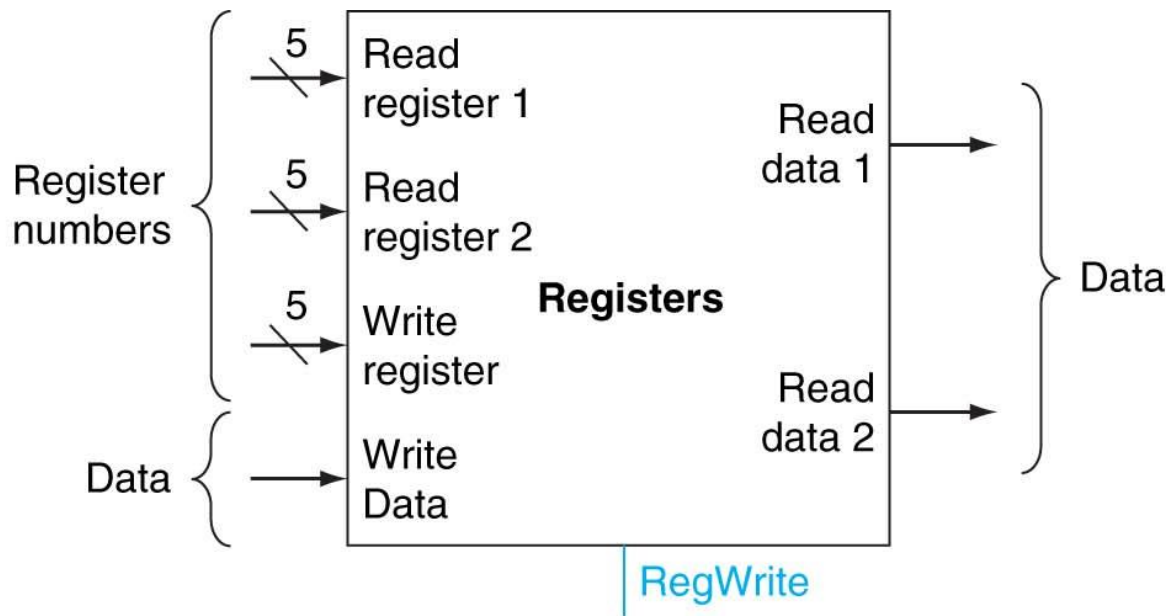
# Building Blocks for R-Type (2)

- Functional units (abstractions) we need for each instruction



a. Registers

 

b. ALU

add \$3, \$1, \$2

- (colored) select/enable signals – how to determine?



# Register File

32-to-1 mux  
(5-bit register no.)

## ❑ Register read

add \$3, \$1, \$2

beq \$1, \$2, 8

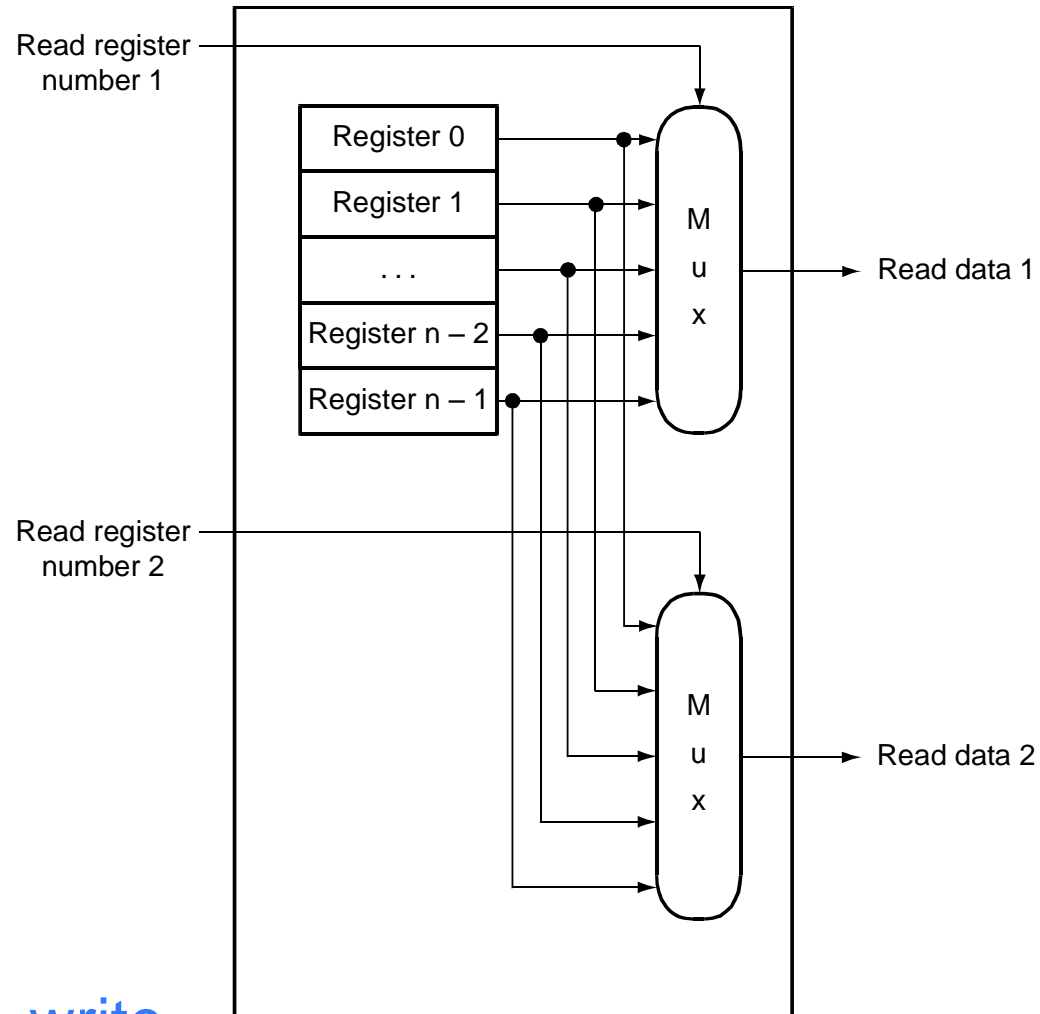 

2 reads and 1 write


# Register File

5-to-32 decoder  
(5-bit register no.),  
only 1 of 32 outputs: “1”

## ❑ Register write

add \$3, \$1, \$2


lw \$3, 8(\$2)

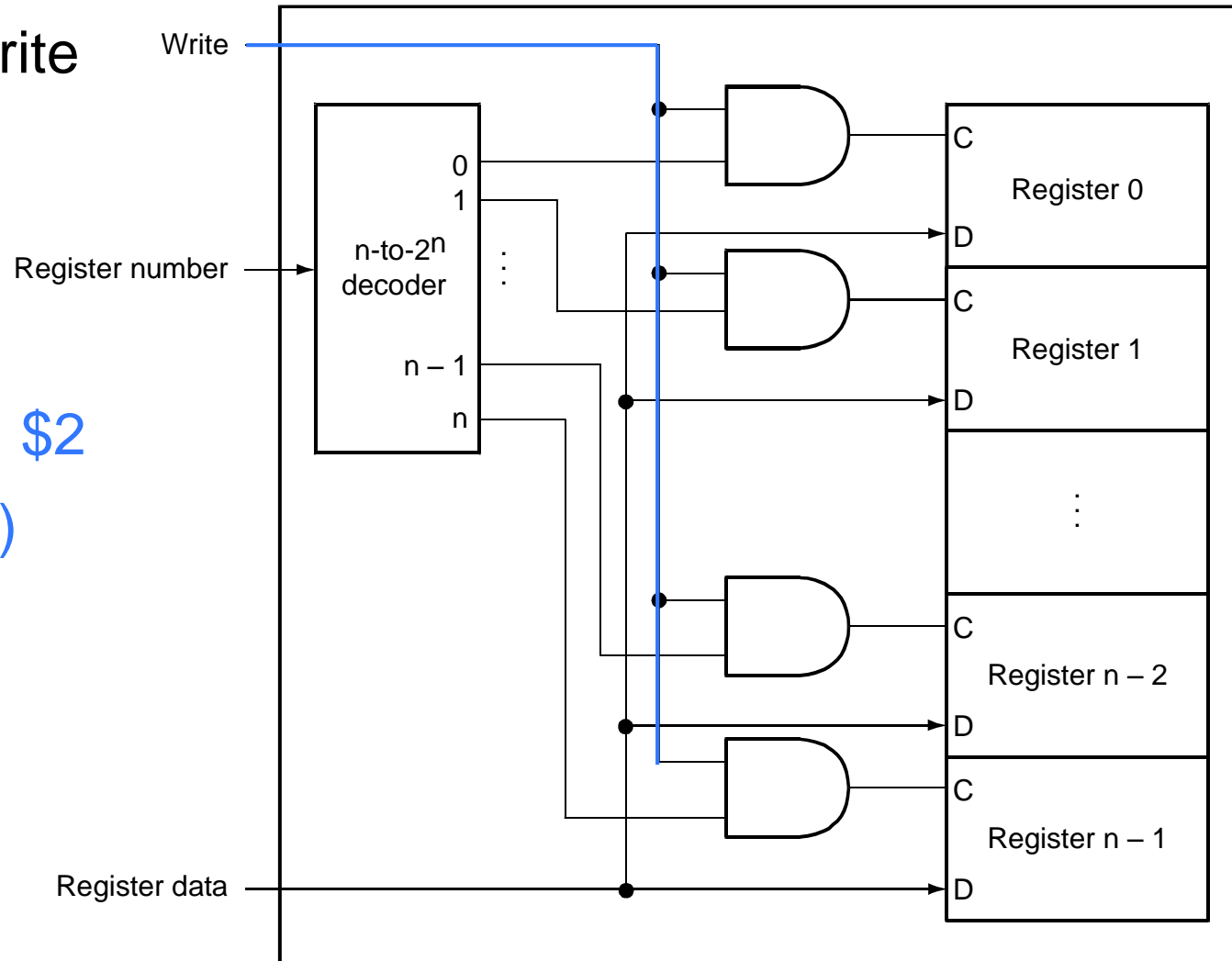

# 3-to-8 Decoder (복습)

| $A_2$ | $A_1$ | $A_0$ | $D_7$ | $D_6$ | $D_5$ | $D_4$ | $D_3$ | $D_2$ | $D_1$ | $D_0$ |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 1     |
| 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 0     |
| 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 0     |
| 0     | 1     | 1     | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 0     |
| 1     | 0     | 0     | 0     | 0     | 0     | 1     | 0     | 0     | 0     | 0     |
| 1     | 0     | 1     | 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0     |
| 1     | 1     | 0     | 0     | 1     | 0     | 0     | 0     | 0     | 0     | 0     |
| 1     | 1     | 1     | 1     | 0     | 0     | 0     | 0     | 0     | 0     | 0     |

3-to-8  
decoder

 


□ 5-to-32 decoder, 2-to-4 decoder, ...
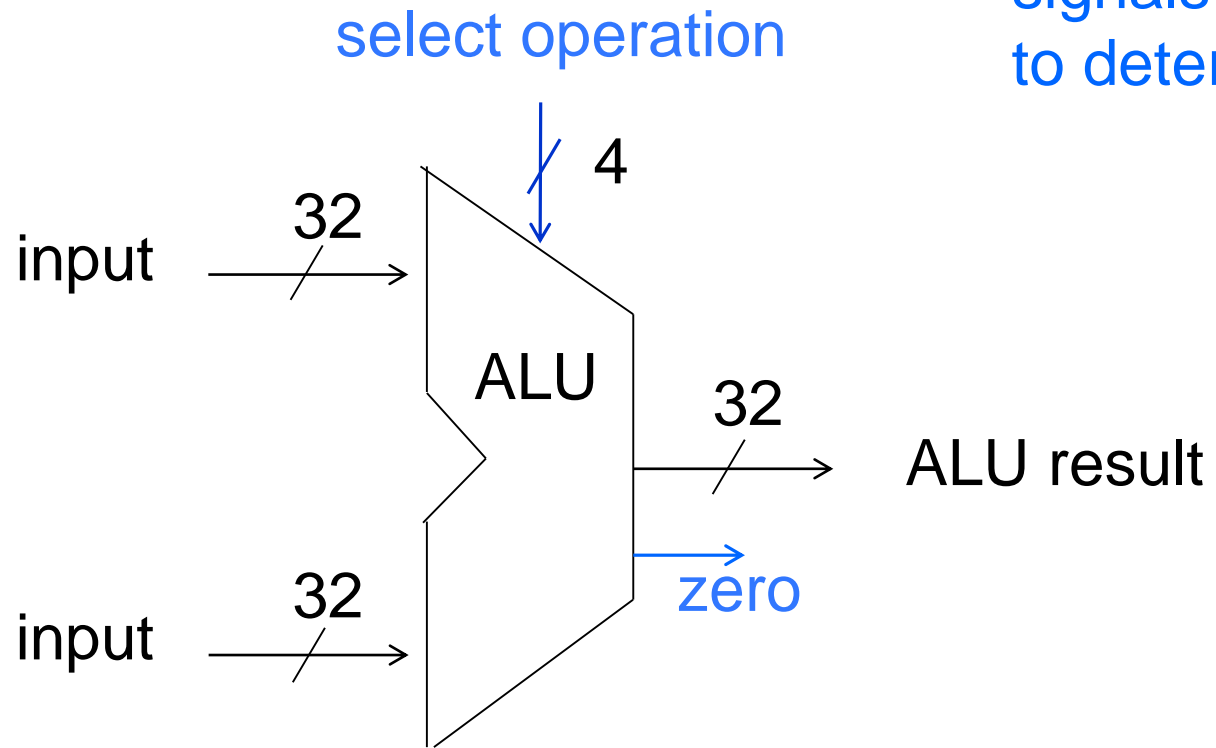
# ALU

- ❑ Combinational blocks, no states

colored select signals (how to determine?)







# R-Format Instructions

- ❑ Read two register operands
- ❑ Perform arithmetic/logical operation
- ❑ Write register result

add \$3, \$1, \$2

 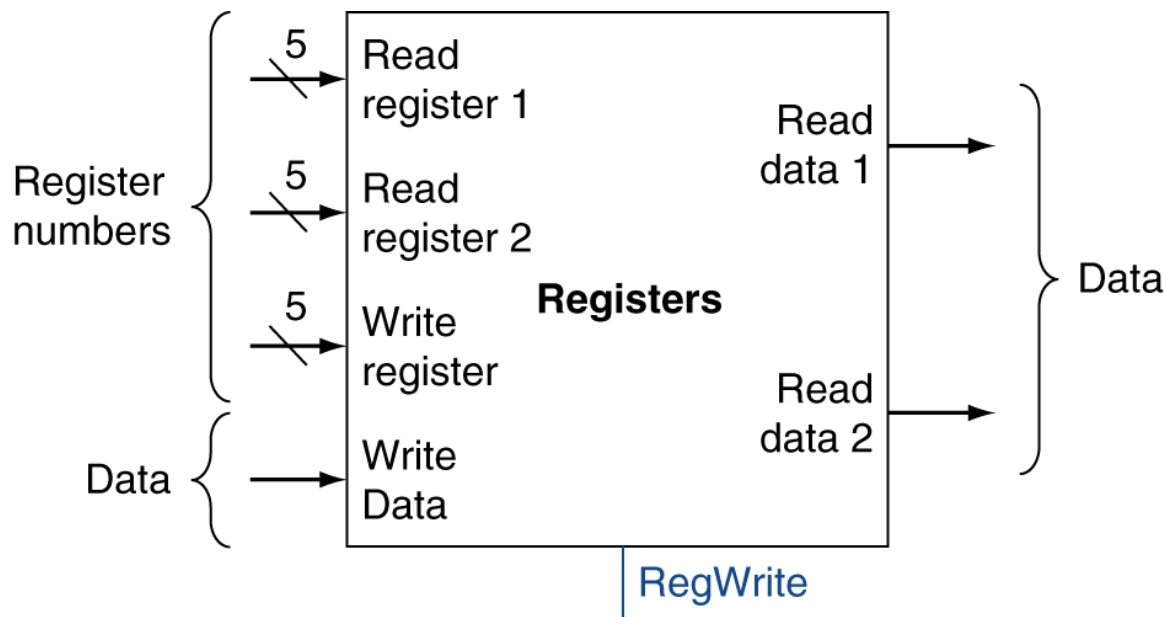


a. Registers


b. ALU
 
# Building Blocks for “lw/sw” (3)

- Functional units (abstractions) we need for each instruction




a. Data memory unit

 

b. Sign extension unit
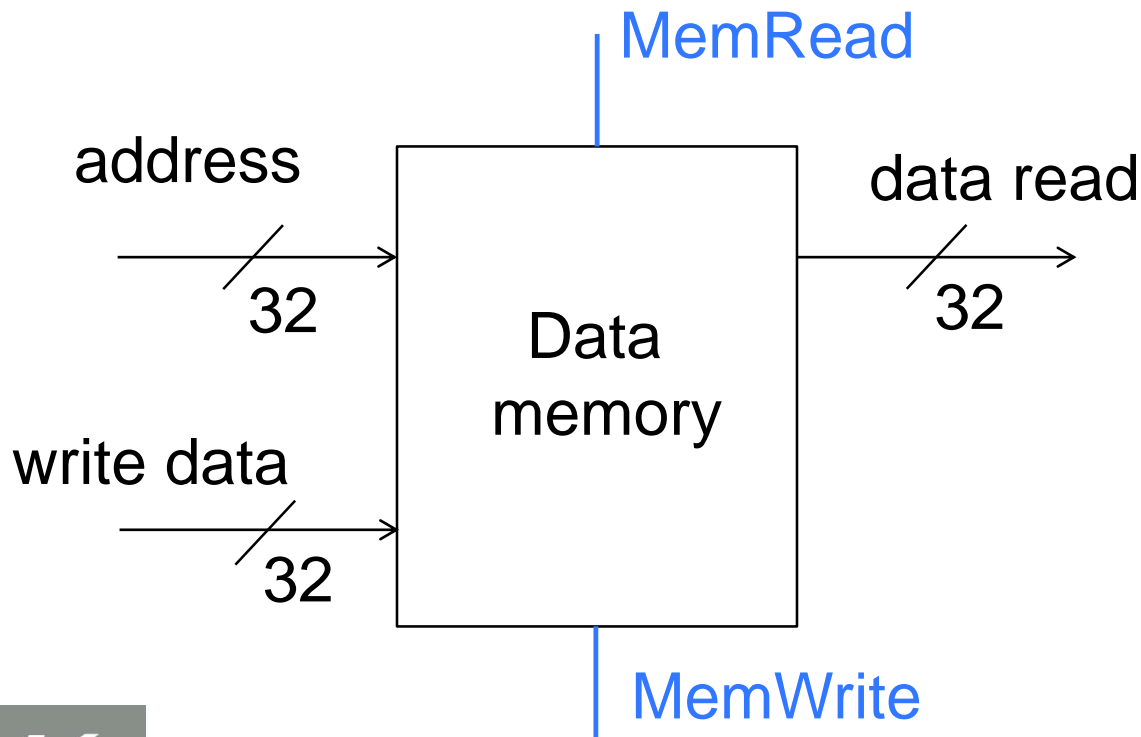
# Data Memory


- ❑ Memory read (**MemRead** = 1) // load
- ❑ Memory write (**MemWrite** = 1) // store




Colored enable signals (how to determine?)
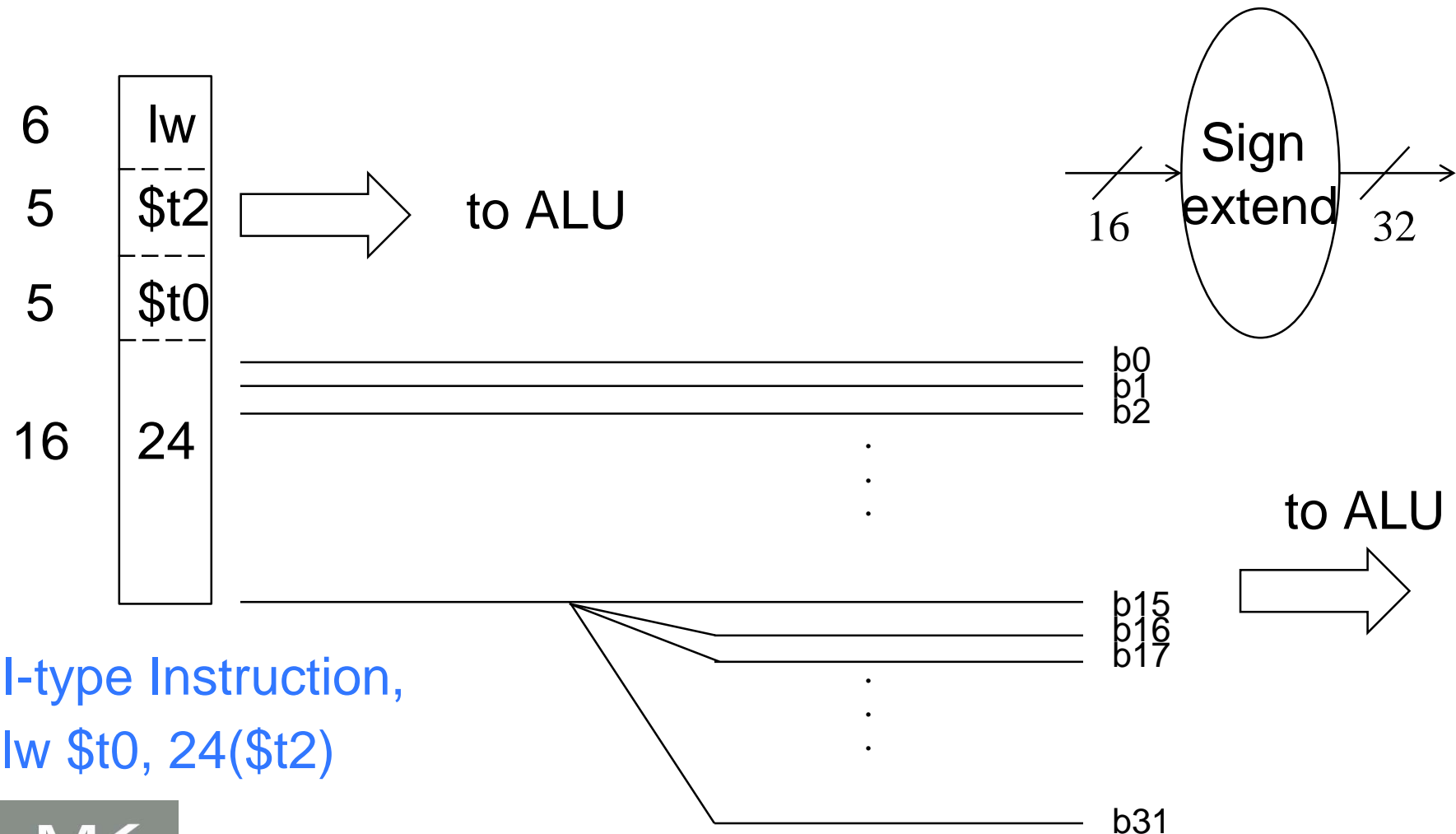
# Sign Extension

- ❑ 16-bit immediate extended to 32-bit before ALU operation



# Load/Store Instructions

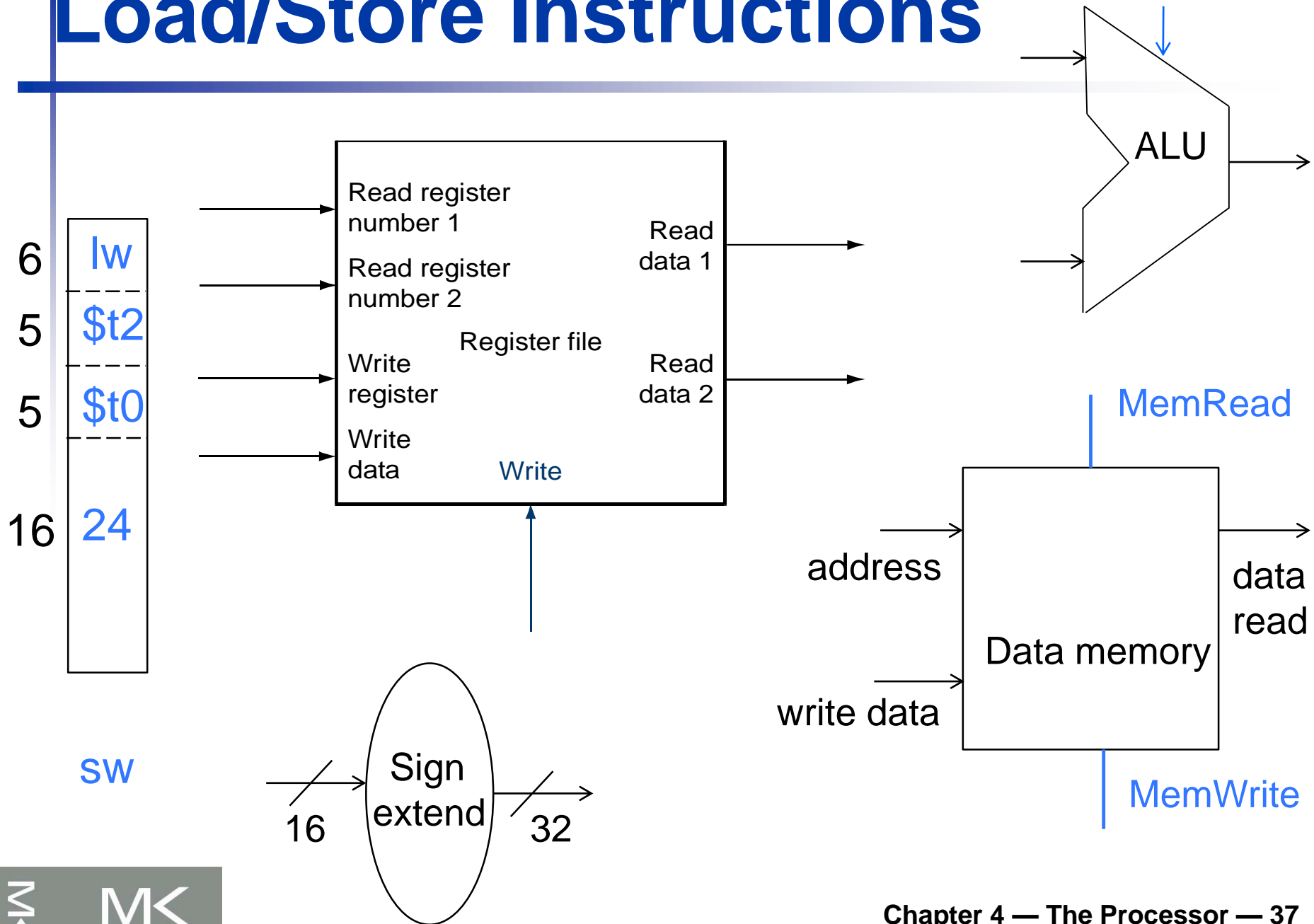


# Load/Store Instructions (부연)

- ❑ Read register operands
- ❑ Calculate address using 16-bit offset
  - Use ALU, but sign-extend offset
- ❑ Load: Read memory and update register
- ❑ Store: Write register value to memory

# Branch Instructions

beq \$t1, \$t2, 8

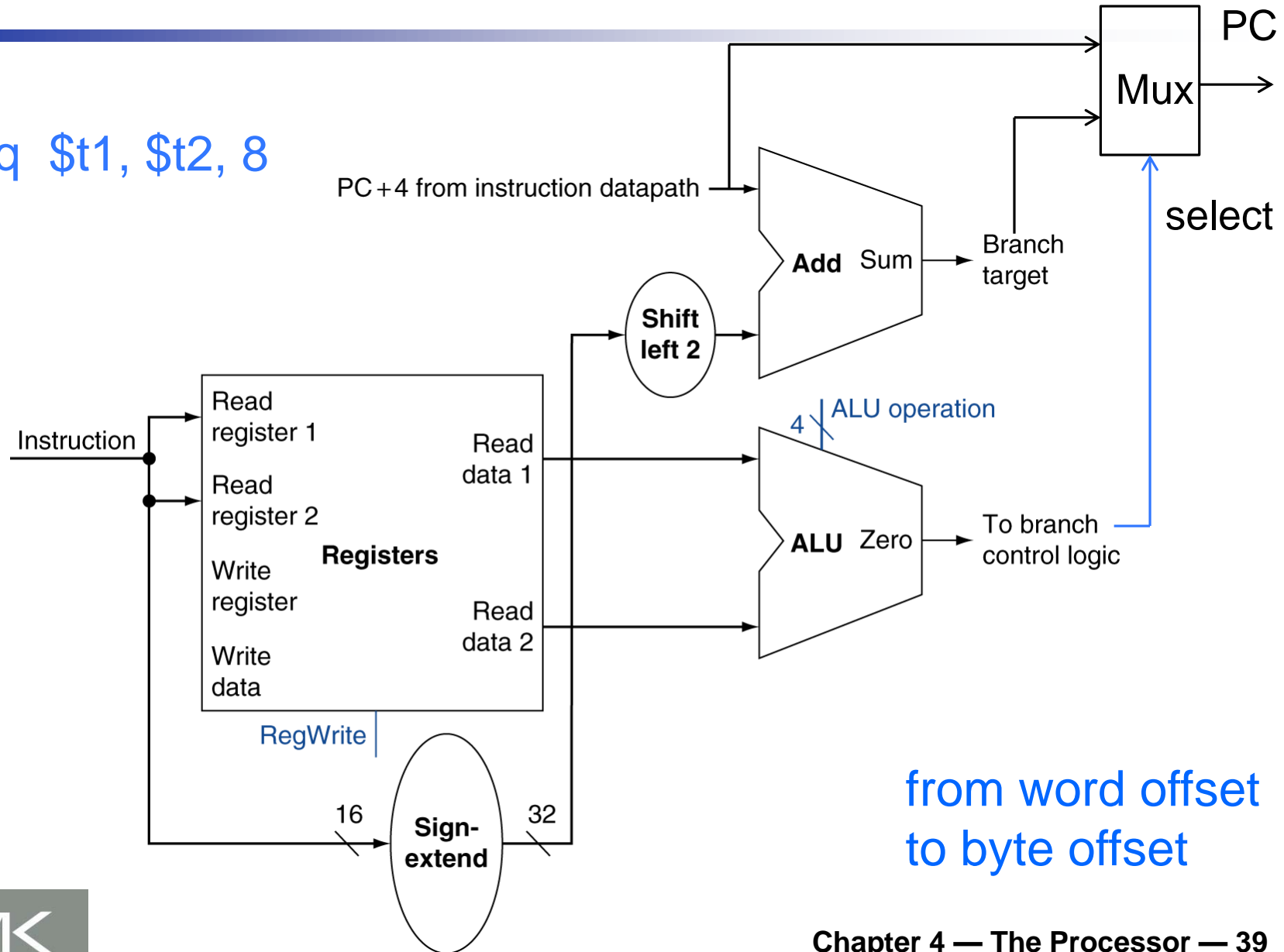


# Branch Instructions (부연)

- ❑ Read register operands
- ❑ Compare operands
  - Use ALU, subtract and check Zero output
- ❑ Calculate target address
  - Sign-extend displacement
  - Shift left 2 places (word displacement)
  - Add to PC + 4



# Full Datapath


# CPU Overview (반복)

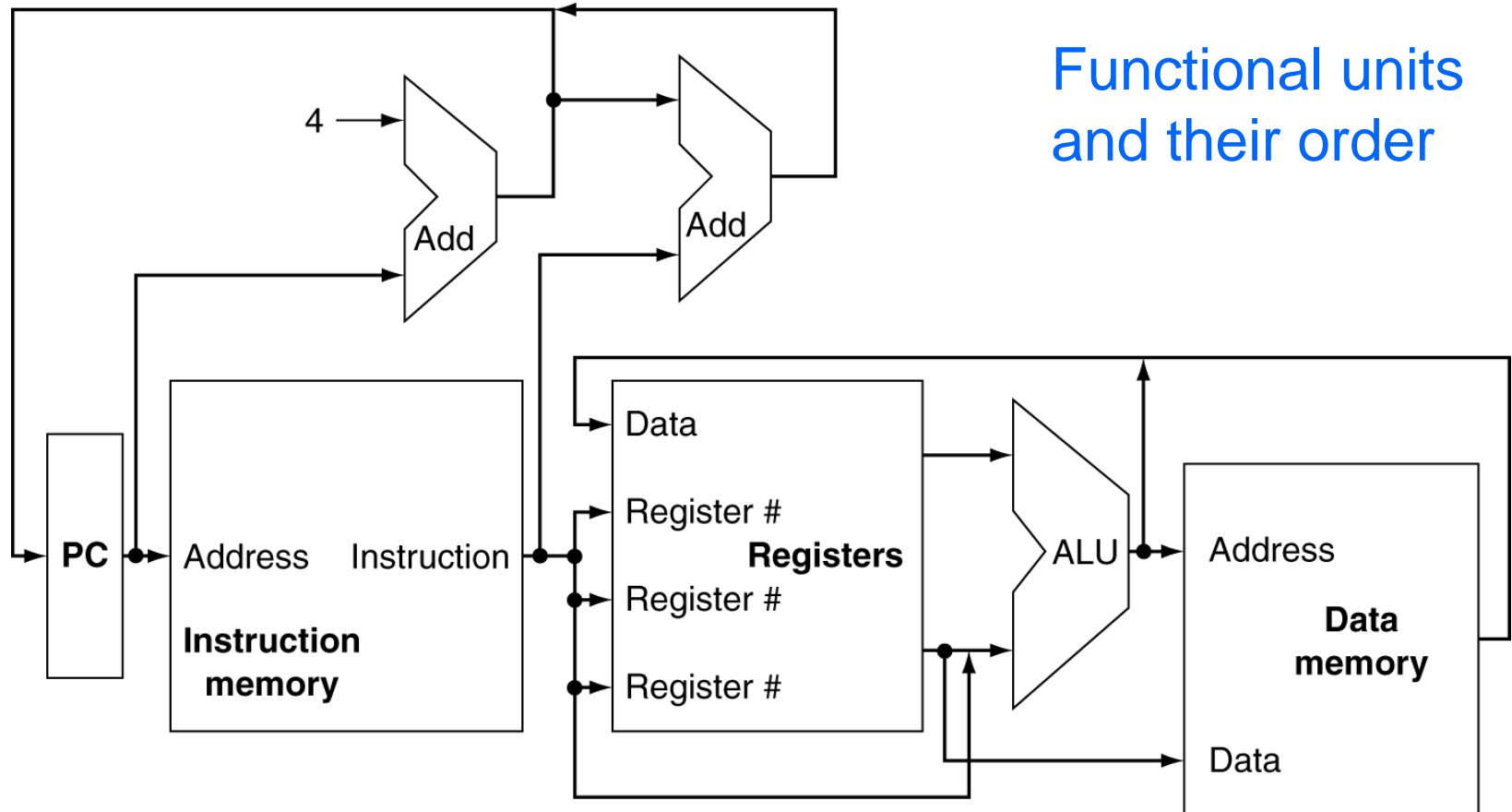

# Full Datapath

add \$t0, \$t1, \$t2


addi \$t0, \$t1, 4

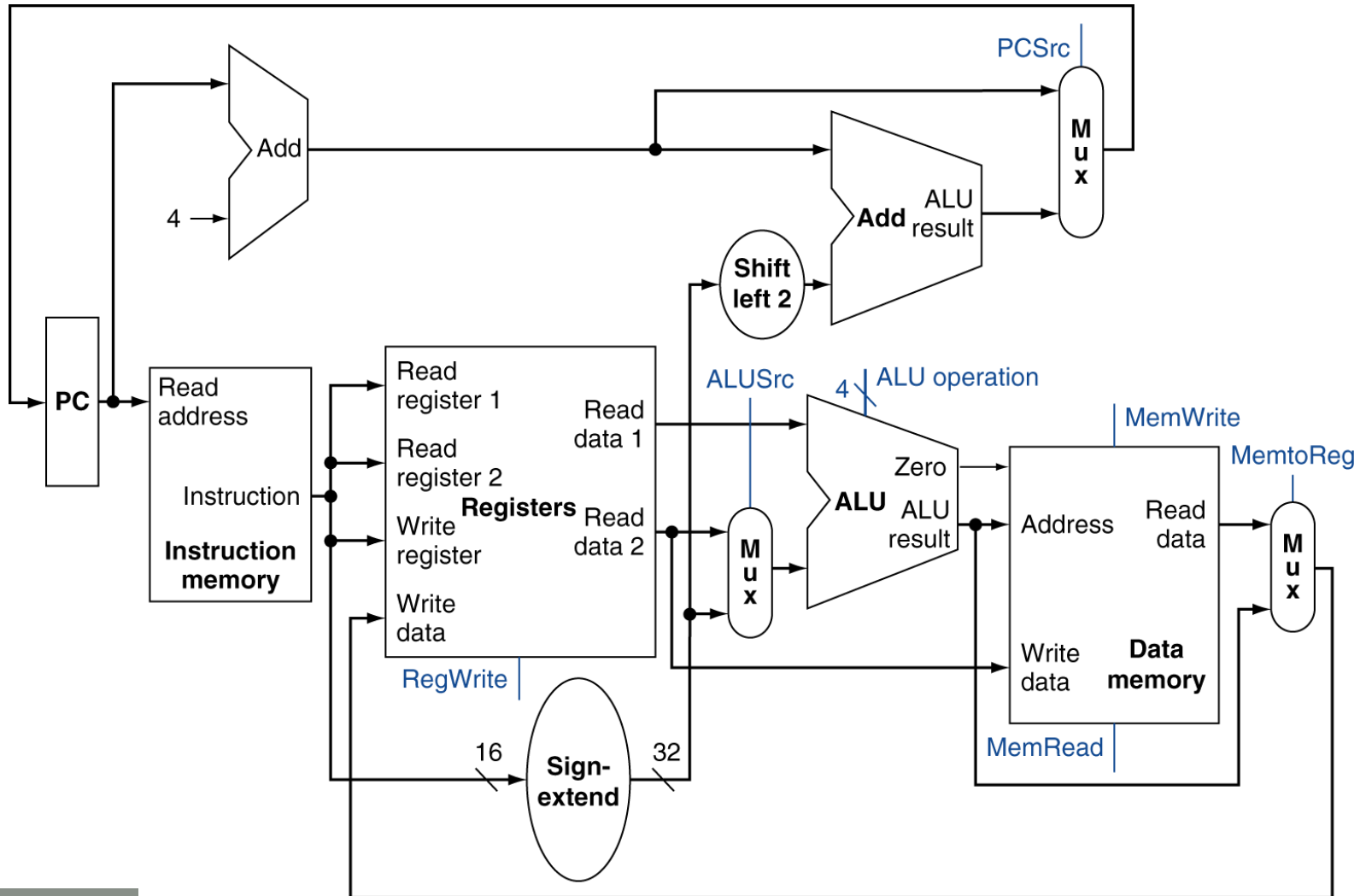

# Full Datapath


lw \$t0, 8(\$t1)

st \$t0, 8(\$t1)

 

# Full Datapath

beq \$t0, \$t1, 8

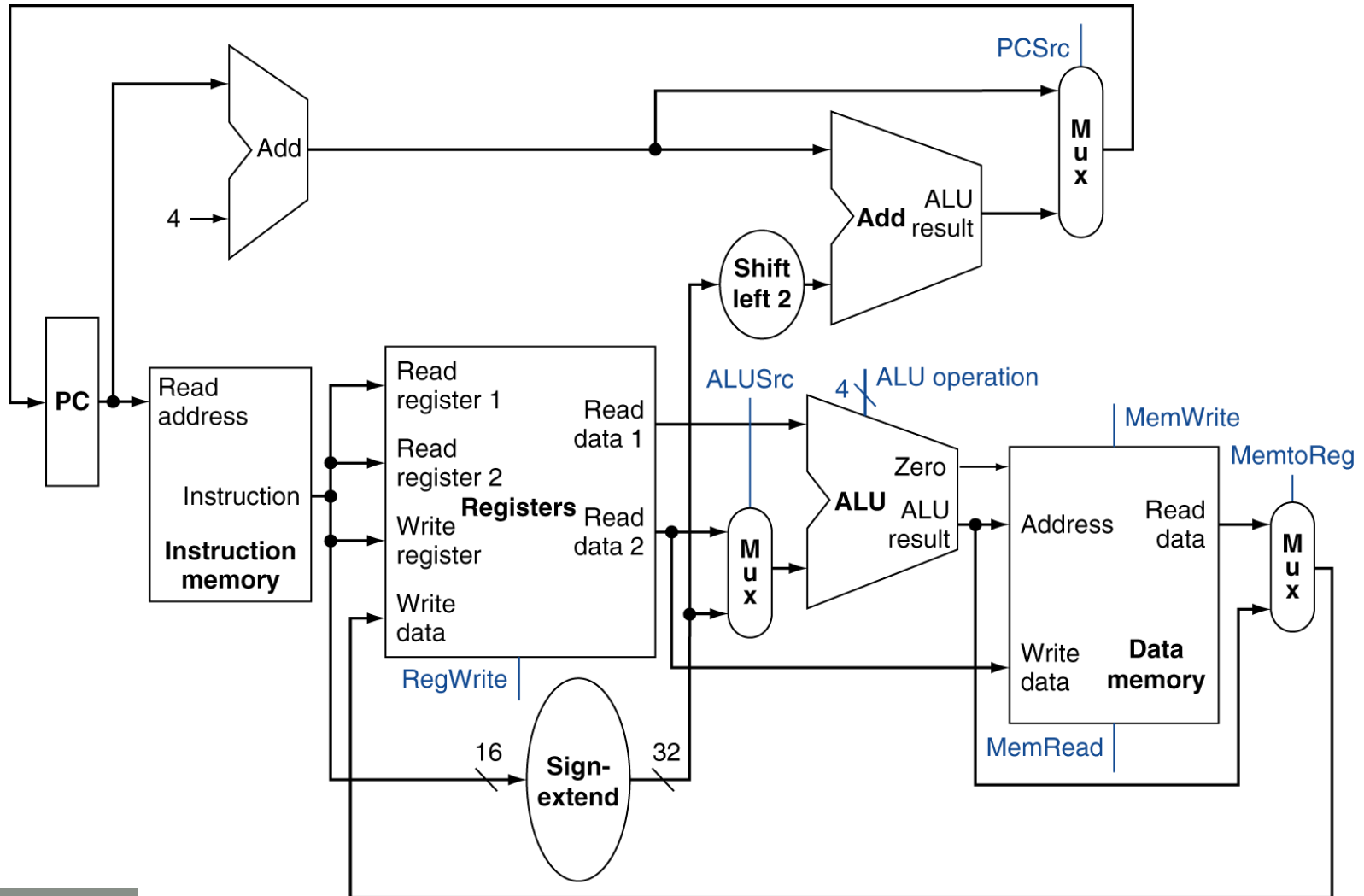

# Building the Datapath

## ☐ What is datapath?

- Major functional units, flow of data between them
- Must execute all MIPS instructions

## ☐ Does it look familiar?

- Because you understand high-level behavior (ISA)

## ☐ Datapath design is high-level organization

- Determine CPI and affect clock cycle time
  - Meaning of single-cycle implementation

# Control Design

## (Datapath and control)

# Building the Datapath


- ❑ Colored control signals (result of datapath design)
  - Use multiplexers where alternate data sources are used for different instructions
  - Enable or disable functional units
  - Select ALU operation
- ❑ How to determine the values of control signals?
  - Opcode (and function code for R-type)
- ❑ What is “instruction decode”?



# Control Signals

| Signal name | Effect when deasserted                                                                       | Effect when asserted                                                                                    |
|-------------|----------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------|
| RegDst      | The register destination number for the Write register comes from the rt field (bits 20:16). | The register destination number for the Write register comes from the rd field (bits 15:11).            |
| RegWrite    | None.                                                                                        | The register on the Write register input is written with the value on the Write data input.             |
| ALUSrc      | The second ALU operand comes from the second register file output (Read data 2).             | The second ALU operand is the sign-extended, lower 16 bits of the instruction.                          |
| PCSrc       | The PC is replaced by the output of the adder that computes the value of $PC + 4$ .          | The PC is replaced by the output of the adder that computes the branch target.                          |
| MemRead     | None.                                                                                        | Data memory contents designated by the address input are put on the Read data output.                   |
| MemWrite    | None.                                                                                        | Data memory contents designated by the address input are replaced by the value on the Write data input. |
| MemtoReg    | The value fed to the register Write data input comes from the ALU.                           | The value fed to the register Write data input comes from the data memory.                              |


# Datapath With Control

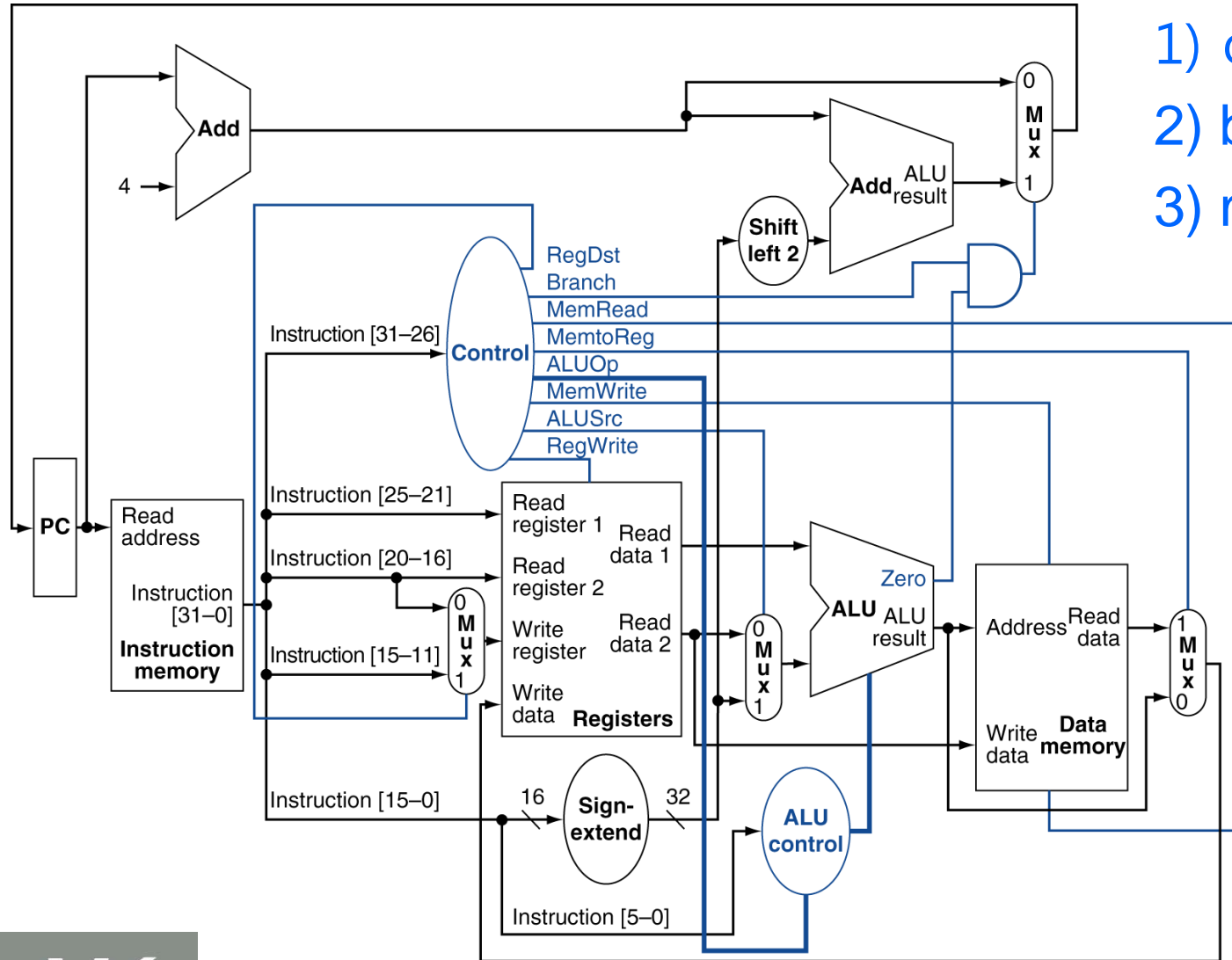

- 1) opcode/funct
- 2) bit 표시,
- 3) mux 추가,
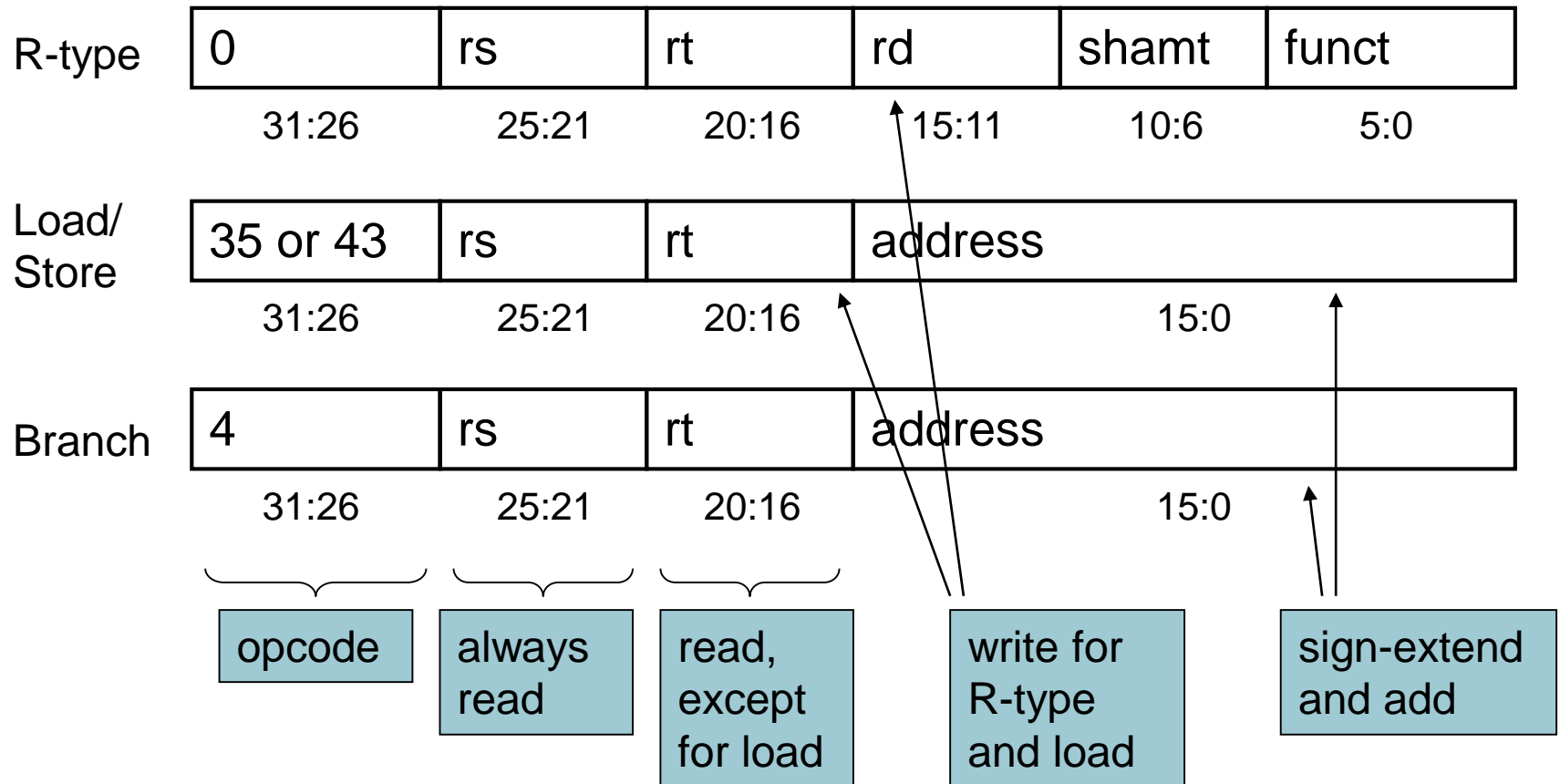
# Building the Datapath

- Datapath and control are derived from instruction



# Instruction Decode

- ❑ Given an instruction, determine values of control signals
  - That's “instruction decode”
- ❑ Not shown in the datapath? (because it's control design)
  - Instead, what have “read two operands (registers)”
    - But we don't know the instruction yet
      - † It does no harm
      - † “**lw, addi**”에서는 하나는 쓰지 않고 버림
- ❑ RISC
  - Parallel instruction decoding and register read

# Control Design (or Decode)

- ❑ Decoding: determine the values of colored control signals
  - Opcode (and function code for R-type)

lw \$1, 100(\$2)

|    |   |   |     |
|----|---|---|-----|
| 35 | 2 | 1 | 100 |
|----|---|---|-----|



|    |    |    |               |
|----|----|----|---------------|
| op | rs | rt | 16-bit offset |
|----|----|----|---------------|

add \$8, \$17, \$18

|   |    |    |   |   |    |
|---|----|----|---|---|----|
| 0 | 17 | 18 | 8 | 0 | 32 |
|---|----|----|---|---|----|

|    |    |    |    |       |       |
|----|----|----|----|-------|-------|
| op | rs | rt | rd | shamt | funct |
|----|----|----|----|-------|-------|

# Control Design (or Decode)

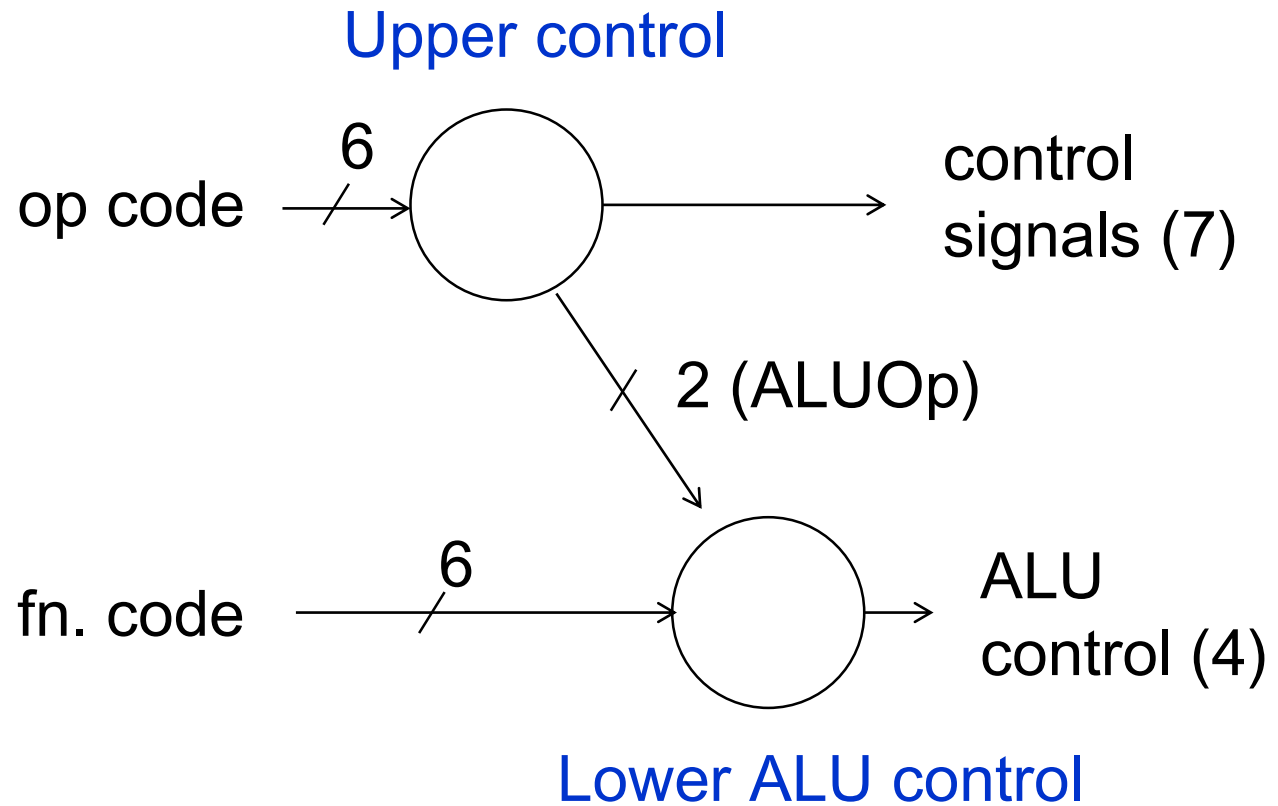 

# Lower ALU Control Unit

# Lower ALU Control Unit


- ❑ Non-R-type instructions: see opcode
  - What should the ALU do with this instruction?
    - Example: lw \$1, 100(\$2)

|    |    |    |               |
|----|----|----|---------------|
| 35 | 2  | 1  | 100           |
| op | rs | rt | 16-bit offset |

- What should the ALU do for “beq”?
- ❑ What about R-type instructions?
  - See function code



# Lower ALU Control Unit

 


- ❑ ALU used for
  - Load/Store: F = add (ALUOp: 00)
  - Branch: F = subtract (ALUOp: 01)
  - R-type: F depends on funct field (ALUOp: 10)
- ❑ ALU designed such that:

| ALU control | Function         |
|-------------|------------------|
| 0000        | AND              |
| 0001        | OR               |
| 0010        | add              |
| 0110        | subtract         |
| 0111        | set-on-less-than |
| 1100        | NOR              |

# Lower ALU Control Unit

- ❑ 2-bit ALUOp derived from opcode

 

| opcode | ALUOp | Operation        | funct  | ALU function     | ALU control |
|--------|-------|------------------|--------|------------------|-------------|
| lw     | 00    | load word        | XXXXXX | add              | 0010        |
| sw     | 00    | store word       | XXXXXX | add              | 0010        |
| beq    | 01    | branch equal     | XXXXXX | subtract         | 0110        |
| R-type | 10    | add              | 100000 | add              | 0010        |
|        |       | subtract         | 100010 | subtract         | 0110        |
|        |       | AND              | 100100 | AND              | 0000        |
|        |       | OR               | 100101 | OR               | 0001        |
|        |       | set-on-less-than | 101010 | set-on-less-than | 0111        |


(input: 8 bits, output: 4 bits)

| Instruction opcode | ALUOp | Instruction operation | Func field | Desired ALU action | ALU control input |
|--------------------|-------|-----------------------|------------|--------------------|-------------------|
| LW                 | 00    | load word             | XXXXXX     | add                | 0010              |
| SW                 | 00    | store word            | XXXXXX     | add                | 0010              |
| Branch equal       | 01    | branch equal          | XXXXXX     | subtract           | 0110              |
| R-type             | 10    | add                   | 100000     | add                | 0010              |
| R-type             | 10    | subtract              | 100010     | subtract           | 0110              |
| R-type             | 10    | AND                   | 100100     | AND                | 0000              |
| R-type             | 10    | OR                    | 100101     | OR                 | 0001              |
| R-type             | 10    | set on less than      | 101010     | set on less than   | 0111              |



| ALUOp  |        | Func field |    |    |    |    |    | Operation |
|--------|--------|------------|----|----|----|----|----|-----------|
| ALUOp1 | ALUOp0 | F5         | F4 | F3 | F2 | F1 | F0 |           |
| 0      | 0      | X          | X  | X  | X  | X  | X  | 0010      |
| 0      | 1      | X          | X  | X  | X  | X  | X  | 0110      |
| 1      | 0      | X          | X  | 0  | 0  | 0  | 0  | 0010      |
| 1      | X      | X          | X  | 0  | 0  | 1  | 0  | 0110      |
| 1      | 0      | X          | X  | 0  | 1  | 0  | 0  | 0000      |
| 1      | 0      | X          | X  | 0  | 1  | 0  | 1  | 0001      |
| 1      | X      | X          | X  | 1  | 0  | 1  | 0  | 0111      |
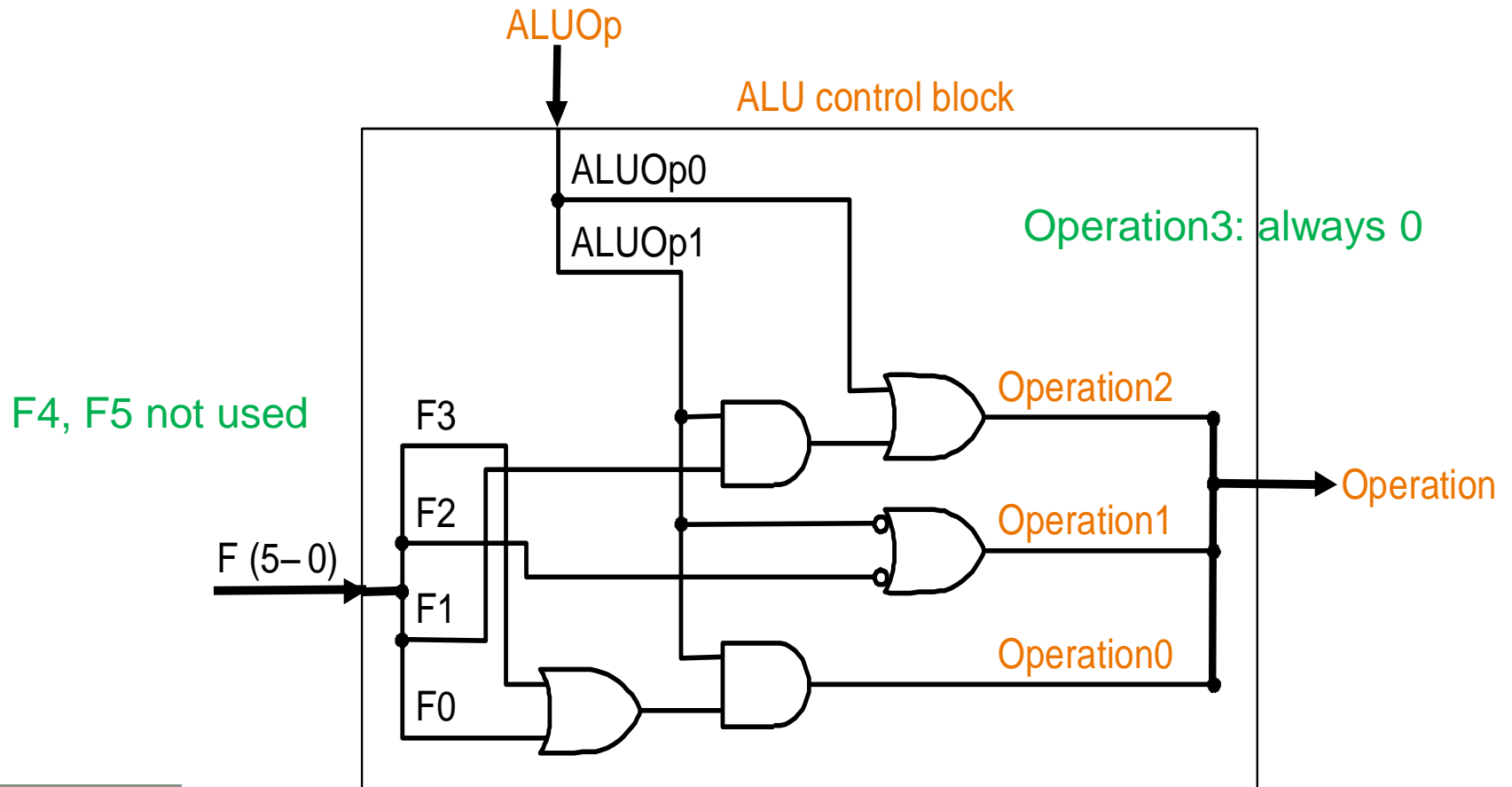
# Lower ALU Control Unit

- ❑ Simple combinational logic (truth tables) – run CAD tools




# Control Design (or Decode) (반복)

  

# Upper Control Unit
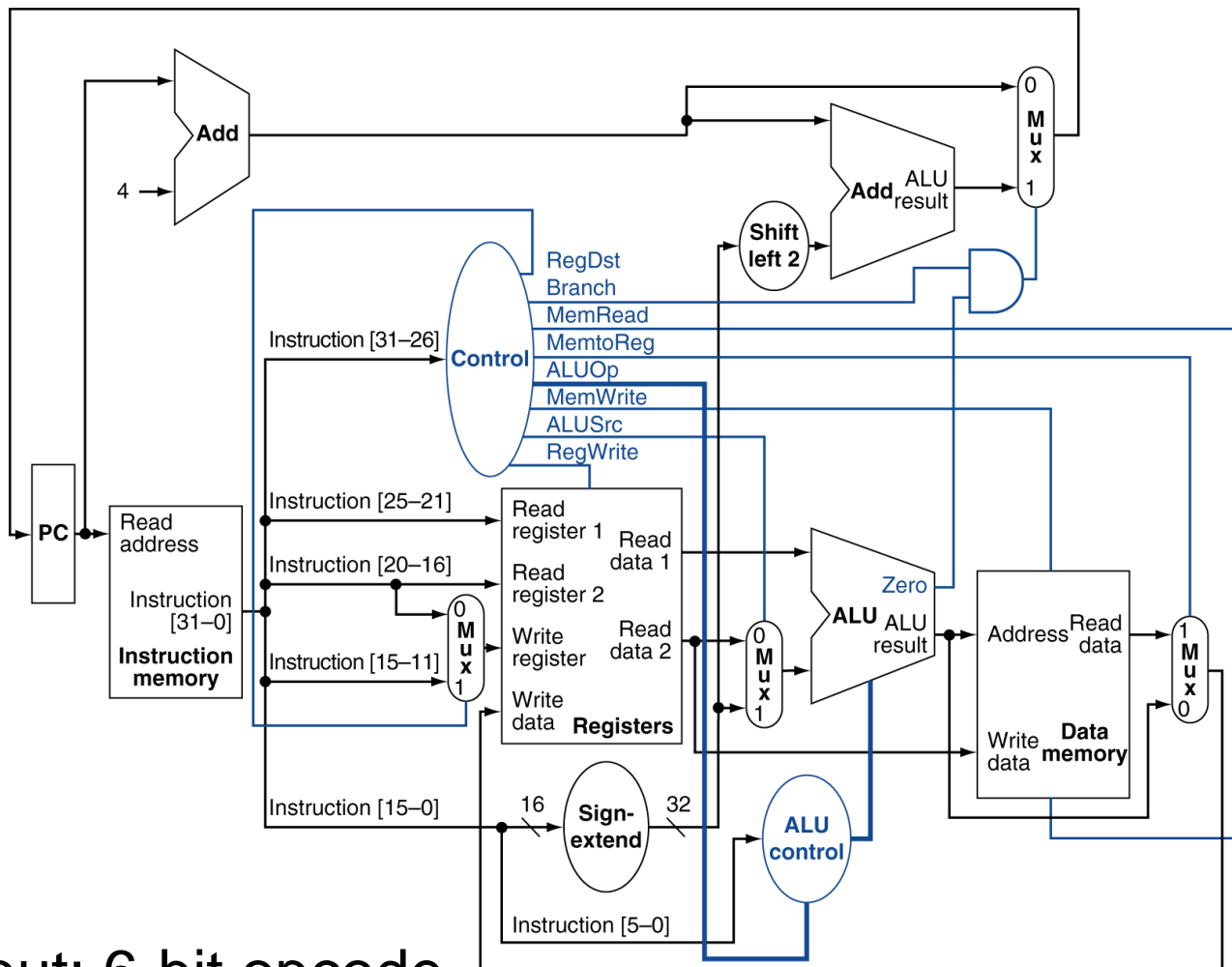
## Design of upper control unit

Imagine what happens in your PC, notebook or smartphone




input: 6-bit opcode

| Instruction | RegDst | ALUSrc | Memto-Reg | Reg-Write | Mem-Read | Mem-Write | Branch | ALUOp1 | ALUOp0 |
|-------------|--------|--------|-----------|-----------|----------|-----------|--------|--------|--------|
| R-format    | 1      | 0      | 0         | 1         | 0        | 0         | 0      | 1      | 0      |
| lw          | 0      | 1      | 1         | 1         | 1        | 0         | 0      | 0      | 0      |
| sw          | X      | 1      | X         | 0         | 0        | 1         | 0      | 0      | 0      |
| beq         | X      | 0      | X         | 0         | 0        | 0         | 1      | 0      | 1      |
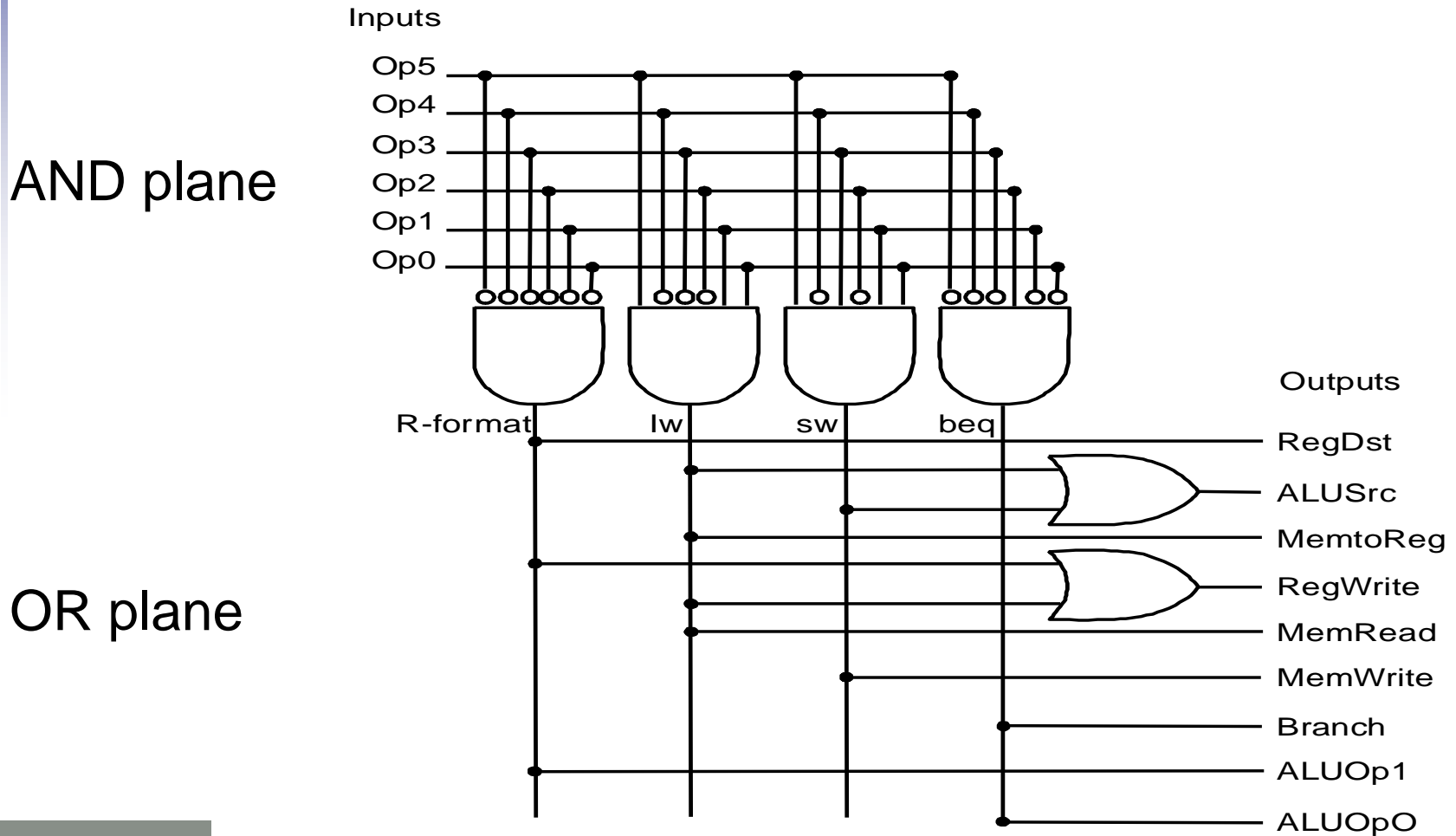
# Upper Control Unit

- ❑ Simple combinational logic (truth tables): hand design





# Control Design

- ❑ Low-level circuit design
  - Determine clock cycle time (not affect IC or CPI)
- ❑ Do you understand the terms datapath and control?
  - ISA designer (architect) consider them in ISA design
    - Higher-level design requires deep understanding of lower-level designs

# MIPS Implementation Done


- ❑ How do we fabricate our processor?
  - What if we visit Intel or Samsung?
    - Same situation when industry develop prototypes
- ❑ Field programmable logic (FPGA) by Altera or Xilinx
  - Software tool (and FPGA chips)
    - VHDL/Verilog description of our design
    - Compile and test
    - Dump to FPGA chips

# Implementing More Instructions

# Implementation 8 Instructions


- ❑ Simple subset, shows most aspects
  - Memory-reference: **lw, sw**
  - Arithmetic-logical: **add, sub, and, or, slt**
  - Control transfer: **beq, (j)**
  
- ❑ What if we want to add “jump” instruction?
  - Same principles
  - Only more datapath and control

# Implementing Jumps

 

- ☐ Jump uses word address
- ☐ Update PC with concatenation of
  - Most-significant 4 bits of PC
  - 26-bit jump address
  - “00”
- ☐ Need an extra control signal decoded from opcode

# Datapath With Jumps Added

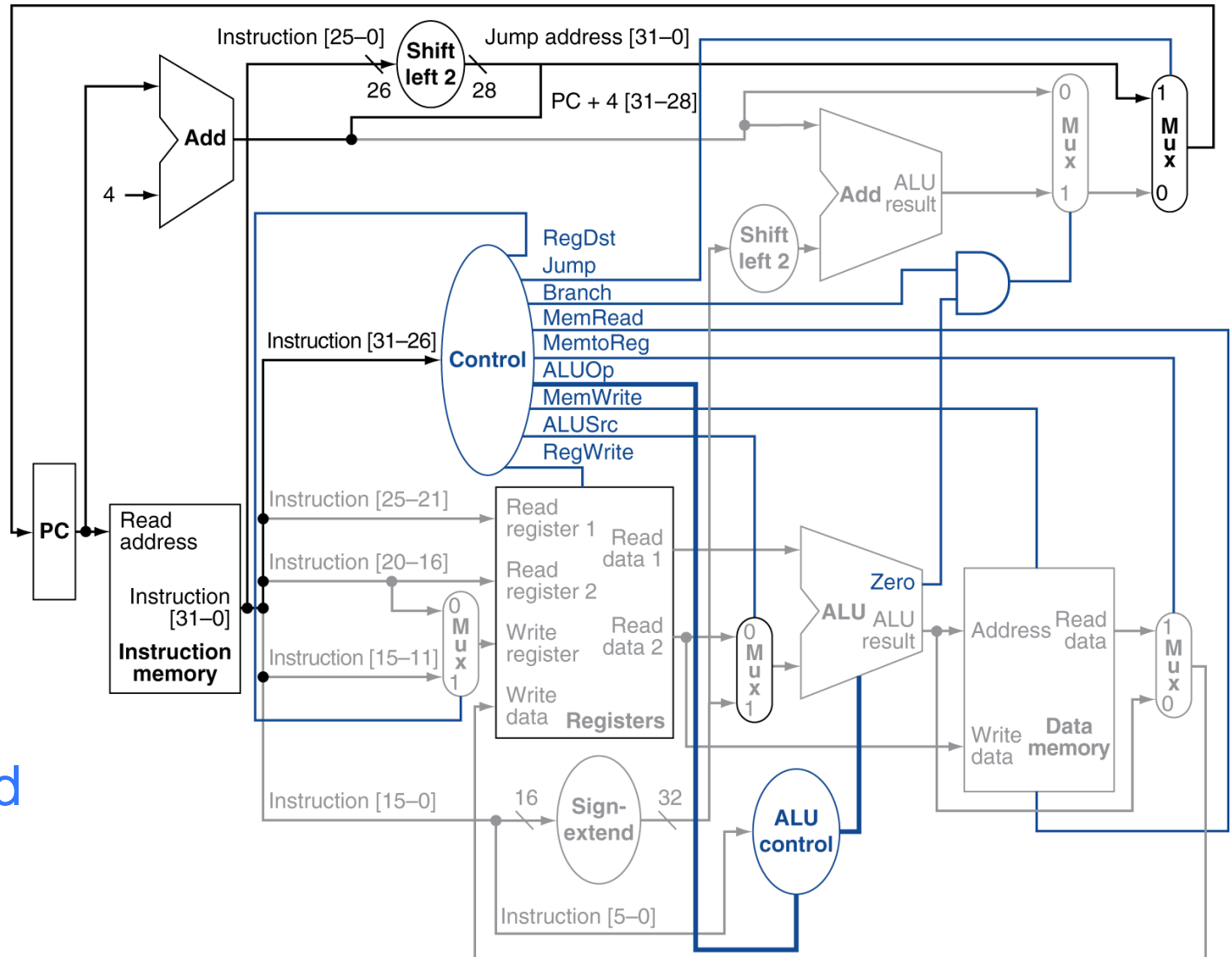

More  
datapath and  
control

# Control for “jump” Instruction

- ❑ One more output signal for control unit
  - Let’s call it “jump”
  - One more column in truth table
- ❑ New jump instruction to implement
  - One more row in truth table

| Instruction | RegDst | ALUSrc | Memto-Reg | Reg-Write | Mem-Read | Mem-Write | Branch | ALUOp1 | ALUOp0 | Jump |
|-------------|--------|--------|-----------|-----------|----------|-----------|--------|--------|--------|------|
| R-format    | 1      | 0      | 0         | 1         | 0        | 0         | 0      | 1      | 0      | 0    |
| lw          | 0      | 1      | 1         | 1         | 1        | 0         | 0      | 0      | 0      | 0    |
| sw          | X      | 1      | X         | 0         | 0        | 1         | 0      | 0      | 0      | 0    |
| beq         | X      | 0      | X         | 0         | 0        | 0         | 1      | 0      | 1      | 0    |
| J           | X      | X      | X         | 0         | 0        | 0         | 0      | X      | X      | 1    |


# Performance Issues

(How good is our implementation?)



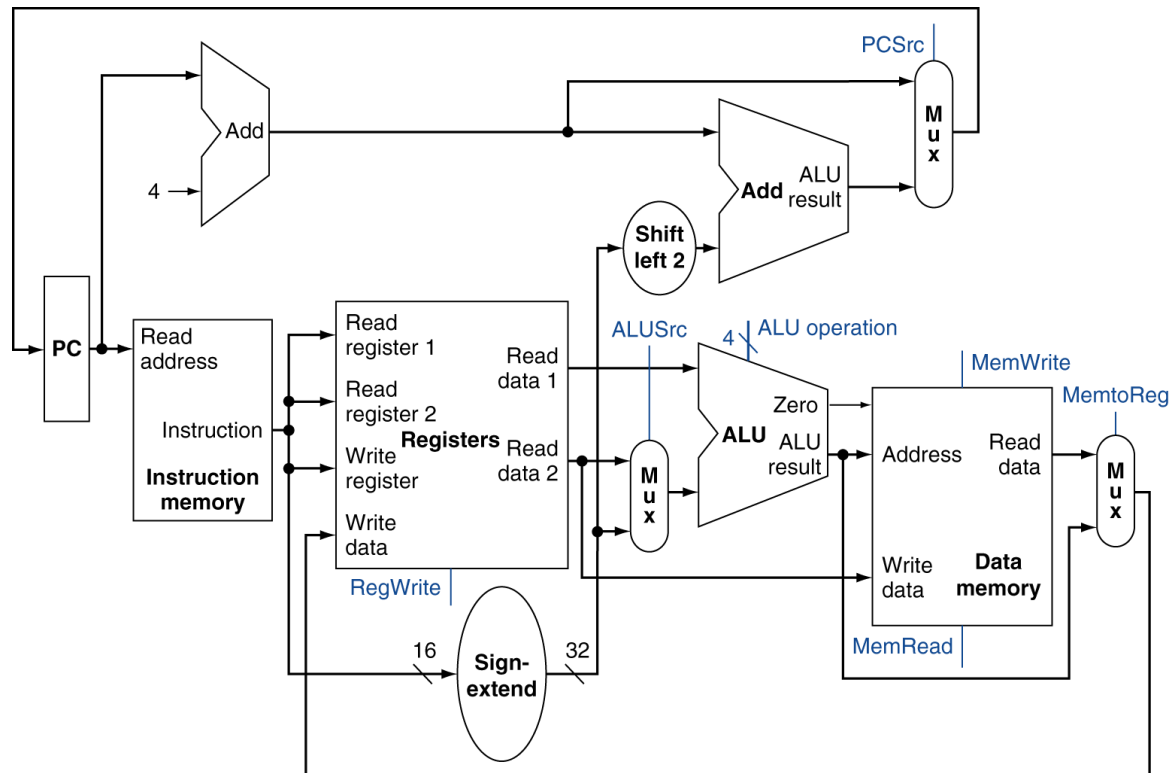
# Single Cycle Implementation

- ❑ Calculate cycle time assuming negligible delays except:
  - Memory access (200ps), ALU and adders (200ps), register file access (100ps)



# Single Cycle Implementation

| Instr    | Instr fetch | Register read | ALU op | Memory access | Register write | Total time |
|----------|-------------|---------------|--------|---------------|----------------|------------|
| lw       | 200ps       | 100 ps        | 200ps  | 200ps         | 100 ps         | 800ps      |
| sw       | 200ps       | 100 ps        | 200ps  | 200ps         |                | 700ps      |
| R-format | 200ps       | 100 ps        | 200ps  |               | 100 ps         | 600ps      |
| beq      | 200ps       | 100 ps        | 200ps  |               |                | 500ps      |

 


- ☐ IM/DM access fast?
- ☐ Register access faster?

# Performance


- ❑ Performance model
  - Execution time =  $IC \times CPI \times \text{clock cycle time}$
  - $CPI = 1$ ,  $cct = 800 \text{ ps}$
- ❑ Longest delay determines clock period
  - Critical path: load instruction
- ❑ Is “load” really the critical path?
  - What about “mult” or FP operations?
 
# High-Level Org.: CPI & Clock Cycle

- ❑ Single-cycle:  $\text{CPI} = 1$ , clock cycle



 - ❑ Multi-cycle:  $\text{CPI} \uparrow$ , clock cycle  $\downarrow$ , overall performance  $\uparrow$   
(IF 하고 저장, ID 하고 저장, ...)




# MIPS Multicycle (Core instruction)

- ❑ Five stages, one step per stage
  1. IF: Instruction fetch from memory
  2. ID: Instruction decode & register read
  3. EX: Execute operation or calculate address
  4. MEM: Access memory operand
  5. WB: Write result back to register

| Instr    | Instr fetch | Register read | ALU op | Memory access | Register write | Total time |
|----------|-------------|---------------|--------|---------------|----------------|------------|
| lw       | 200ps       | 100 ps        | 200ps  | 200ps         | 100 ps         | 800ps      |
| sw       | 200ps       | 100 ps        | 200ps  | 200ps         |                | 700ps      |
| R-format | 200ps       | 100 ps        | 200ps  |               | 100 ps         | 600ps      |
| beq      | 200ps       | 100 ps        | 200ps  |               |                | 500ps      |

# Multicycle vs. Pipeline

 

# Where We Are Heading (부연)

- ❑ Single Cycle Problems:
  - What if we had a more complicated instruction like floating point?
- ❑ Multicycle implementation
  - Use a “smaller” cycle time
  - Different instructions take different numbers of cycles
- ❑ Pipelining (pipelined datapath and control)
  - Overlapped instruction execution ( $CPI = 1$ )
  - Instruction-level parallelism

# Homework #11 (see Class Homepage)

- 1) Write a report summarizing the materials discussed in Topic 4-1 (이번 주 수업 내용)
- 2) Write a report summarizing the materials discussed in Topic 4-2 (이번 주 수업 내용)

\*\* 문장으로 써도 좋고 파워포인트 형태의 개조식 정리도 좋음

- 3) Solve Chapter 4 exercises 4.2, 4.3, 4.5, 4.6 (crosstalk faults, stuck-at-0 faults), 4.7

□ Due: see Blackboard

- Submit electronically to Blackboard



# Class Topics (클래스 홈페이지 참조)

- ❑ Part 1: Fundamental concepts and principles
- ❑ Part 2: 빠른 컴퓨터를 위한 ISA design
  - Topic 1 Computer performance and ISA design (Ch. 1)
  - Topic 2 RISC (MIPS) instruction set (Chapter 2)
  - Topic 3 Computer arithmetic and ALU (Chapter 3)
- ❑ Part 3: ISA 의 효율적인 구현 (pipelining, cache memory)
  - Topic 4 Processor design (Chapter 4)
    - Single cycle implementation
    - Pipelined implementation
  - Topic 5 Memory system design (Chapter 5)